

MIC05: Teste de Circuitos Integrados

Marcelo Lubaszewski

PGMicro - UFRGS

2007/II

Lecture 2 - Fault Modeling

- Defects, Errors, and Faults
- Why model faults?
- Some real defects in VLSI and PCB
- Common fault models
- Stuck-at faults
 - Single stuck-at faults
 - Fault equivalence
 - Fault dominance and checkpoint theorem
 - Classes of stuck-at faults and multiple faults
- Other Common Faults
- Faults in FPGAs

Defects, Faults, and Errors

- **Defect:** unintended difference between the implemented HW and its intended design
 - May or may not cause a system failure
- **Fault:** representation of a defect at the abstracted function level



Defects, Faults, and Errors

- **Error:** Manifestation of a fault that results in incorrect circuit (system) outputs or states
 - Caused by faults
- **Failure:** Deviation of a circuit or system from its specified behavior
 - Fails to do what it should do
 - Caused by an error
- Defect --> Fault ---> Error ---> Failure


Some Real Defects in Chips

- Processing defects
 - Missing contact windows
 - Parasitic transistors
 - Oxide breakdown
 - . . .
- Material defects
 - Bulk defects (cracks, crystal imperfections)
 - Surface impurities (ion migration)
 - . . .
- Time-dependent defects
 - Dielectric breakdown
 - Electromigration
 - . . .
- Packaging defects
 - Contact degradation
 - Seal leaks. . .

Ref.: M. J. Howes and D. V. Morgan, *Reliability and Degradation - Semiconductor Devices and Circuits*, Wiley, 1981.

 Example


- Defect: a short to ground
- Fault: signal b stuck at logic 0



- Error: *z* has the wrong value if $a = b = 1$

 Example

- Defect: a short to ground
- Fault: signal b stuck at logic 0



- Error: *z* has the wrong value if $a = b = 1$
- **But, if $a = 0$, fault exists, but no error!**

Why Model Faults?

- Real defects (often mechanical) too numerous and often not analyzable
- A fault model identifies targets for testing
 - Model faults most likely to occur
- Fault model limits the scope of test generation
 - Create tests only for the modeled faults
- A fault model makes analysis possible
 - Associate specific defects with specific test patterns
- Effectiveness measurable by experiments
 - Fault coverage can be computed for specific test patterns to reflect its effectiveness

Common Fault Models


- Single stuck-at faults
- Transistor open and short faults
- Memory faults
- PLA faults (stuck-at, cross-point, bridging)
- Functional faults (processors)
- Delay faults (transition, path)
- Analog faults

Single Stuck-at Fault

- Three properties define a single stuck-at fault
 - Only one line is faulty
 - The faulty line is permanently set to 0 or 1
 - The fault can be at an input or output of a gate


Single Stuck-at Fault

 - Three properties define a single stuck-at fault
 - Only one line is faulty
 - The faulty line is permanently set to 0 or 1
 - The fault can be at an input or output of a gate
- Example: NAND gate has 3 fault sites (●) and 6 single stuck-at faults




Single Stuck-at Fault

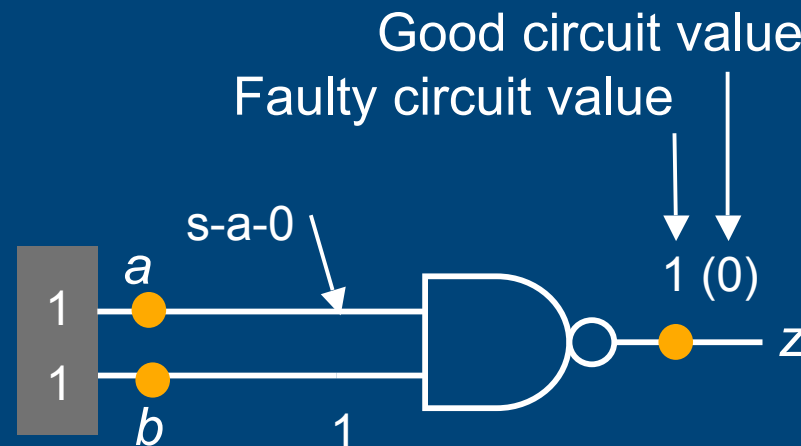- Three properties define a single stuck-at fault
 - Only one line is faulty
 - The faulty line is permanently set to 0 or 1
 - The fault can be at an input or output of a gate
- Example: NAND gate has 3 fault sites (●) and 6 single stuck-at faults




Single Stuck-at Fault

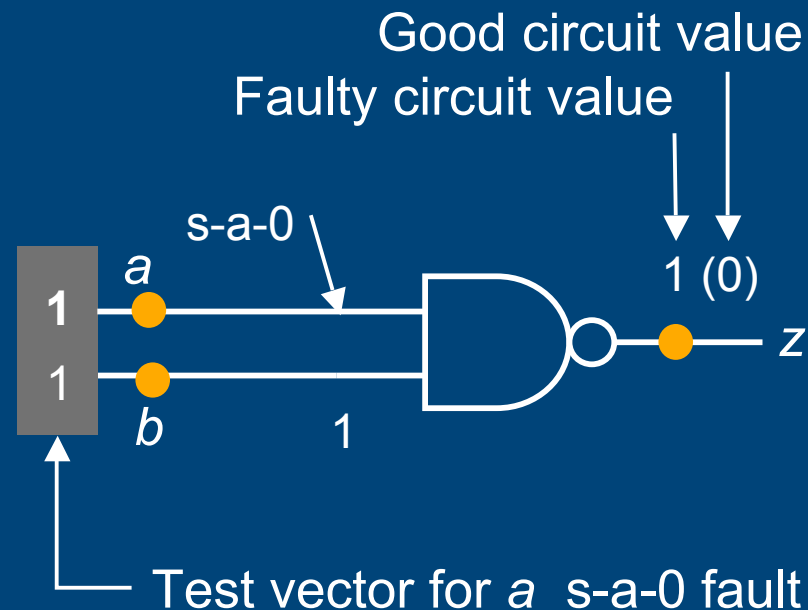- Three properties define a single stuck-at fault
 - Only one line is faulty
 - The faulty line is permanently set to 0 or 1
 - The fault can be at an input or output of a gate
- Example: NAND gate has 3 fault sites (●) and 6 single stuck-at faults




Single Stuck-at Fault

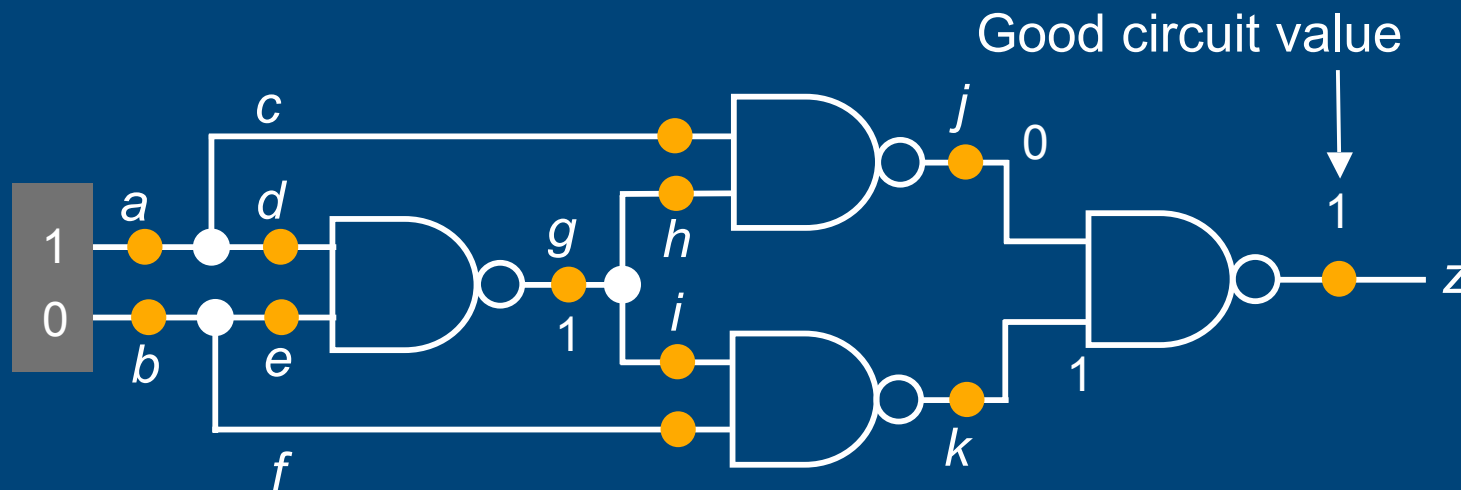Example: XOR circuit has 12 fault sites and 24 single stuck-at faults



Single Stuck-at Fault

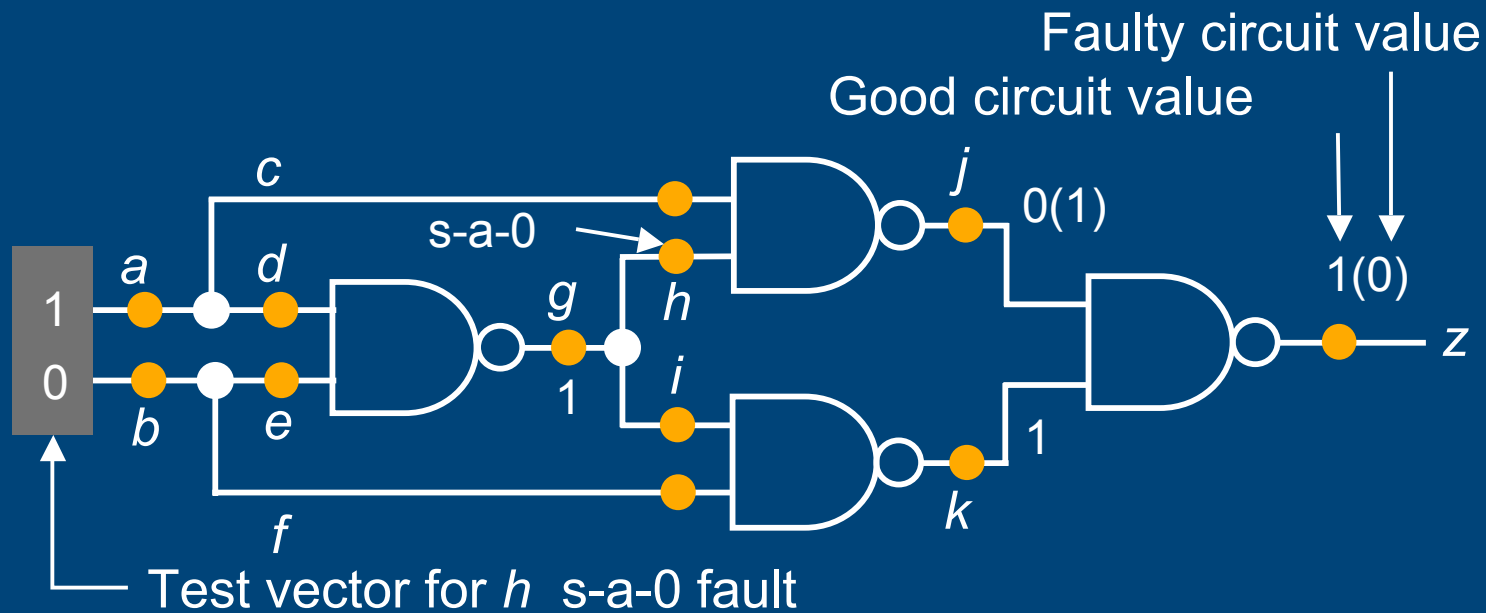
Example: XOR circuit has 12 fault sites and 24 single stuck-at faults










Fault Equivalence

- Fault equivalence: Two faults f_1 and f_2 are equivalent if all tests that detect f_1 also detect f_2 .
- If faults f_1 and f_2 are equivalent then the corresponding faulty functions are identical.
- Fault collapsing: All single faults of a logic circuit can be divided into disjoint equivalence subsets, where all faults in a subset are mutually equivalent. A collapsed fault set contains one fault from each equivalence subset.


Equivalence Rules

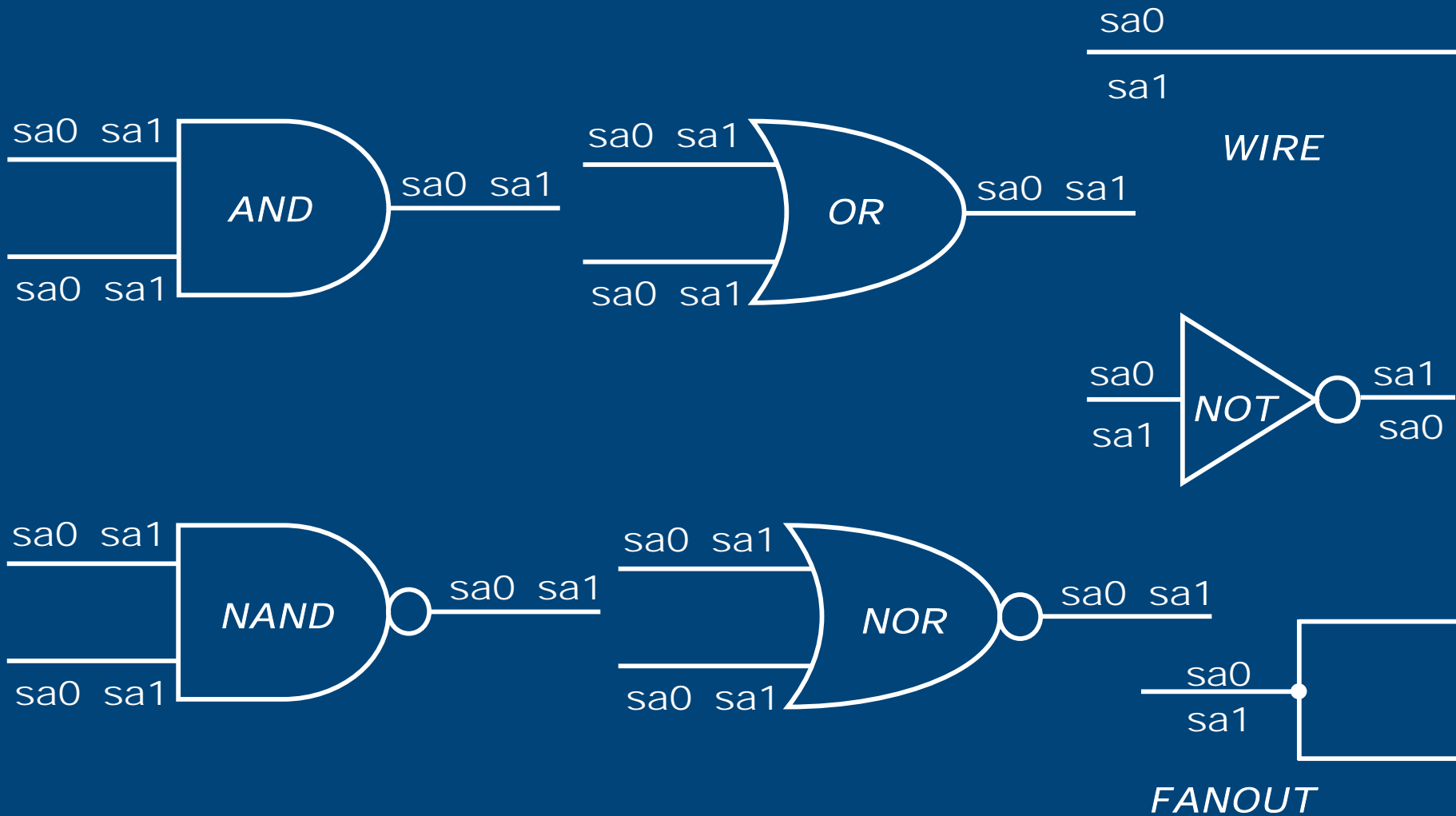


Equivalence Rules

 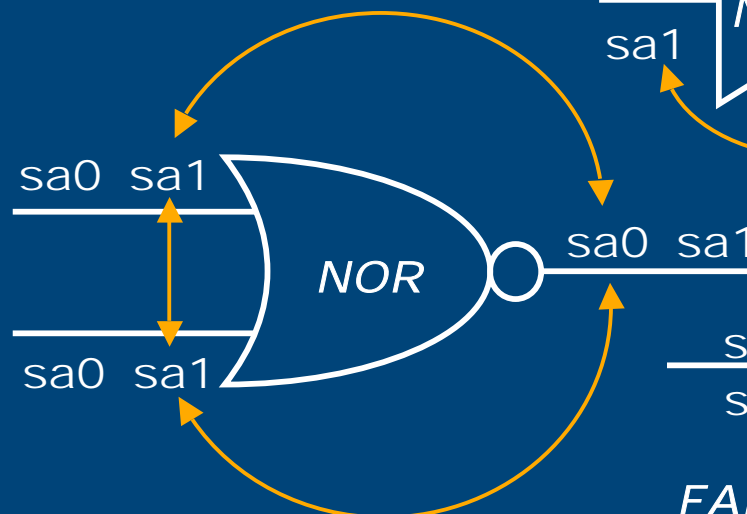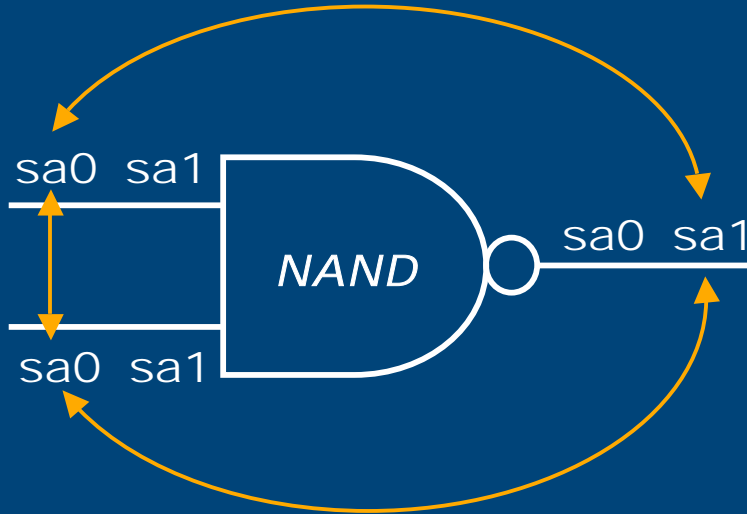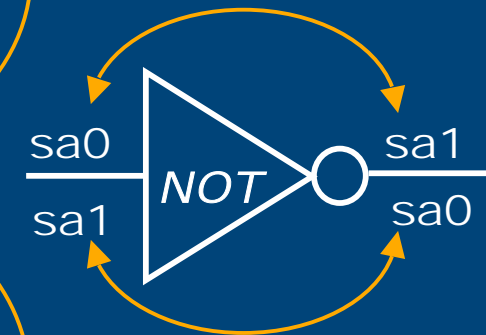  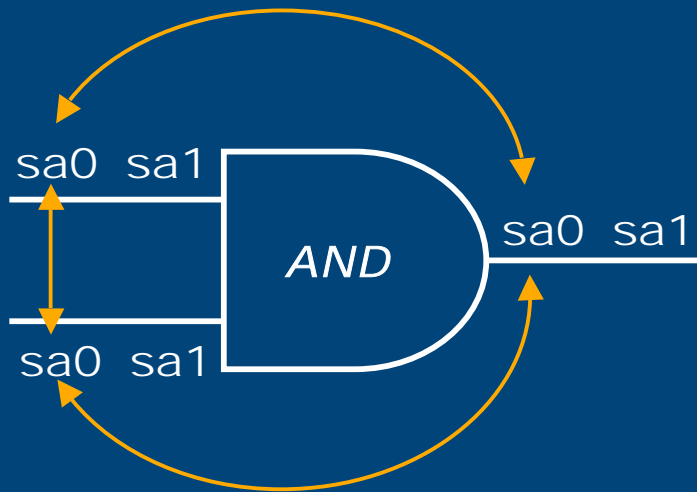


Equivalence Example

 


Equivalence Example

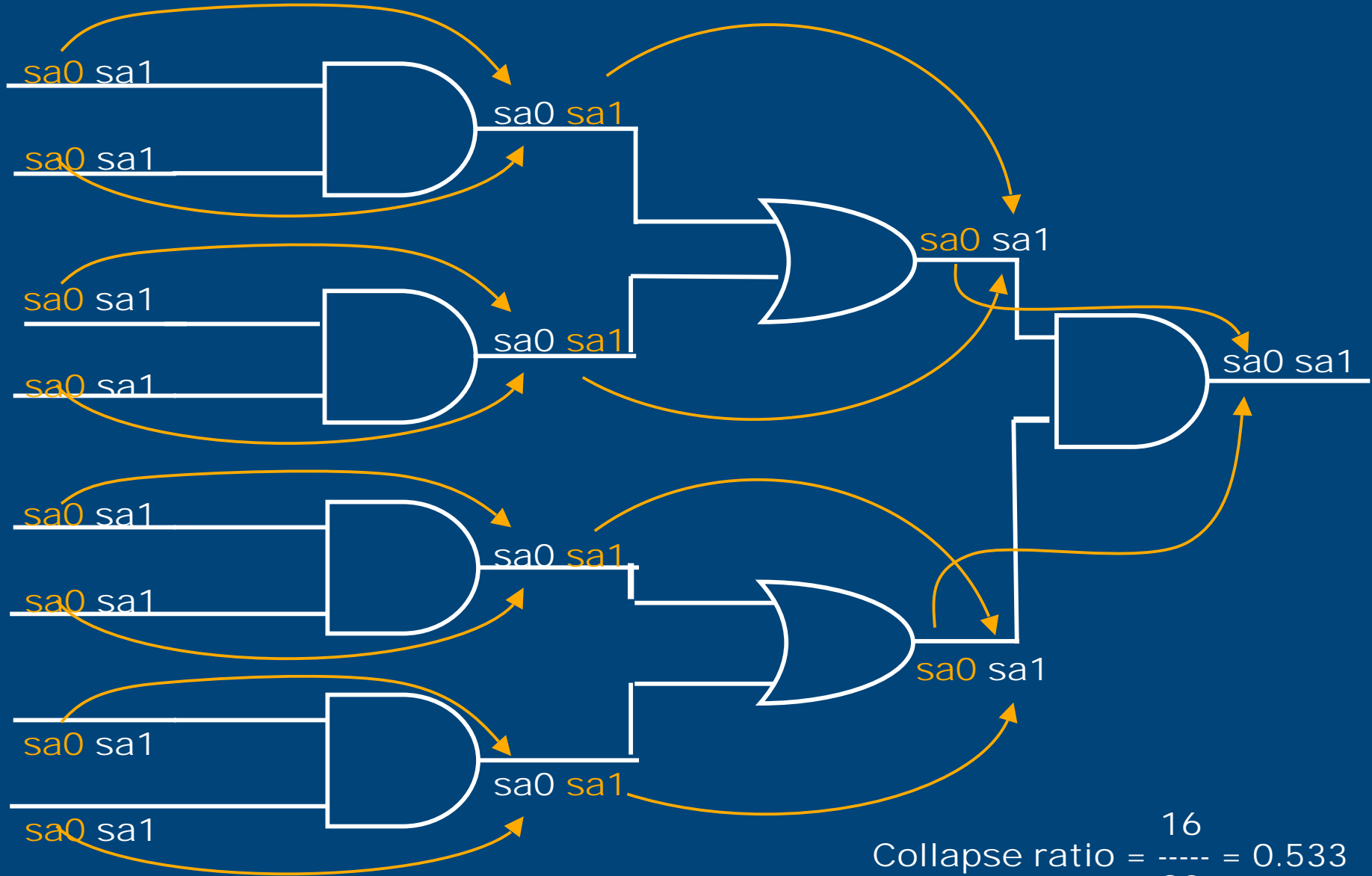

Equivalence Example

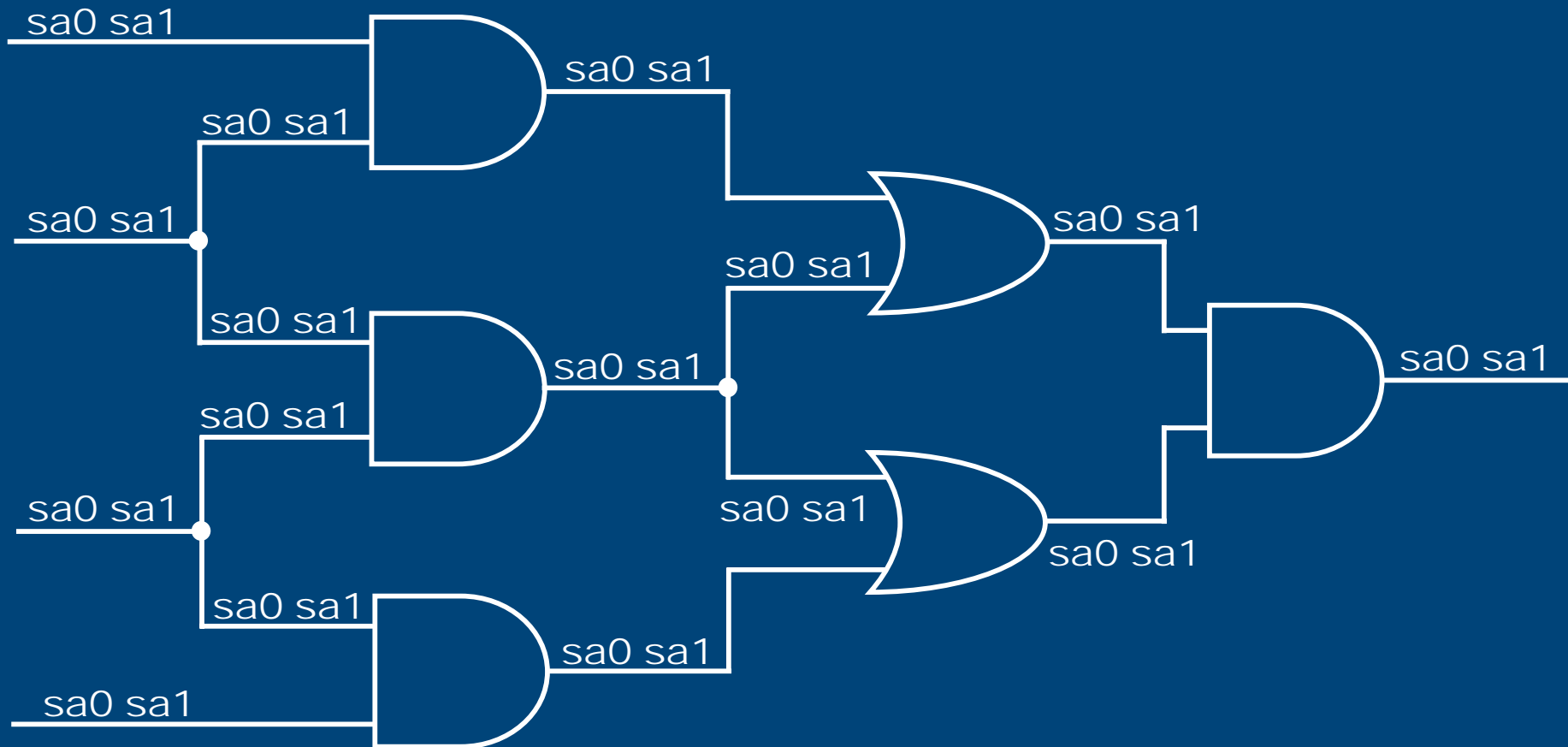

Equivalence Example

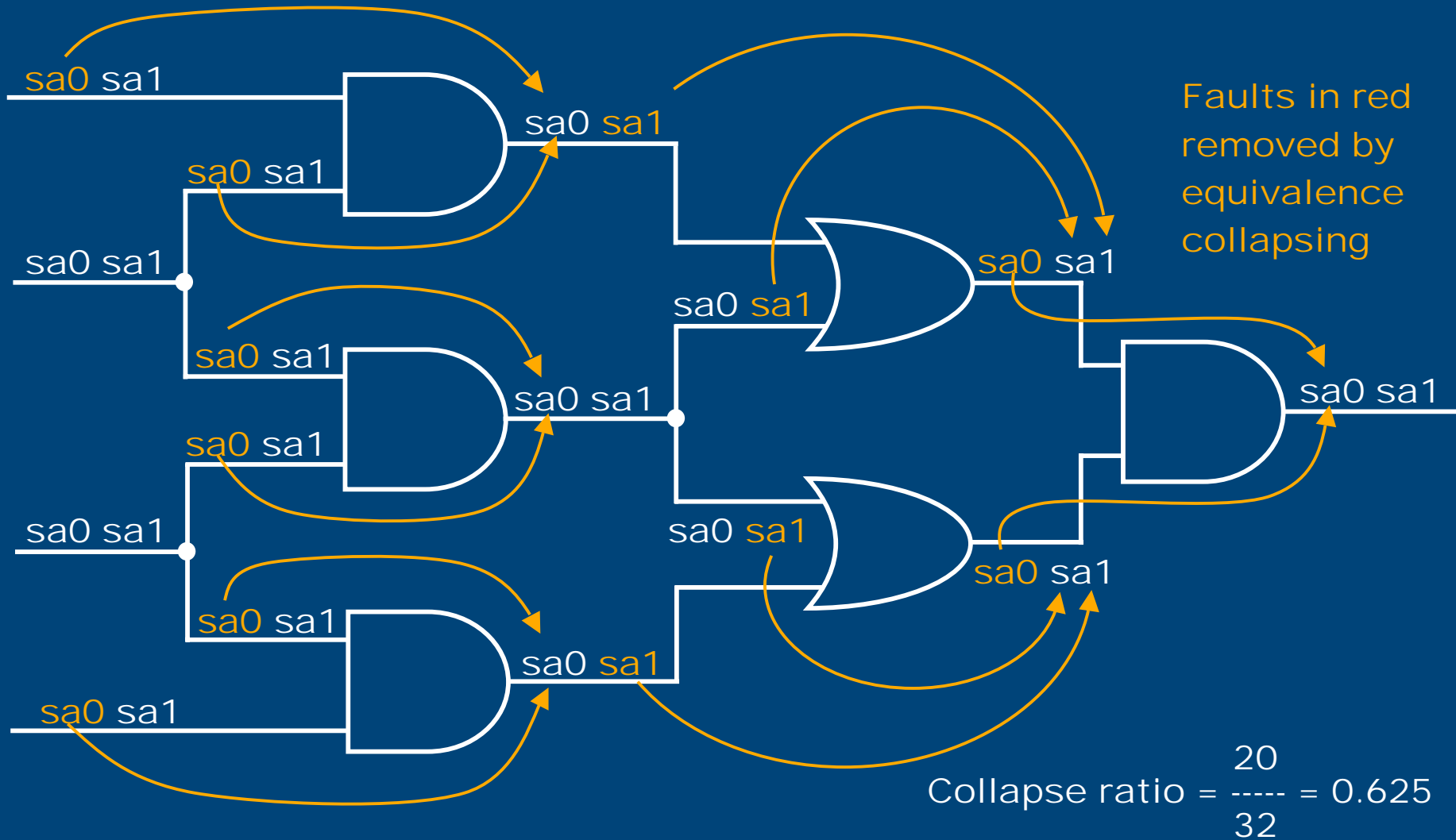


Fault Dominance

- If all tests of some fault $F1$ detect another fault $F2$, then $F2$ is said to dominate $F1$.
- Dominance fault collapsing: If fault $F2$ dominates $F1$, then $F2$ is removed from the fault list.
- When dominance fault collapsing is used, it is sufficient to consider only the input faults of Boolean gates. See the next example.


Dominance Example



Dominance Example

 


Dominance Example

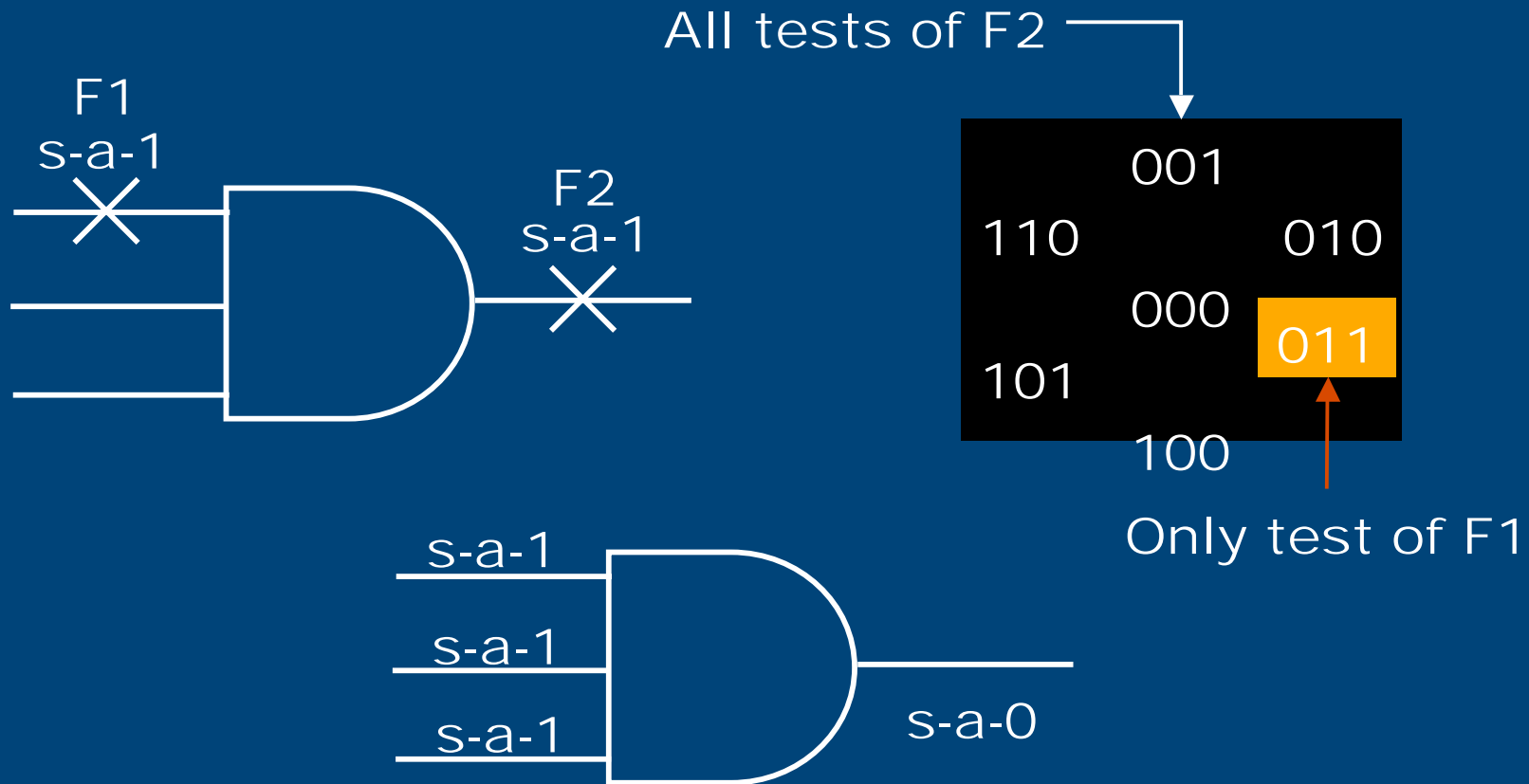


A dominance collapsed fault set


Dominance Example

 


Dominance Example

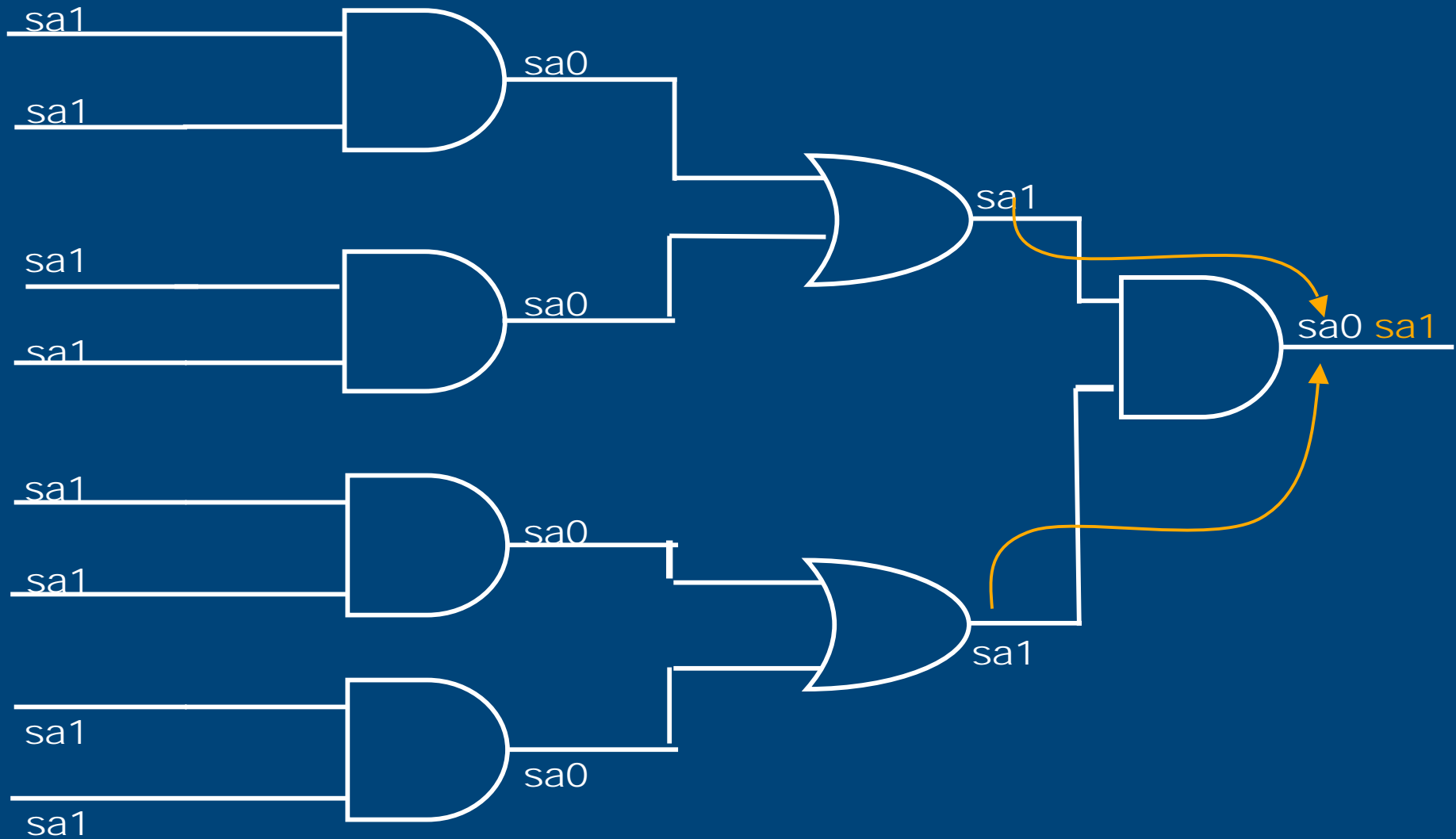

Dominance Example

 


Dominance Example

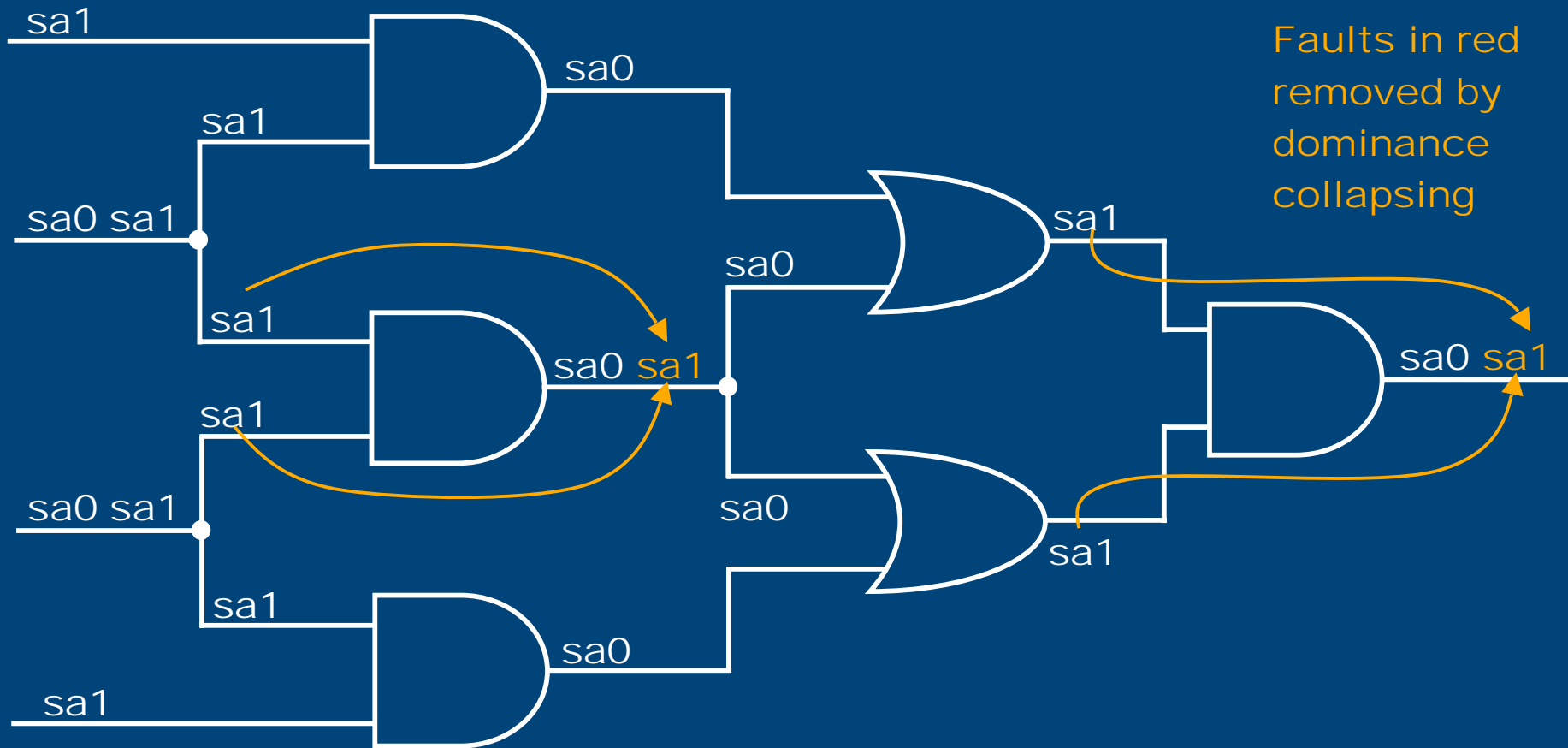

Checkpoints

 
- Primary inputs and fanout branches of a combinational circuit are called *checkpoints*.



Total fault sites = 16


Checkpoints

 - Primary inputs and fanout branches of a combinational circuit are called *checkpoints*.



Checkpoints

 
- Primary inputs and fanout branches of a combinational circuit are called *checkpoints*.




Checkpoint theorem: A test set that detects all single (multiple) stuck-at faults on all checkpoints of a combinational circuit, also detects all single (multiple) stuck-at faults in that circuit.

Bridging Faults

 - Two or more normally distinct points (lines) are shorted together
 - Logic effect depends on technology
 - Wired- AND for TTL




- Wired- OR for ECL

 


- CMOS?

CMOS Transistor Stuck- Short

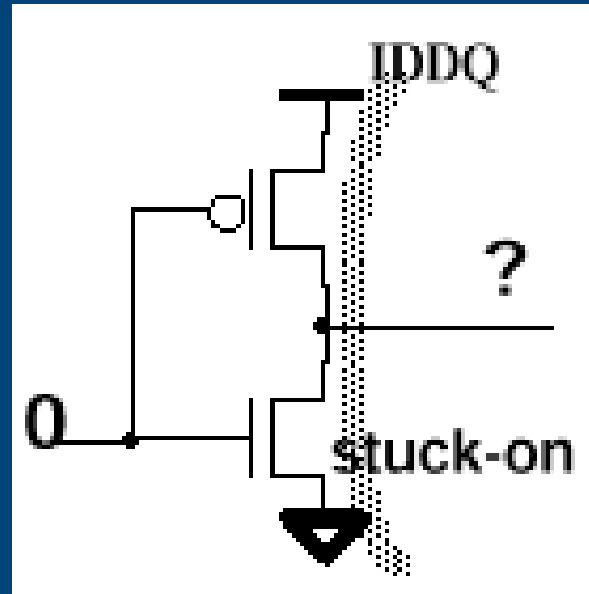

- Transistor stuck- on may cause ambiguous logic level
 - depends on the relative impedances of the pull- up & pull- down networks
- When input is low, both P and N transistors are conducting causing increased quiescent current, called IDDQ fault.

CMOS Transistor Stuck- OPEN

 


- Transistor stuck- open may cause output floating.

Functional Faults

- Fault effects modeled at a higher level than logic for function modules, such as
 - Decoders
 - Multiplexers
 - Adders
 - Counters
 - RAMs
 - ROMs


Functional Faults of Decoder

 - $f(L_i / L_j)$: Instead of line L_i , Line L_j is selected
- $f(L_i / L_i + L_j)$: In addition to L_i , L_j is selected
- $f(L_i / 0)$: None of the lines are selected



Memory Faults

 
- Pattern- sensitive faults: the presence of a faulty signal depends on the signal values of the nearby points
 - Most common in DRAMs



- Adjacent cell coupling faults
 - Pattern sensitivity between a pair of cells


Gate- Delay- Fault

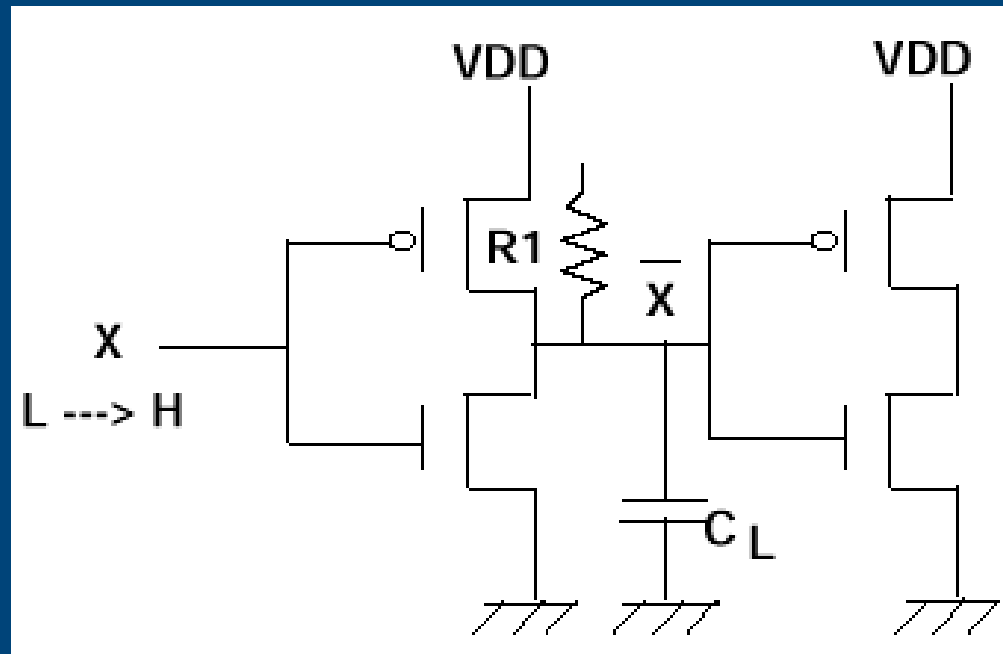- Slow to rise, slow to fall
 - x is slow to rise when channel resistance R1 is abnormally high




Path- Delay- Fault

 - Propagation delay of the path exceeds the clock interval.
- The number of paths grows exponentially with the number of gates.




State Transition Graph

 - Each state transition is associated with a 4-tuple:
 - source state, input, output, destination state




Single State Transition Fault Model

 - A fault causes a single state transition to a wrong destination state.



Faults in FPGAs


FPGA building blocks:

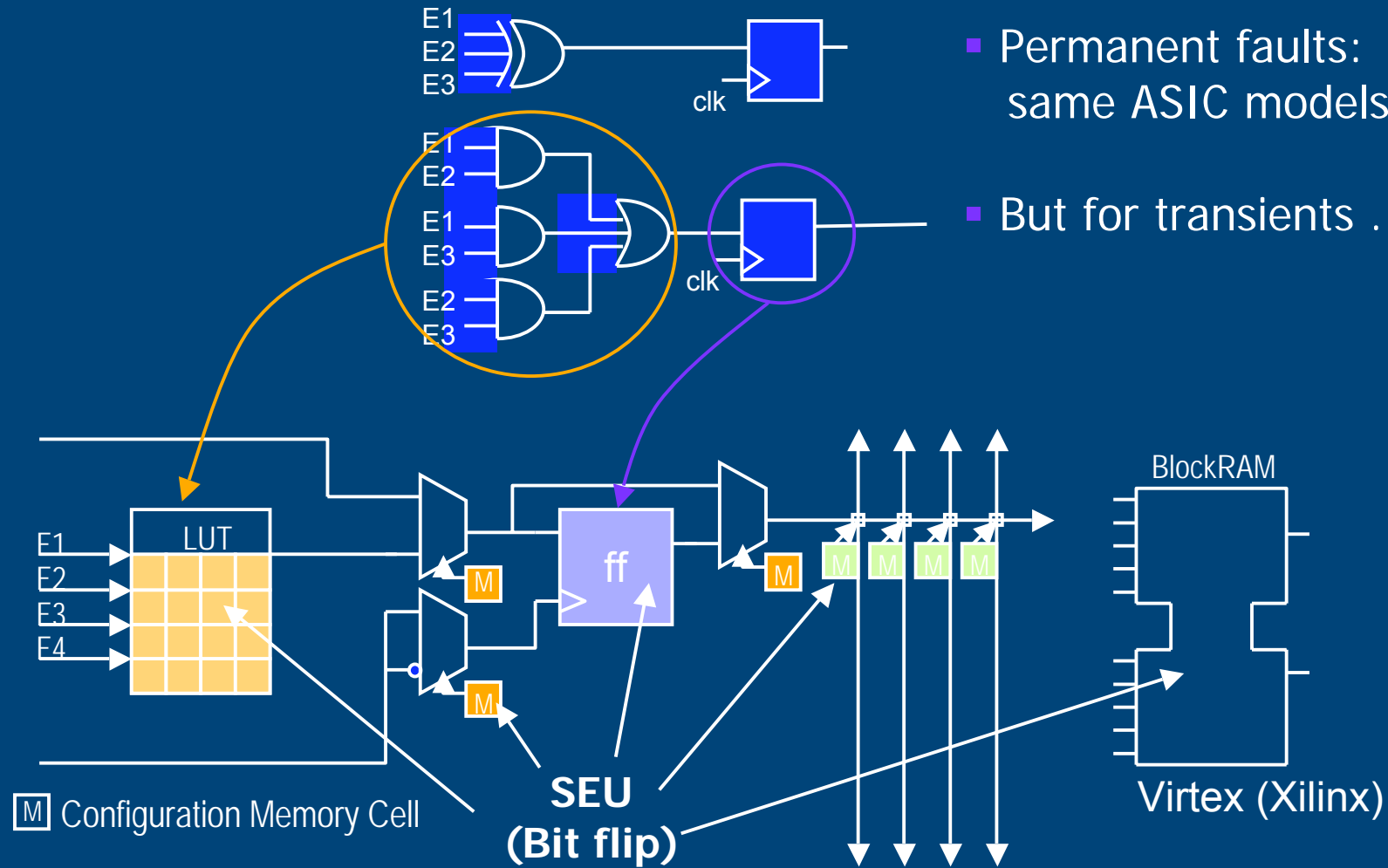

Effect of Transients in SRAM-based FPGAs

CLB Comb. Logic:

~0.5 % of the FPGA sensitive area

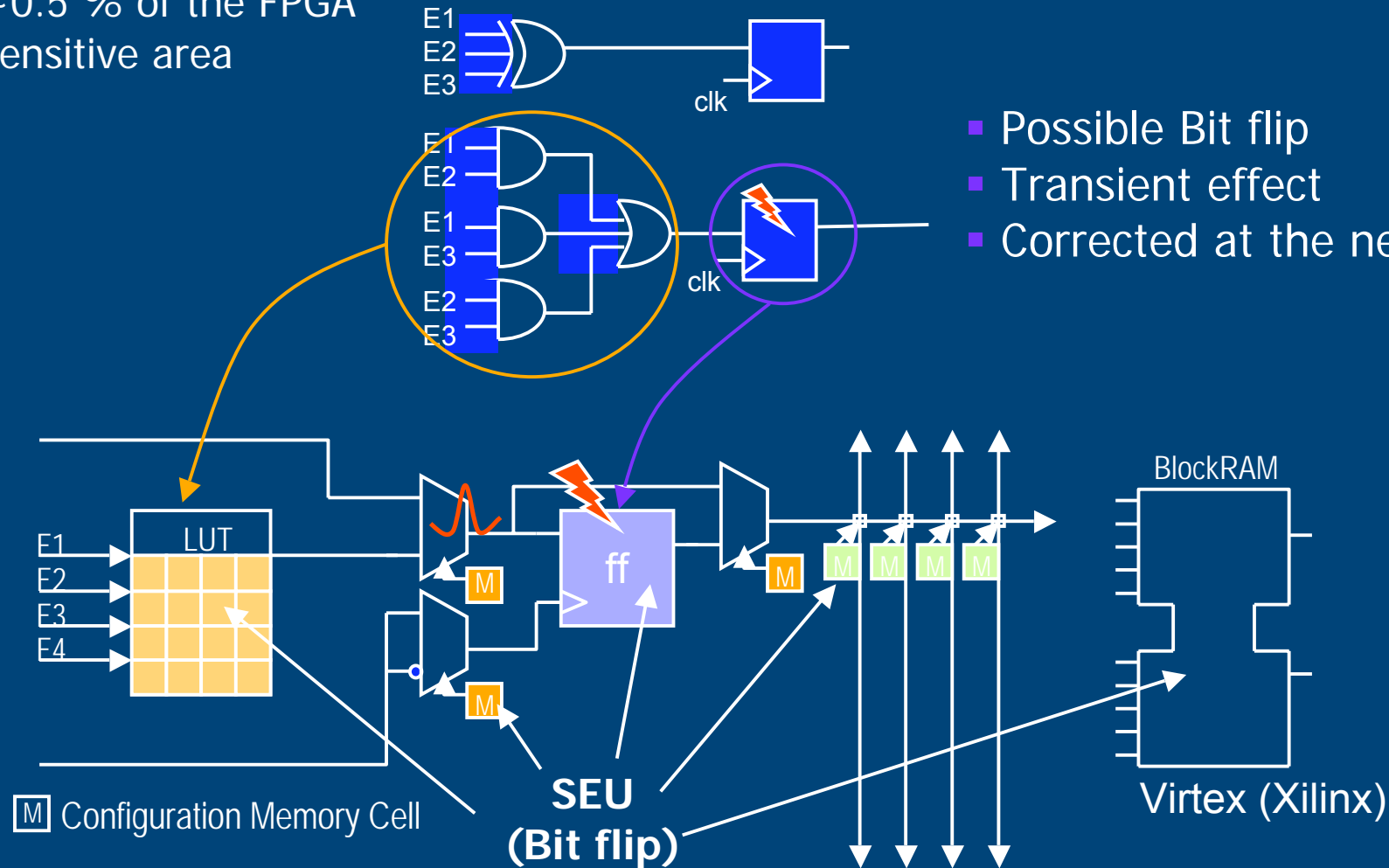


- Possible Bit flip
- Transient effect
- Corrected at the next load

Effect of Transients in SRAM-based FPGAs

CLB Flip-flops:


~0.5 % of the FPGA sensitive area

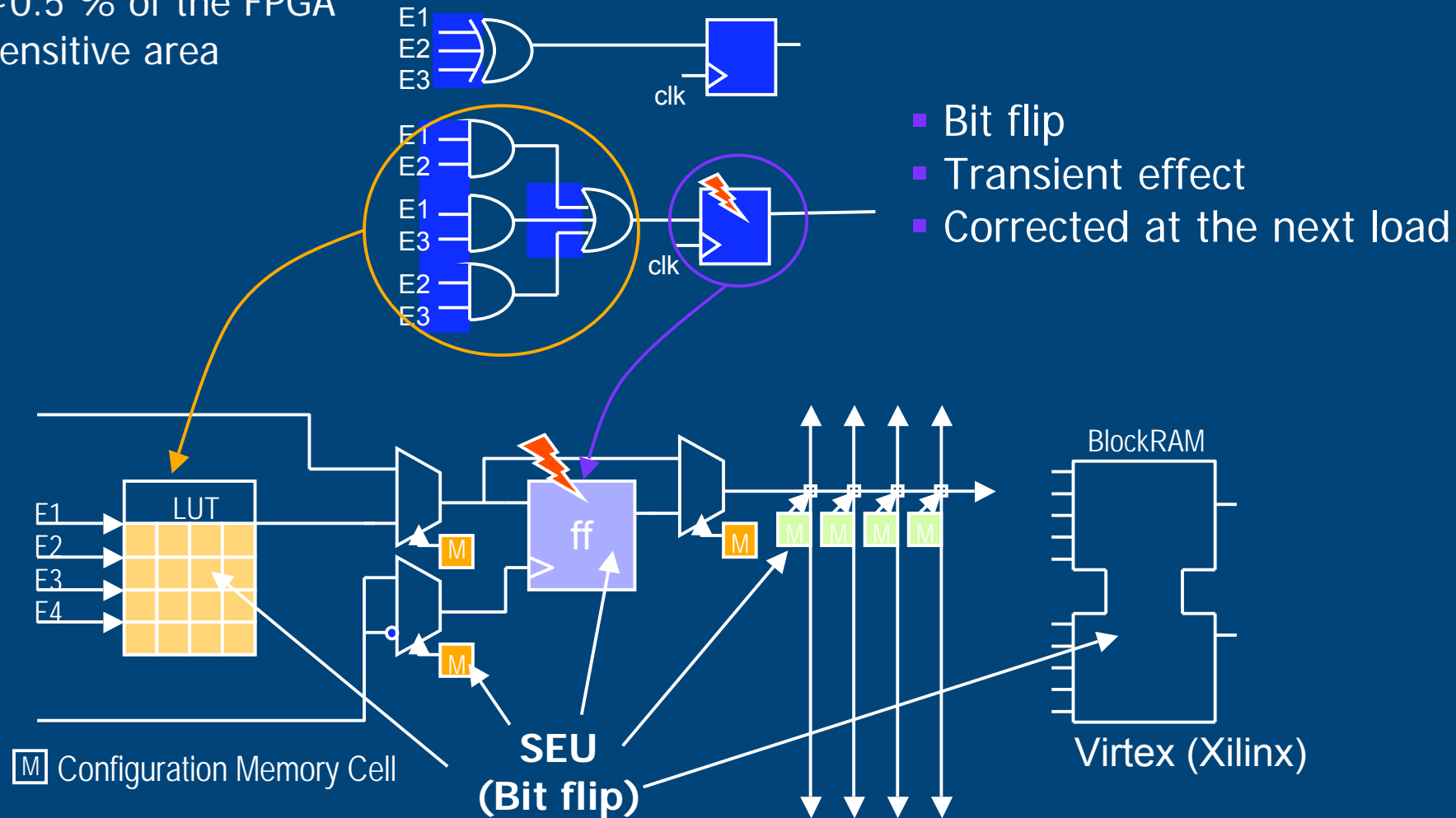

Effect of Transients in SRAM-based FPGAs


CLB LUTs:

~8% of the FPGA sensitive area

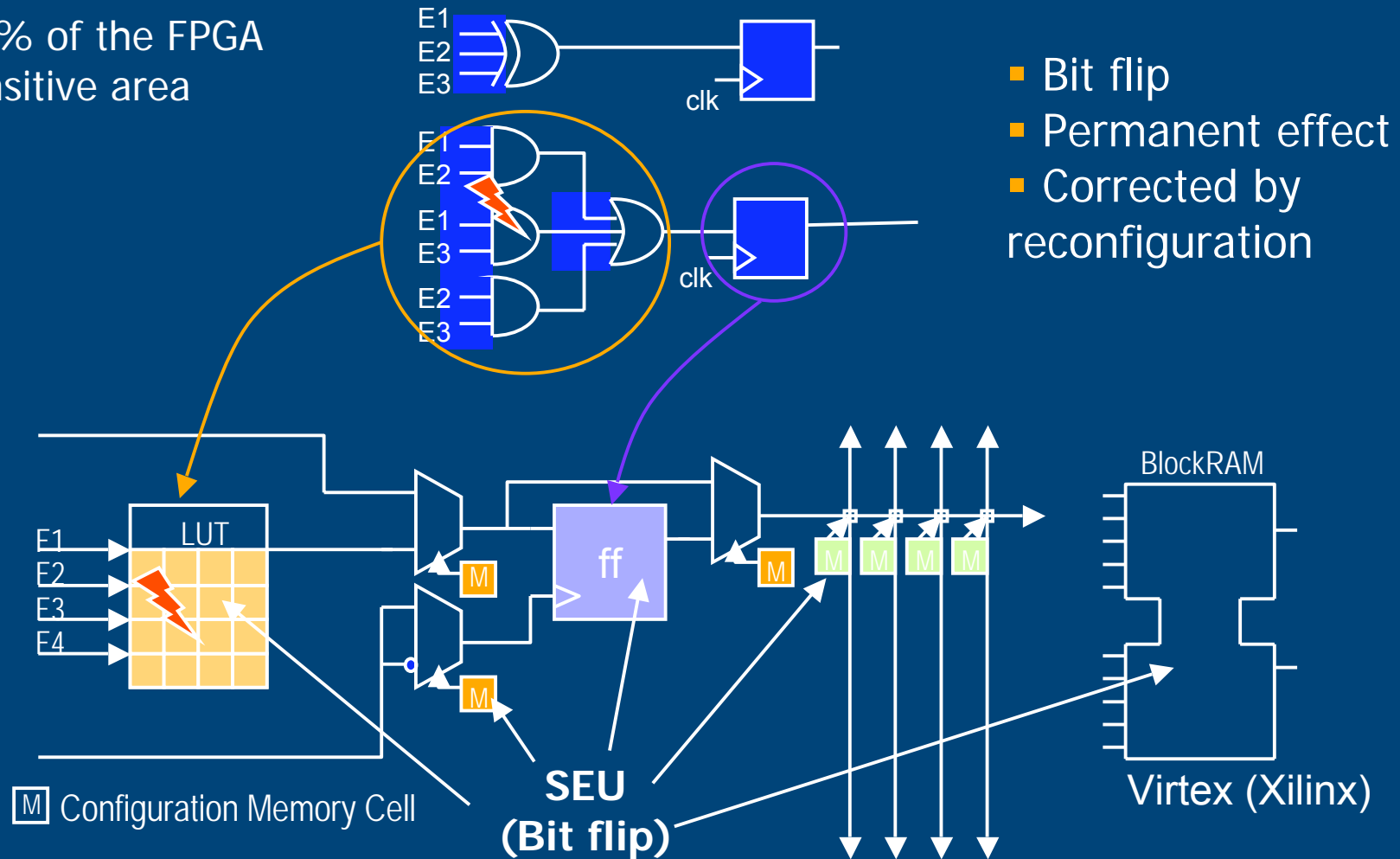

Effect of Transients in SRAM-based FPGAs

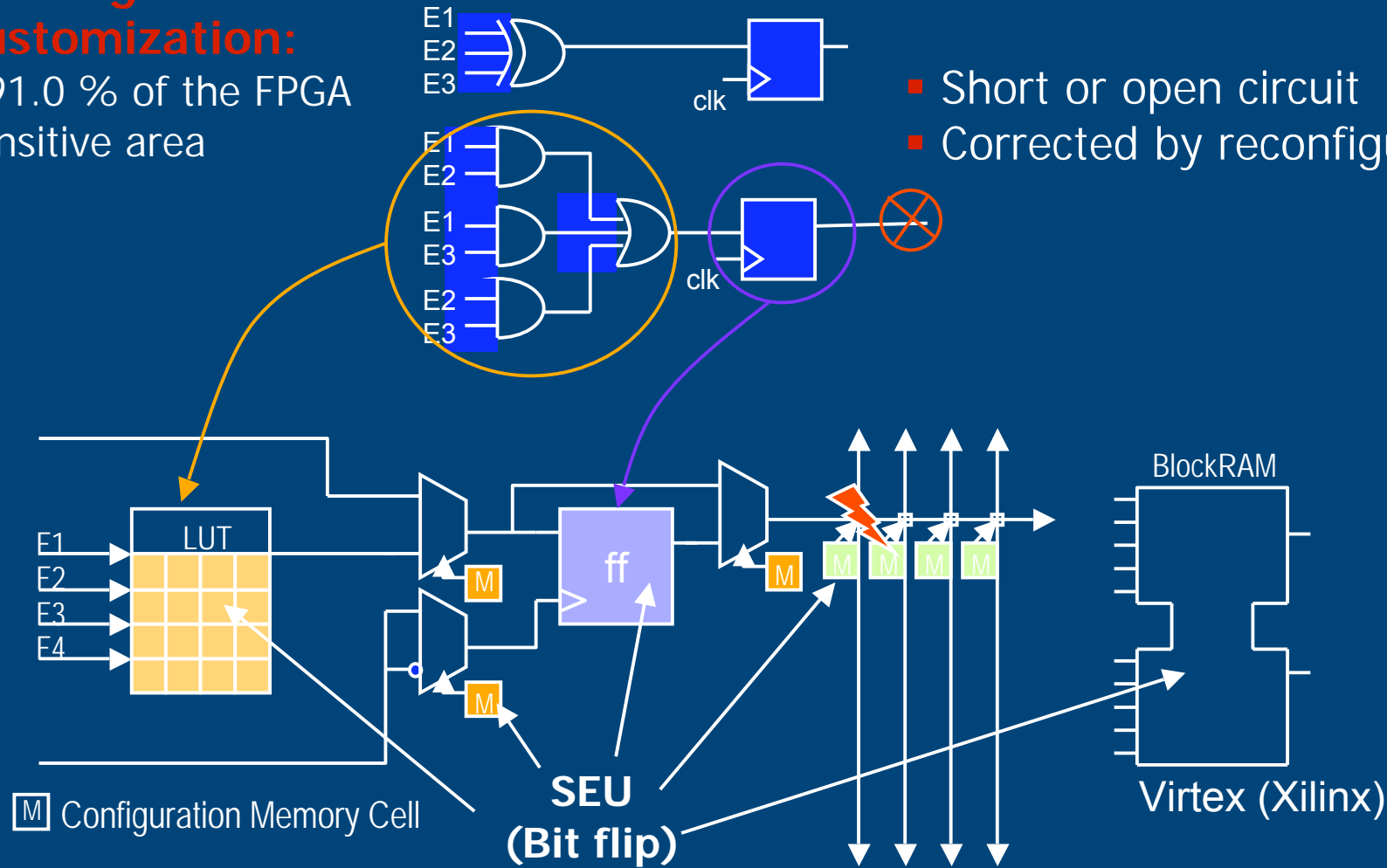Routing and CLB customization:
~91.0 % of the FPGA sensitive area



- Short or open circuit
- Corrected by reconfiguration

M Configuration Memory Cell

SEU
(Bit flip)

BlockRAM

Virtex (Xilinx)

Summary

- Fault models are analyzable approximations of defects and are essential for a test methodology.
- For digital logic single stuck-at fault model offers best advantage of tools and experience.
- Many other faults (bridging, stuck-open and multiple stuck-at) are largely covered by stuck-at fault tests.
- Stuck-short and delay faults are technology-dependent faults and require special tests.
- Memory and analog circuits need other specialized fault models and tests.
- Transient faults may have permanent effects in FPGAs