

MIC05: Teste de Circuitos Integrados

Marcelo Lubaszewski


PGMICRO - UFRGS

2007/II

Lecture 5 – Test Pattern Generation

- Automatic test pattern generation
 - Structural vs. functional test
 - Definitions
 - Types of Algorithms
 - Summary

Functional vs. Structural ATPG

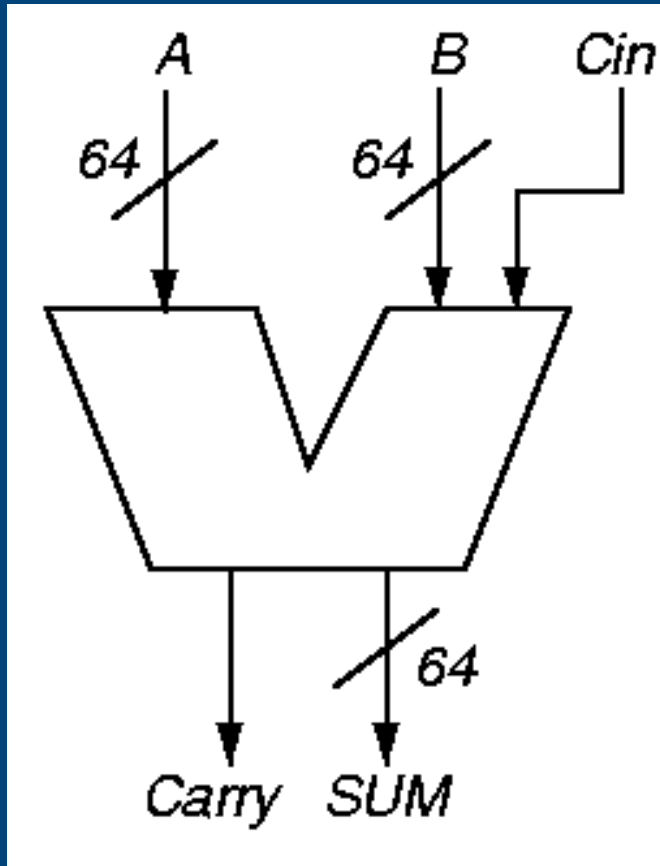

Functional ATPG

- generate complete set of tests for circuit input-output combinations
- 129 inputs, 65 outputs:



$$2^{129} =$$

680,564,733,841,876,926,926,749,
214,863,536,422,912

patterns

- Using 1 GHz ATE, would take 2.15×10^{22} years

Sum and Carry Circuits

  

Functional vs. Structural (Cont'd)

- Structural test:
 - No redundant adder hardware, 64 bit slices
 - Each with 27 faults (using fault equivalence)
 - At most $64 \times 27 = 1728$ faults (tests)
 - Takes 0.000001728 s on 1 GHz ATE
- Designer gives small set of functional tests –
augment with structural tests to boost coverage to 98+ %

Definition of Automatic Test-Pattern Generator

- Operations on digital hardware:
 - Inject fault into circuit modeled in computer
 - Use various ways to activate and propagate fault effect through hardware to circuit output
 - Output flips from expected to faulty signal
- Test generation cost
 - fault-dependent or not
- Quality of generated test
 - fault coverage (fault simulation)
- Test application cost
 - test time, memory requirements

TG Types


- Exhaustive
 - cheap generation, high FC, expensive application
- Fault-Oriented (deterministic)
 - expensive generation, possibly high FC, cheaper application
 - reduction of generation costs
- Random (pseudo-random)
 - cheap generation, low FC, + - expensive application

Exhaustive Algorithm

- For n -input circuit, generate all 2^n input patterns
- Infeasible, unless circuit is partitioned into cones of logic, with ≤ 15 inputs
 - Perform exhaustive ATPG for each cone
 - Misses faults that require specific activation patterns for multiple cones to be tested


Random-Pattern Generation

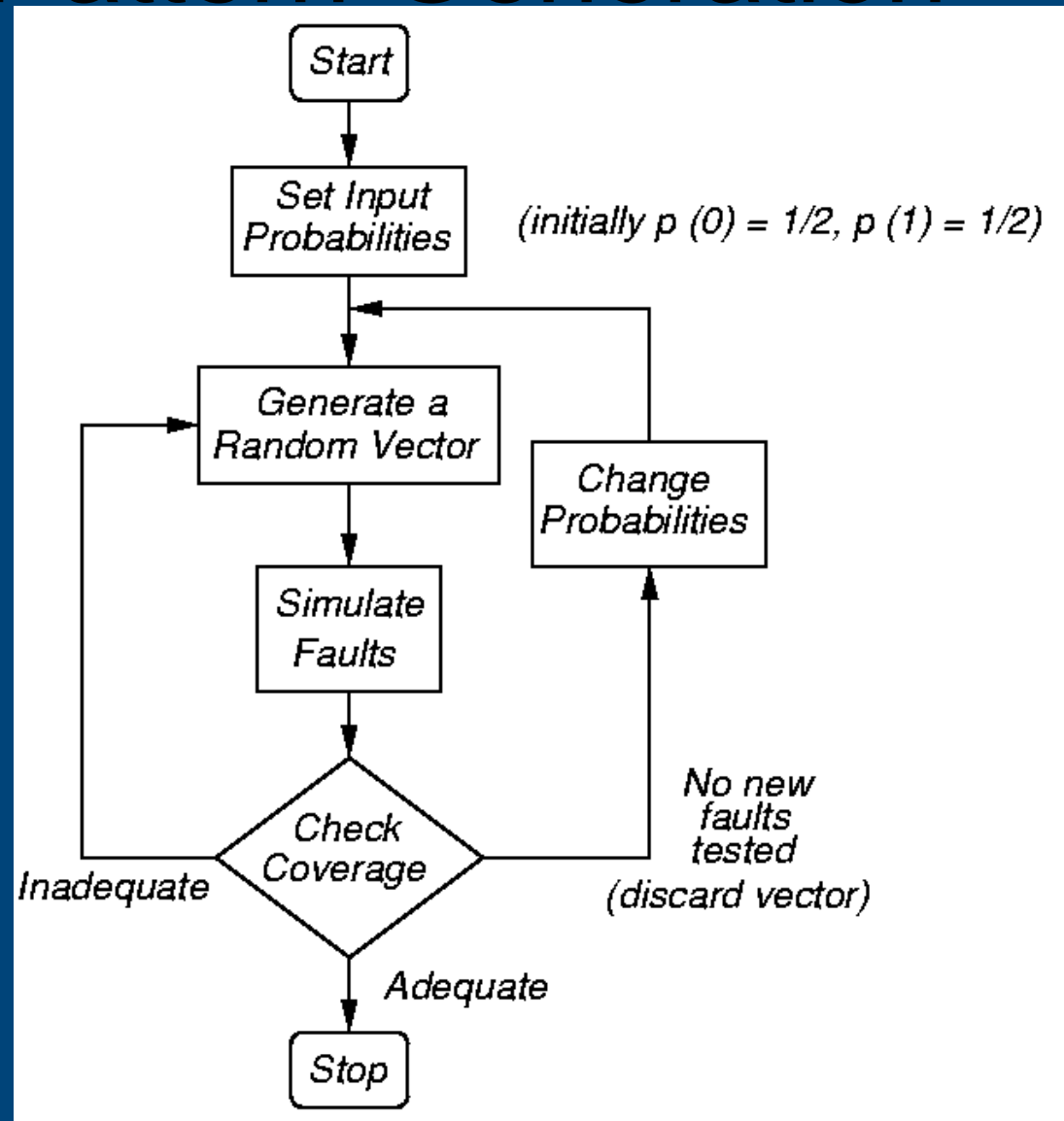- Flow chart for method
- Use to get tests for 60-80% of faults, then switch to D-algorithm or other ATPG for rest



Path Sensitization Method

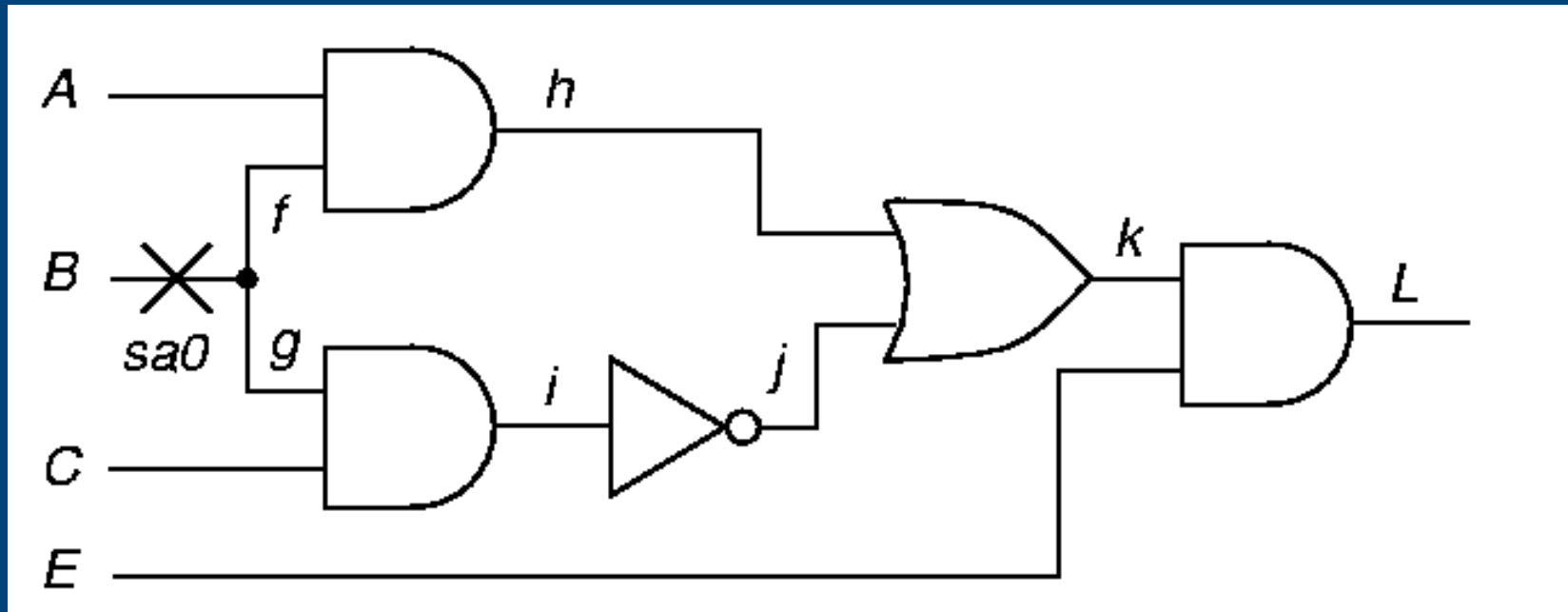- 1 Fault Sensitization (activation)
- 2 Fault Propagation
- 3 Line Justification



Path Sensitization Method


- Fault / *s-a-v*
- Activation
 - set / to \bar{v}
- Propagation
 - find a path from / to a primary output that keeps faulty value
- Justification
 - set the primary inputs to activate the fault

Composite Logic Values

- consider line value for original AND faulty circuit
- $v/v_f = \text{original/faulty}$
- Symbols D and \bar{D} (Roth, 1966)
- $D = 1/0$
- $\bar{D} = 0/1$
- $0 = 0/0$
- $1 = 1/1$


Path Sensitization Method

- Propagation

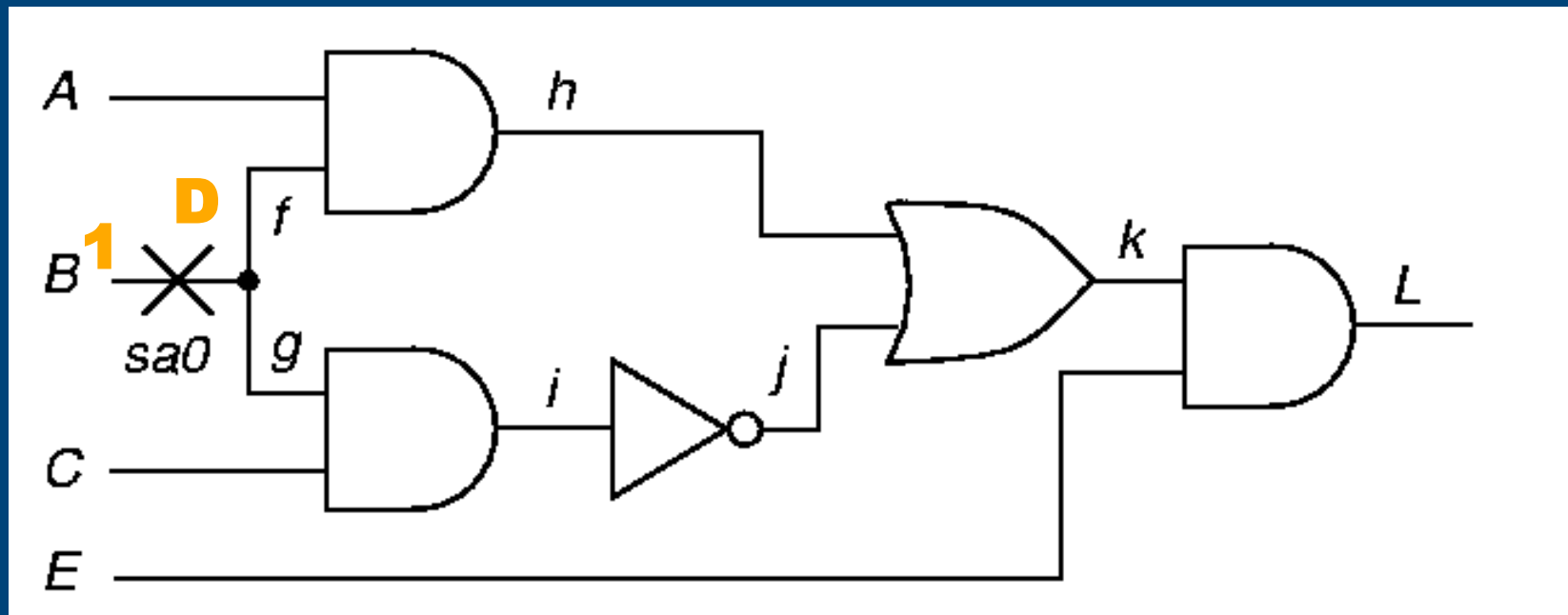


Path Sensitization Method

- Propagation: try path $f - h - k - L$

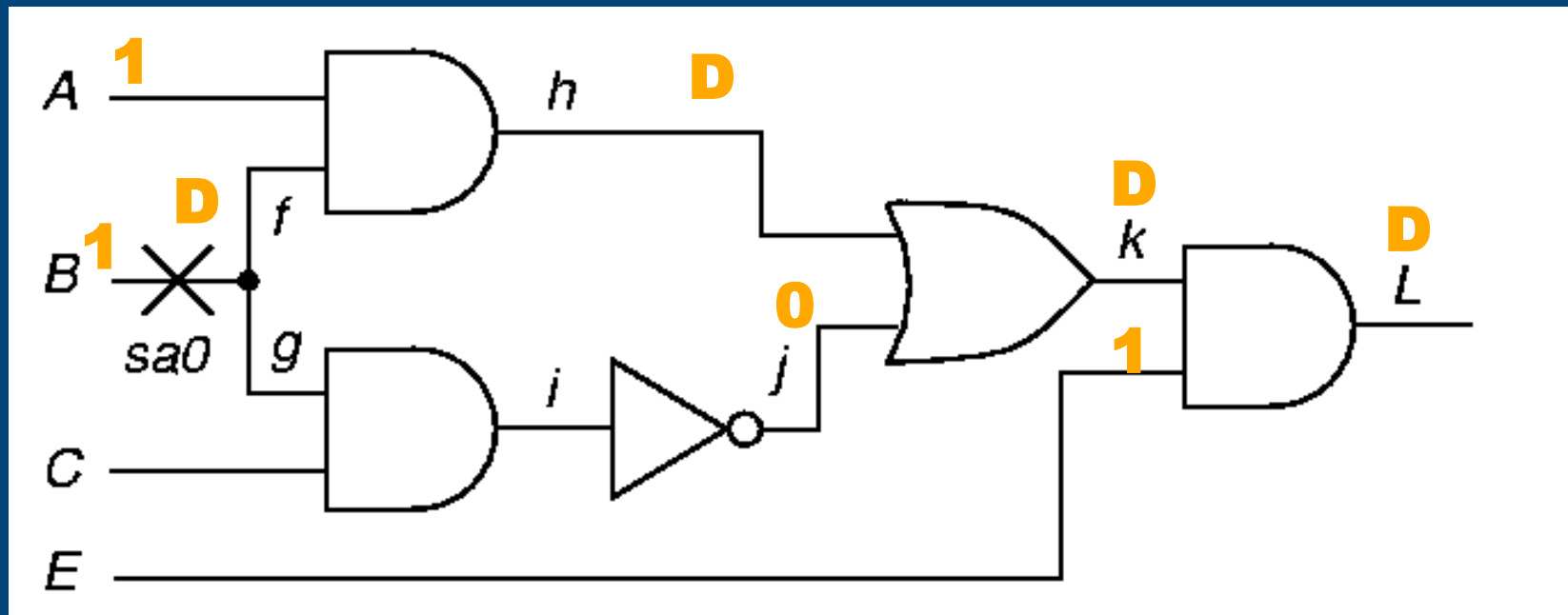


Path Sensitization Method

- Propagation: try path $f - h - k - L$

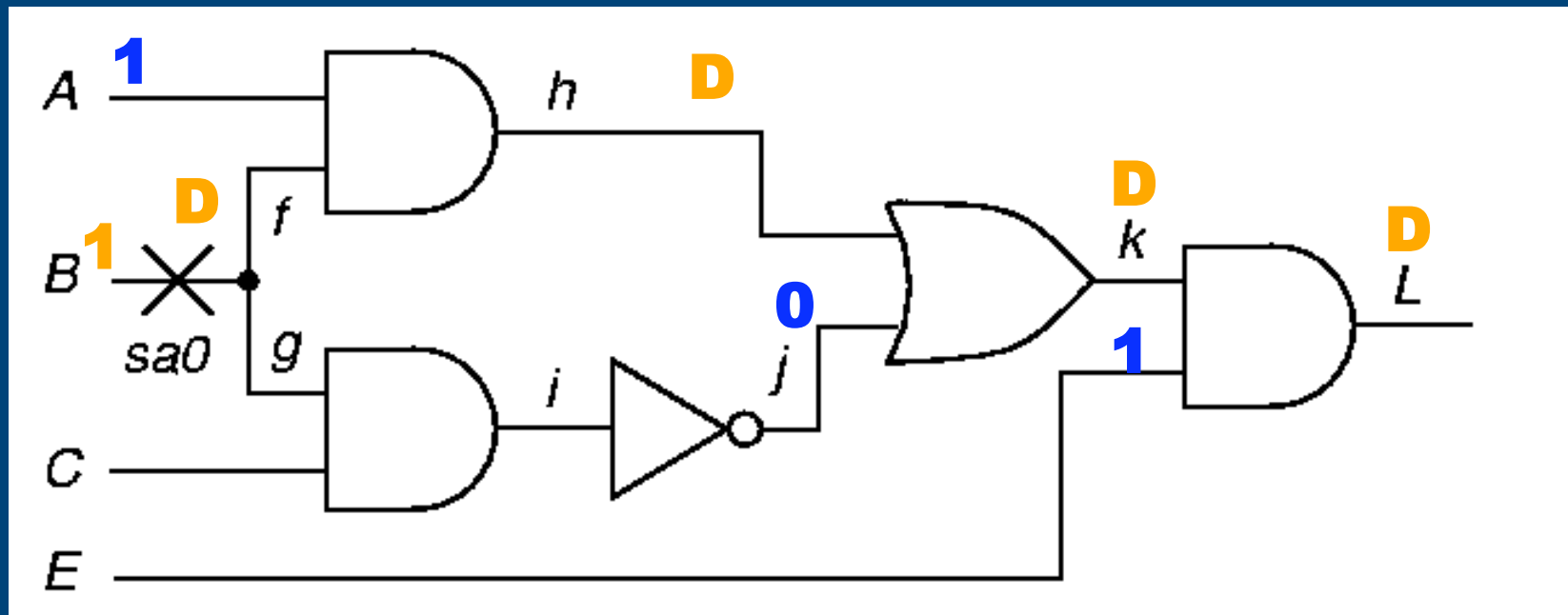


Path Sensitization Method

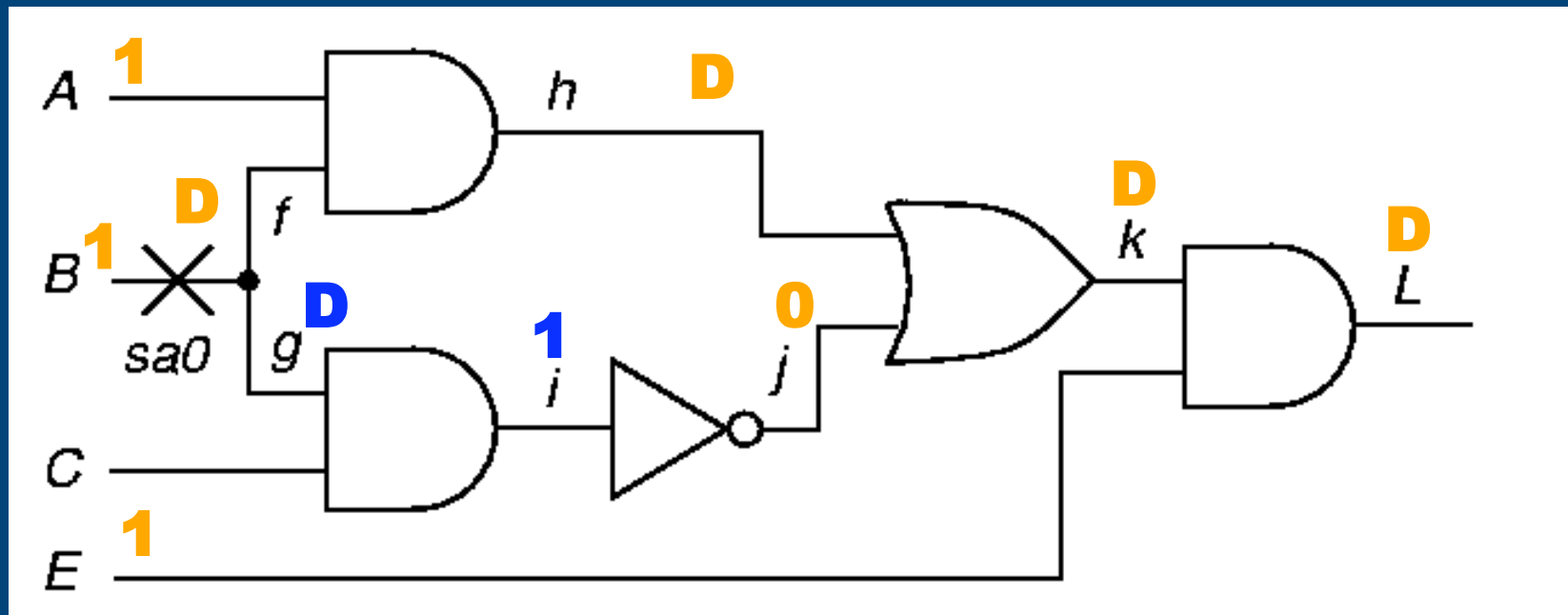- Justification: Try path $f-h-k-L$ blocked at j , since there is no way to justify the 1 on i




Path Sensitization Method

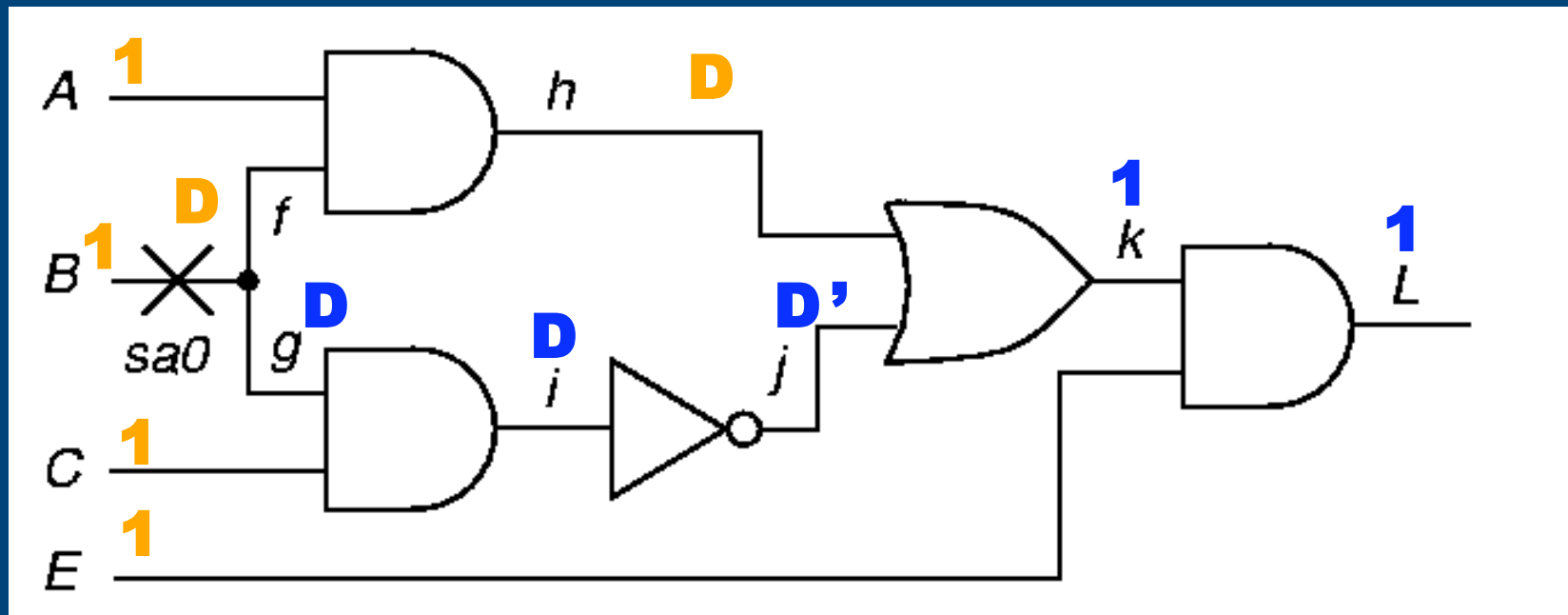- Justification: Try path $f-h-k-L$ blocked at j , since there is no way to justify the 1 on i




Path Sensitization Method

- Backtracking!

 


Path Sensitization Method

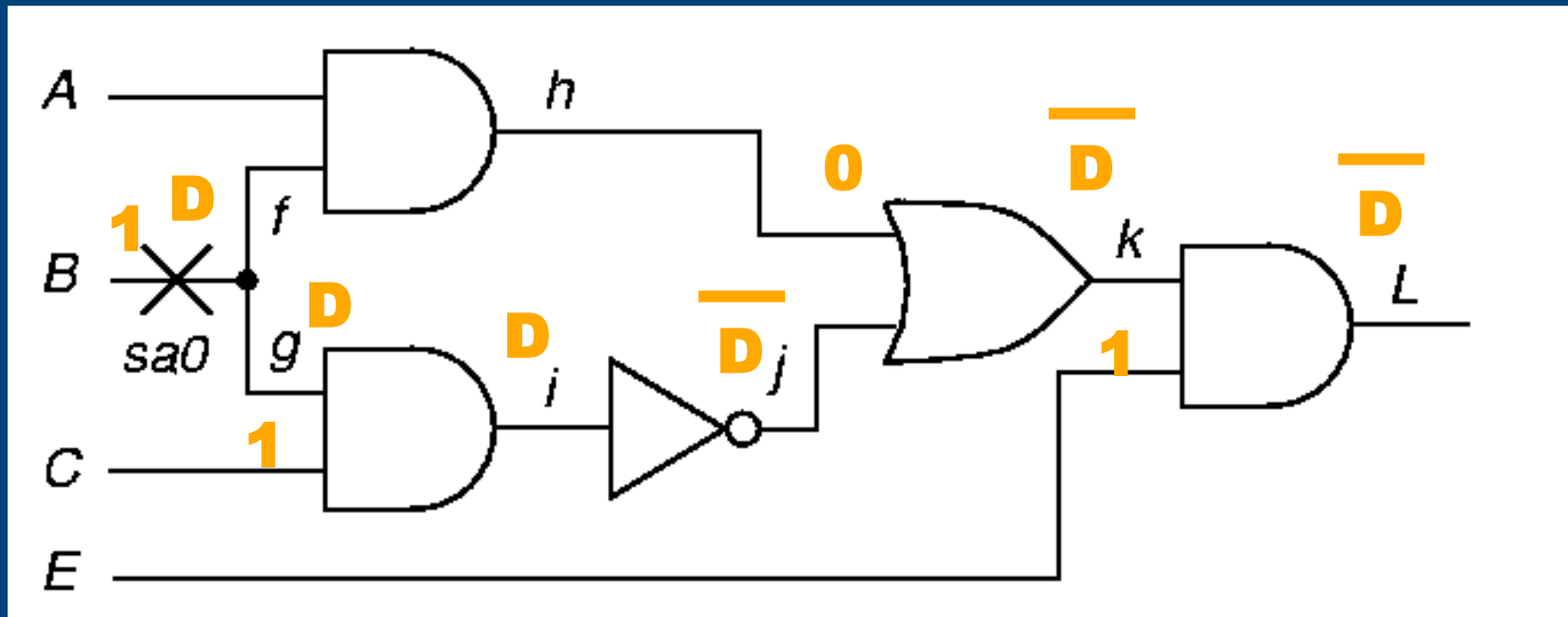- Try other propagation: path $g - i - j - k - L$




Path Sensitization Method

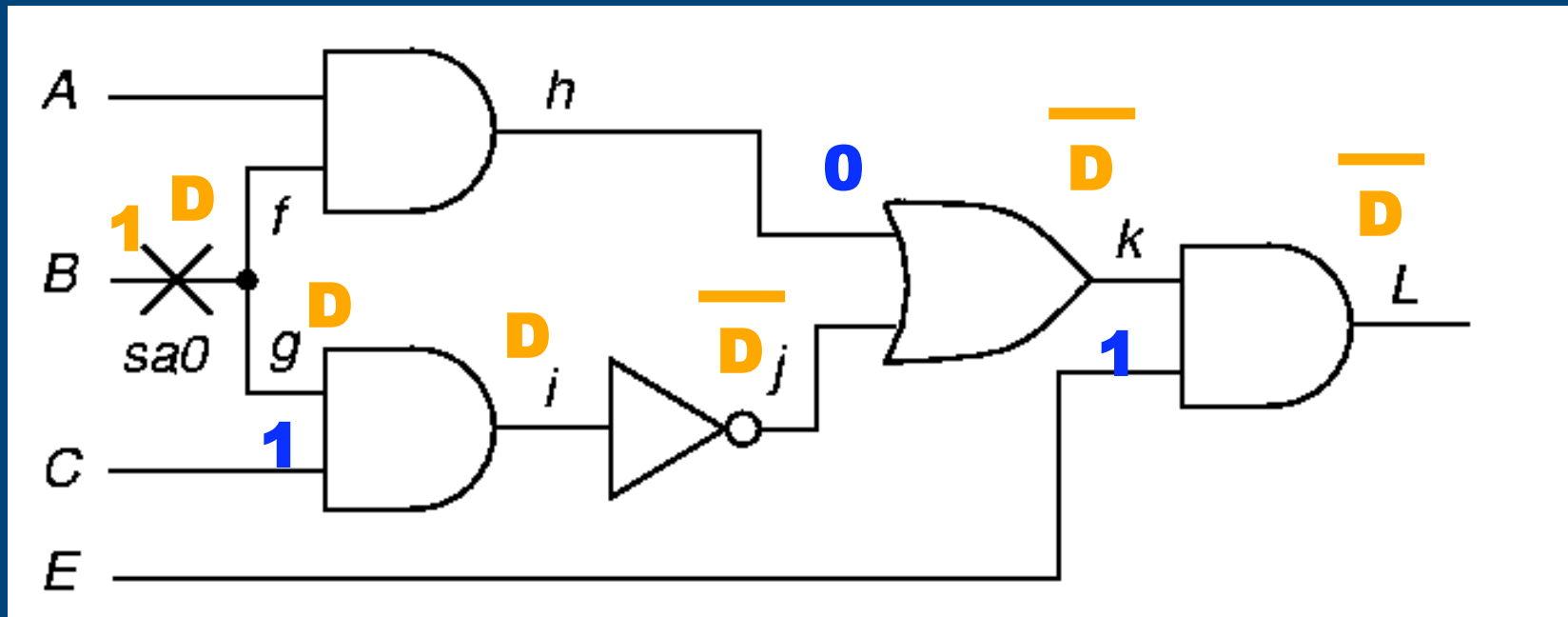- Try other propagation: path $g - i - j - k - L$



Path Sensitization Method

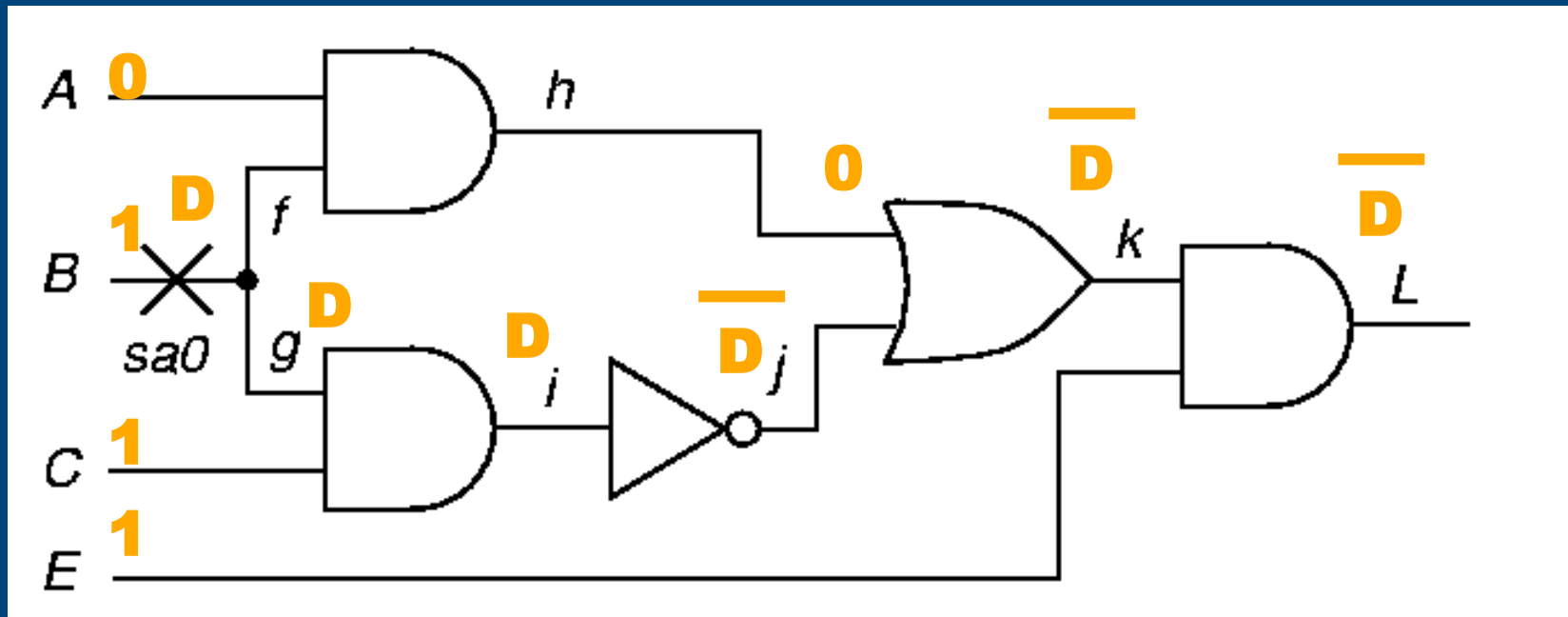- Try other propagation: path $g - i - j - k - L$



Major Combinational Automatic Test-Pattern Generation Algorithms


- D-Algorithm (Roth) -- 1966
- PODEM (Goel) -- 1981
- FAN (Fujiwara and Shimono) --1983

Sequential Circuit ATPG

Time-Frame Expansion

- Problem of sequential circuit ATPG
- Time-frame expansion

Example of Sequential Circuit

 


Sequential Circuits

- A sequential circuit has memory in addition to combinational logic.
- Test for a fault in a sequential circuit is a sequence of vectors, which
 - Initializes the circuit to a known state
 - Activates the fault, and
 - Propagates the fault effect to a primary output
- Methods of sequential circuit ATPG
 - Time-frame expansion methods
 - Simulation-based methods


Extended D-Algorithm

1. Pick up a target fault f .
2. Create a copy of a combinational logic, set it time-frame 0.
3. Generate a test for f using D-algorithm for time-frame 0.
4. When the fault effect is propagate to the DFFs, continue fault propagation in the next time-frame.
5. When there are values required in the DFFs, continue the justification in the previous time-frame.


Example for Extended D-Algorithm

 


Example: Step 1

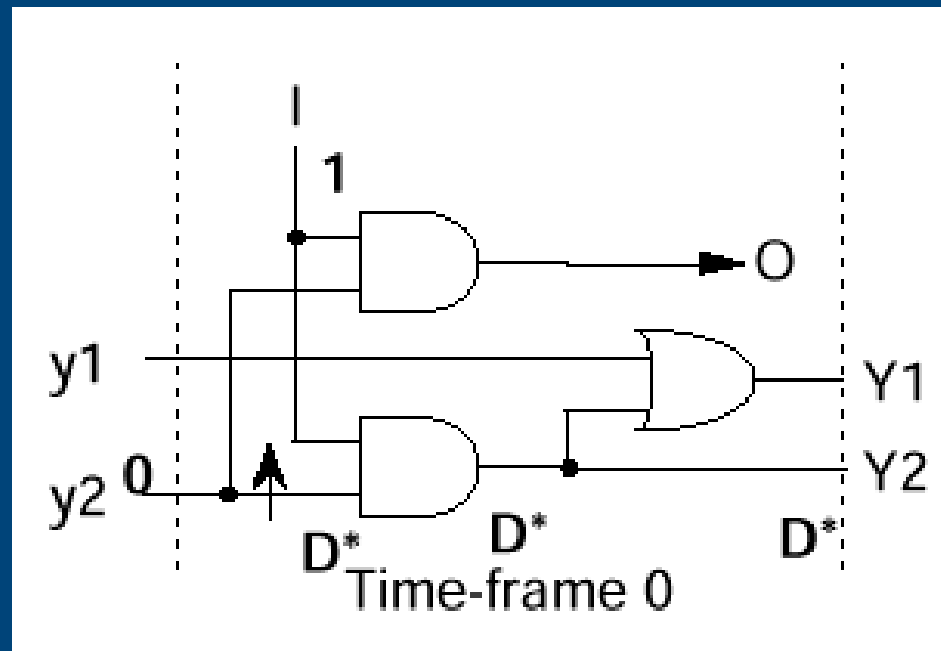

Example: Step 2

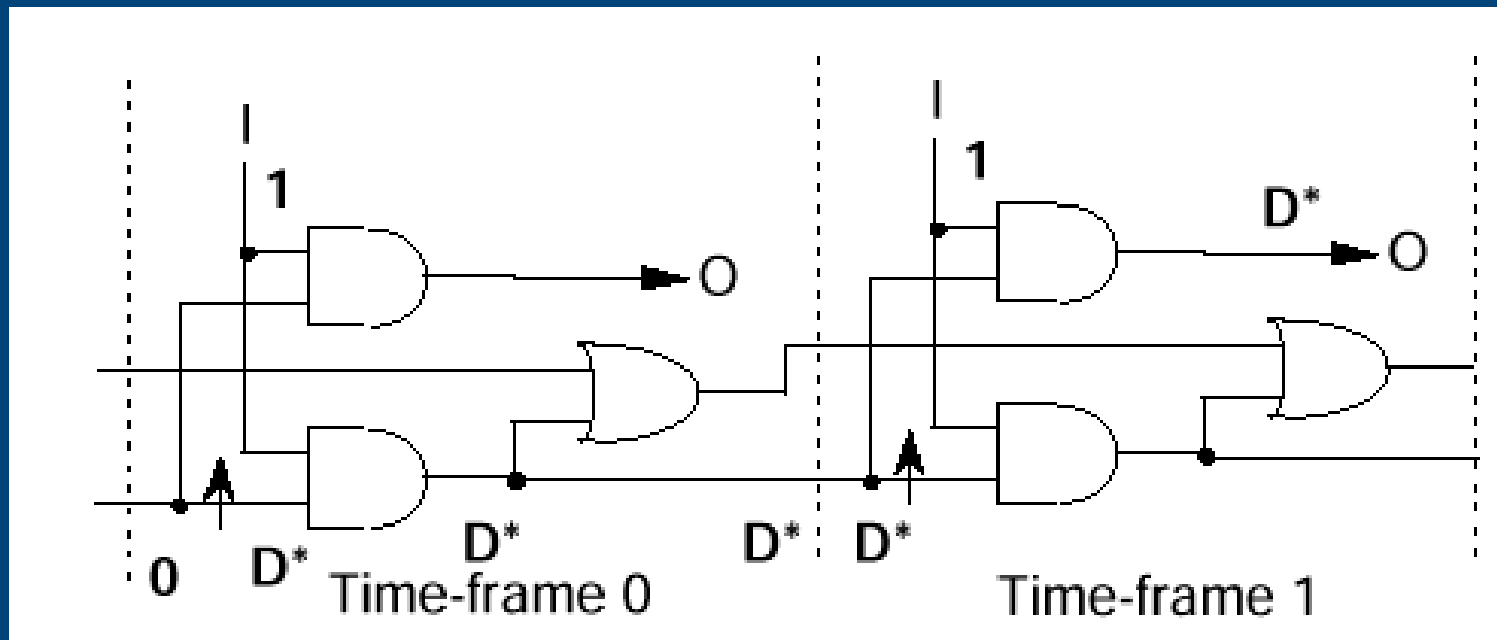

Example: Step 3

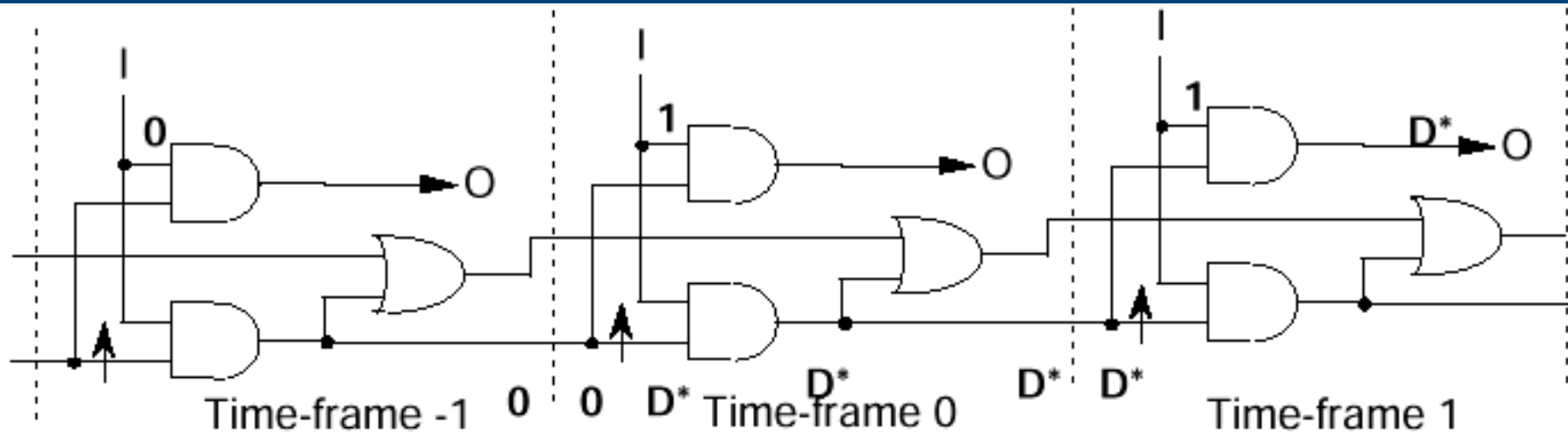

Summary

- Hierarchical ATPG -- 9 Times speedup (Min)
 - Handles adders, comparators, MUXes
- Advances over D-algorithm
- Results of 40 years research – mature – methods:
 - Path sensitization
 - Simulation-based
 - Boolean satisfiability and neural networks
 - Genetic algorithms