 


Introdução a Sistemas Digitais


- Uso de banco de registradores e Memórias

Uso de Memória em Circuitos Integrados



Leitura e Escrita em Memória

 - Na figura ao lado, o sinal de WR é sensível a zero, logo quando o sinal de WR for para zero, o conteúdo armazenado no endereço indicado no barramento Memory address será colocado no barramento de dados.
- O barramento de dados pode ser bi-direcional (data in/out) ou pode haver um barramento data_in e um barramento de dados data_out.



Descrição de Memória em VHDL

Model description

```
library IEEE;
use IEEE.std_logic_1164.all;
library BITLIB;
use BITLIB.bit_pack.all;
```

```
entity RAM6116 is
port(Cs_b, We_b: in bit;
Address: in bit_vector(7 downto 0);
IO: inout std_logic_vector(7 downto 0));
end RAM6116;
```

```
architecture simple_ram of RAM6116 is
```

```
type RAMtype is array(0 to 255) of std_logic_vector(7 downto 0);
signal RAM1: RAMtype:=(others=> (others=>'0')); -- Initialize all bits to '0'
```


Begin

```
process
begin
if Cs_b = '1' then IO <= "ZZZZZZZZ"; -- chip not selected
else
if We_b'event and We_b = '1' then -- rising-edge of We_b
RAM1(vec2int(Address'delayed)) <= IO; -- write
wait for 0 ns; -- wait for RAM update
end if;
if We_b = '1' then
IO <= RAM1(vec2int(Address)); -- read
else IO <= "ZZZZZZZZ"; -- drive high-Z
end if;
end if;
wait on We_b, Cs_b, Address;
end process;
```


```
end simple_ram;
```

Usando BRAMs como Memorias

 - Todo o FPGA customizado por células de memória SRAM possui blocos de memória embarcada (BRAM) para implementar memória na matriz.
- No FPGA Editor é possível observar a BRAM e suas conexões com os CLBs.



Usando BRAM como Memorias

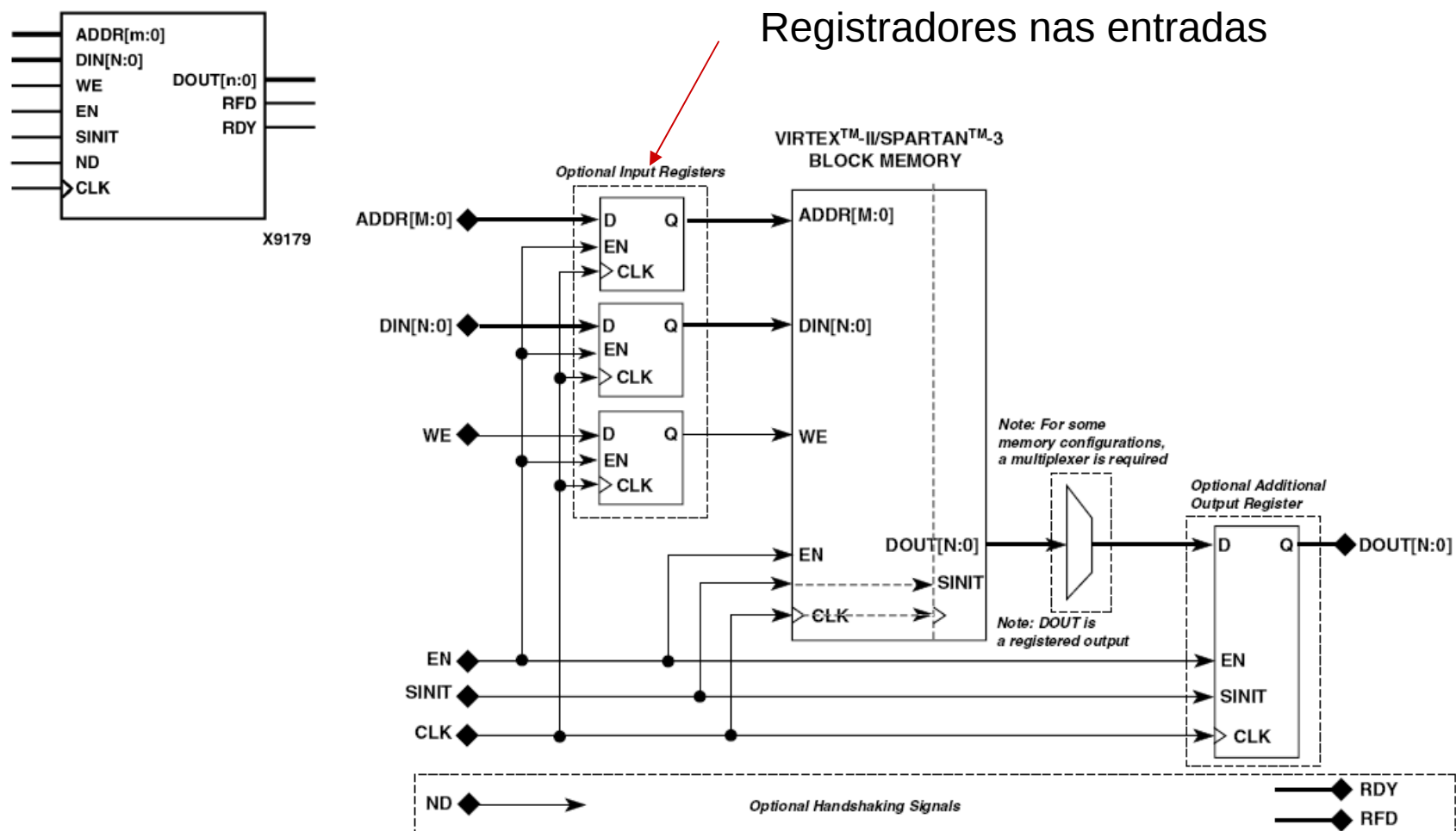

Sinais da BRAM

Clock - CLK


- Block Memory is fully synchronous with the clock input.

Enable - EN

- The enable pin affects the read, write, and SINIT functionality of the port.
- When the Block Memory has an inactive enable pin, the output pins are held in the previous state and writing to the memory is disabled.
- By default the enable pin is active high. Users, however, have the option to configure the enable pin active high or active low. Configuring the enable pin active low will not use extra resources.

Write Enable - WE

- Activating the write enable pin enables writing to the memory locations.
- When active, the contents of the DIN bus is written to memory at the address pointed to by the ADDR bus.
- The output latches are loaded or not loaded according to the write configuration (Write First, Read First, No Change).
- When WE is inactive, a read operation occurs, and the contents of the memory addressed by the ADDR bus are driven on the DOUT bus.
- In the Read Only port configuration (ROM configuration), the WE pin is not available.
- By default the write enable pin is active high. Users, however, have the option to configure the write enable pin active high or active low.
- Configuring the write enable pin active low will not use extra resources.

 

Sinais da BRAM

Synchronous Initialization - SINIT

- When enabled, the SINIT pin forces the data output latches to synchronously load the predefined SINIT value.
- For the Virtex implementation, the SINIT value is zero. Therefore, asserting the SINIT pin causes the output latches to reset.
- For the Virtex-II implementation, the SINIT value is defined by the user.
- Consequently, asserting the SINIT pin causes the output latches to contain the user-defined SINIT value.
- This operation does not affect memory locations and does not disturb write operations.
- Like the read and write operation, the SINIT function is active only when the enable pin of the port is active.
- By default, the SINIT pin is active high.
- Users, however, have the option to configure the SINIT pin active high or active low.
- Configuring the write enable pin active low will not use extra resources.

Address Bus - ADDR[m:0]

- The address bus selects the memory location for read or write access.

Data-In Bus - DIN[n:0]


- The DIN bus provides the data value to be written into the memory.
- Data input and output signals are always buses; that is, in a 1-bit width configuration, the data input signal is DIN[0] and the data output signal is DOUT[0].
- In the Read Only port configuration (ROM configuration), the DIN bus is not available.

Data-Out Bus - DOUT[n:0]

- The DOUT bus reflects the contents of memory locations referenced by the address bus during a read operation.

Funcionamento BRAM

- Read/Write Operation

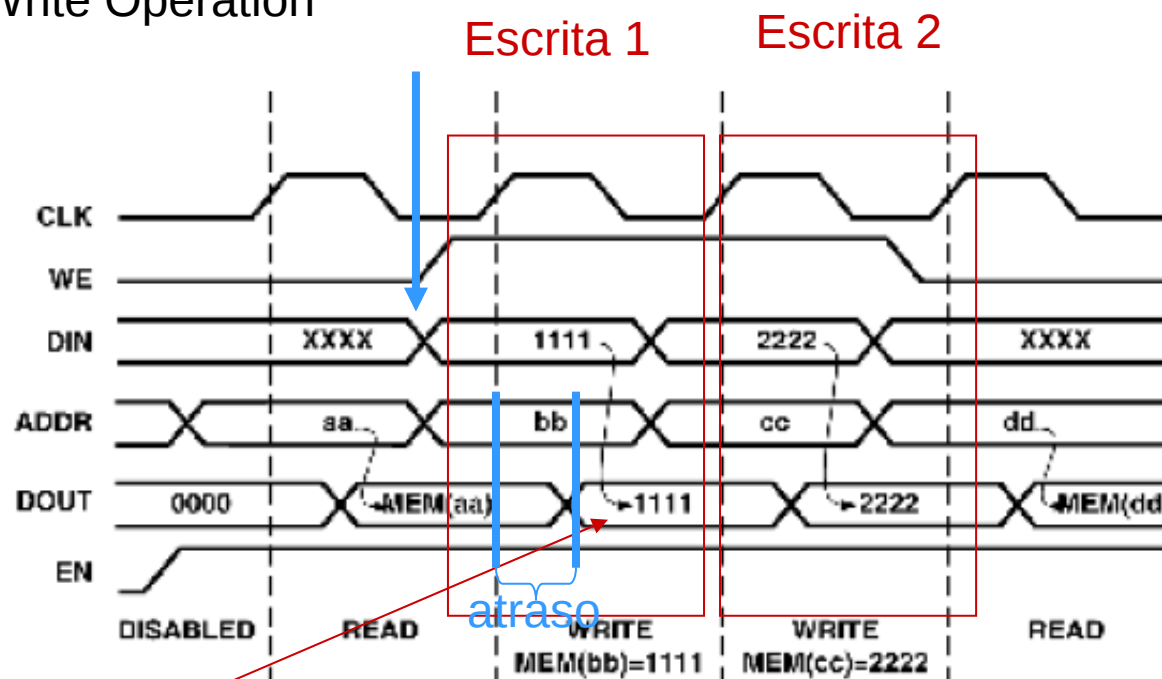


Na saída aparece o valor novo gravado

Write First Mode Waveform

Funcionamento BRAM

- Read/Write Operation

 


Na saída aparece o
valor antigo e não o
novo gravado

Read First Mode Waveform

Funcionamento BRAM

- Read/Write Operation

 


A saída não muda
desde a ultima leitura

No Change on Write Mode Waveform


Usando BRAM como memória

Uso da ferramenta CoreGenerator

 

Usando BRAM como memória

Uso da ferramenta CoreGenerator

 

Single Port Block Memory

Parameters Core Overview Contact Web Links

LogiCORE

Single Port Block Memory

Component Name: memoria

Port Configuration

☒ Read And Write ☐ Read Only

Memory Size

Width: 8 Valid Range 1..256

Depth: 256 Valid Range: 2..524288

Write Mode

☒ Read After Write ☐ Read Before Write ☐ No Read On Write

<Back Next>

Page 1 of 4

Generate Dismiss Data Sheet... Version Info...

Modos de funcionamento apresentados

Single Port Block Memory

Parameters Core Overview Contact Web Links

Single Port Block Memory

Primitive Selection

☒ Optimize For Area ☐ Select Primitive 16kx1

Design Options

Optional Pins: ☐ Enable Pin ☐ Handshaking Pins

Register Options: ☐ Register Inputs

Output Register Options

Additional Output Pipe Stages 0

☐ SINIT pin (sync. reset of output registers)

Init Value (Hex) 0


<Back Next>


Page 2 of 4

Generate Dismiss Data Sheet... Version Info...

Banco de Registradores

Aula

 

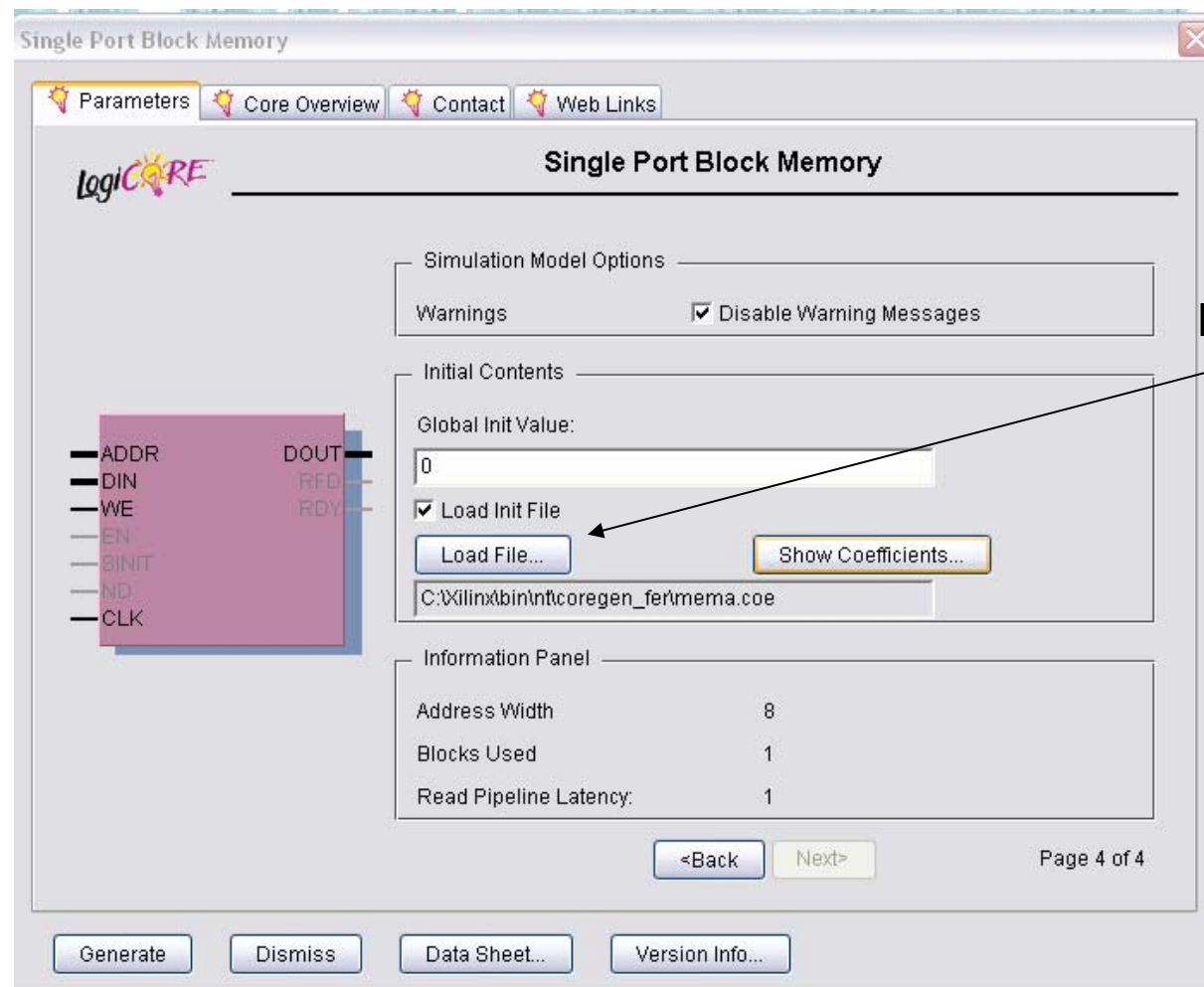

Ler arquivo .coe


Ver modelo
no prox. slide

Exemplo de arquivo .coe


Arquivo de Inicialização da memória

- MEMORY_INITIALIZATION_RADIX=10;
- MEMORY_INITIALIZATION_VECTOR=1, 2, 3, 4, 5, 6, 10, 11, 12, 16, 76,;

Importante: colocar tudo na mesma linha.

 

Uma vez lido .coe

 

Memory Values


Invalid initialization values are shown in red

Address (HEX)	Value (DECIMAL)
0	1
1	2
2	3
3	4
4	5
5	6
6	10
7	11
8	12
9	16
A	76
B	89
C	99
D	101
E	102
F	45
10	67
11	220
12	30
13	45
14	33
15	22
16	56
17	14
18	1
19	2
1A	3
1B	4
1C	5
1D	6
1E	10
1F	11
20	12
21	16
22	76
23	89
24	99
25	101
26	102
27	45
...	...

Descrição em VHDL de Banco de Reg.

- Banco de registradores é um arranjo de registradores que podem ser endereçados de maneira mais direta e rápida, como por exemplo em banco de registradores em um microprocessador.
- Em microprocessadores, um banco de registrador é composto normalmente por células de memória SRAM, barramento de dados de entrada, saída e endereço e mecanismos parecidos com memória para leitura e escrita.
- Em FPGAs, não usamos barramento, logo o arranjo de multiplexadores é organizado de tal forma a usar codificadores e decodificadores no endereço e saída a fim de selecionar o registrador. O barramento dos dados de entrada (`data_in`) é o mesmo para todos os registradores. De acordo com o sinal de enable (`Enx`) apenas um registrador por vez armazena o valor do `data_in`.

Banco de Registradores

 

Banco de Registradores em VHDL

Exemplo para arranjo de 4 registradores de 8bits cada

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity banco_registradores is
  Port ( data_in : in  STD_LOGIC_VECTOR (7 downto 0);
        clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        wr : in STD_LOGIC;
        address : in  STD_LOGIC_VECTOR (1 downto 0);
        data_out : out STD_LOGIC_VECTOR (7 downto 0));
end banco_registradores;
```

```
architecture Behavioral of banco_registradores is
```

```
  signal en0, en1, en2, en3 : std_logic;
  signal reg0, reg1, reg2, reg3 : std_logic_vector(7 downto 0);
begin
```

```
  --- registradores
  process(reset, clk)
  begin
    if reset='1' then
      reg0 <= "00000000";
    elsif (clk'event and clk='1') then
      if en0='1' then
        reg0 <= data_in;
      else
        reg0 <= reg0;
      end if;
    end if;
  end process;
```

```
  process(reset, clk)
  begin
    if reset='1' then
      reg1 <= "00000000";
    elsif (clk'event and clk='1') then
      if en1='1' then
        reg1 <= data_in;
      else
        reg1 <= reg1;
      end if;
    end if;
  end process;
```

```
  process(reset, clk)
  begin
    if reset='1' then
      reg2 <= "00000000";
    elsif (clk'event and clk='1') then
      if en2='1' then
        reg2 <= data_in;
      else
        reg2 <= reg2;
      end if;
    end if;
  end process;
```


```
  process(reset, clk)
  begin
    if reset='1' then
      reg3 <= "00000000";
    elsif (clk'event and clk='1') then
      if en3='1' then
        reg3 <= data_in;
      else
        reg3 <= reg3;
      end if;
    end if;
  end process;
```

```
  ---- decodificador de enderecos e do data_out
  process(address, wr)
  begin
    CASE address IS
      WHEN "00" => data_out <= reg0;
        en0 <= WR; en1 <='0'; en2 <= '0'; en3 <='0';
      WHEN "01" => data_out <= reg1;
        en0 <= '0'; en1 <=WR; en2 <= '0'; en3 <='0';
      WHEN "10" => data_out <= reg2;
        en0 <= '0'; en1 <='0'; en2 <= WR; en3 <='0';
      WHEN others => data_out <= reg3;
        en0 <= '0'; en1 <='0'; en2 <= '0'; en3 <=WR;
    END CASE;
  end process;
```

```
end Behavioral;
```


Sintese no ISE

Aula

 

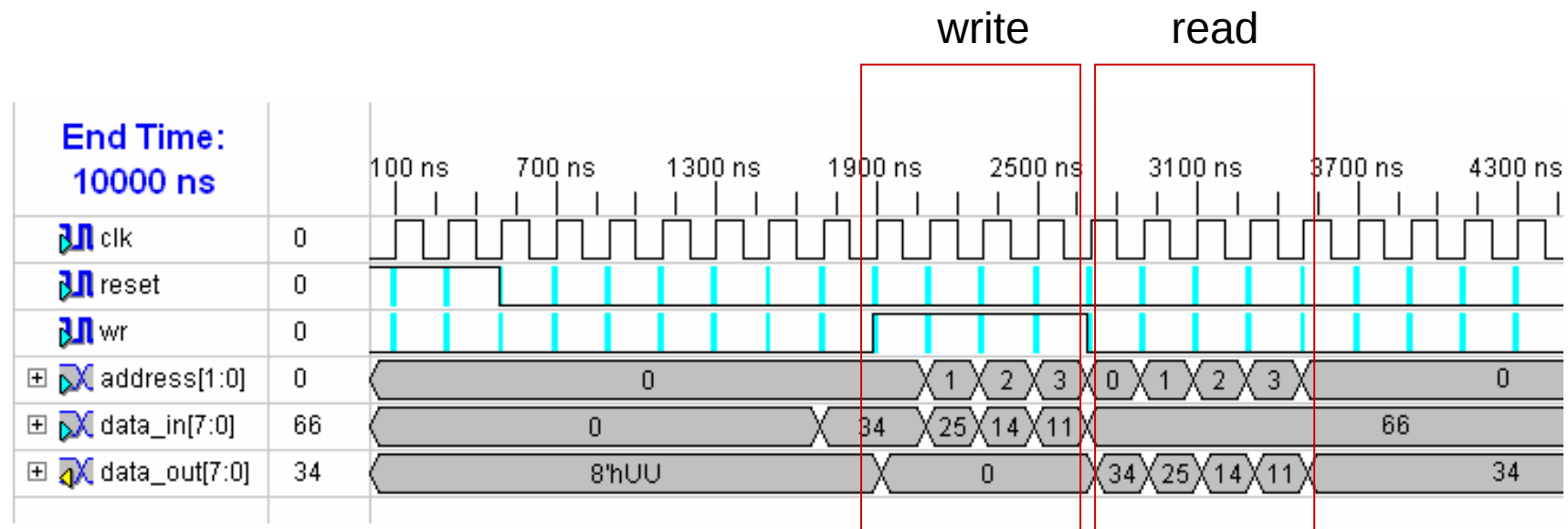
Exercícios em VHDL

- Simular o Banco de Registradores
- Gravar 4 valores diferentes em cada um dos registradores e ler os valores depois. Veja a simulação a seguir.



 
Exercícios em VHLD

- Simular com atraso o Banco de Registradores
- Gravar 4 valores diferentes em cada um dos registradores e ler os valores depois. Veja a simulação a seguir.



Atraso na leitura do dado que esta sendo gravado

 Olhe que na leitura não ha dependencia do clk.



Atraso na leitura (mudou o endereco, mudou o dado lido)


Exercicio em VHDL

Sistema Digital para inicializar memoria

- Instanciar uma BRAM de 8bits de dados e 256 posições de endereço. Use o Coregenerator.
- Desenvolver um programa que muda o conteudo de todos dados de 8bits para “10010001”.

Assim iremos exercitar a escrita.

 Simule no ISE e verifique o funcionamento.



Exemplo

```
entity memoria_teste is
  Port ( clk : in  STD_LOGIC;
        reset : in  STD_LOGIC;

        pronto : out STD_LOGIC;

        dado : out  STD_LOGIC_VECTOR (7 downto 0));
end memoria_teste;

architecture Behavioral of memoria_teste is

  component memoria IS
    port (
      addr: IN std_logic_VECTOR(7 downto 0);
      clk: IN std_logic;
      din: IN std_logic_VECTOR(7 downto 0);
      dout: OUT std_logic_VECTOR(7 downto 0);
      we: IN std_logic);
  END component;

  signal cont, dadomem_in: STD_LOGIC_VECTOR (7 downto 0);
  signal leitura, escrita, leitura2, WR: std_logic;

begin

  MEM_INST: memoria
    port map( addr => cont,


              clk => clk,
              din => dadomem_in,
              dout => dado,
              we => WR);

  process (clk, reset)
  begin
    if (reset = '1') then
      cont <= "00000000";
      leitura<='0';
      escrita<='0';
      leitura2<='0';
      pronto <='0';
    elsif (clk'event and clk='1') then
      if (leitura = '0') then
        WR<='0';
        if (cont < "11111111") then
          cont <= cont +1;
        else leitura <= '1';
        end if;
      elsif (escrita = '0') then
        dadomem_in <= "10010001";
        cont <= "00000000";
        WR<='1';
        if(cont < "11111111") then
          cont <= cont +1;
        else
          escrita <= '1';
          end if;
        else WR<= '0';
          cont <= "00000000";
        end if;
      end if;
    end process;

  end Behavioral;
```

Exercicio 2: Leitura e Escrita em Memória

- Instanciar duas BRAM, uma de 8bits de dados e 256 posições de endereço e a outra de 16 bits e 128 posições de endereço. Inicializar a BRAMs de 256 posições com valores quaisquer (diferentes de zero). Use o Coregenerator e o arquivo .txt para isso.
- Desenvolver um sistema digital que lê os dados de dois endereços consecutivos e grava o resultado na outra memória. Assim por diante iniciando do endereço 0 ate 255.

 **Cuidado:**

O circuito deve ter pelo menos um registrador aux. para armazenar um dos dados da memória a fim de fazer a soma