


# Lecture 3 - Fault Simulation and Fault Injection

- Fault simulation
- Fault simulation algorithms
  - Serial
  - Parallel
  - Deductive
  - Random Fault Sampling
- Fault Injection
  - ASIC
  - FPGAs

# Problem and Motivation

- Fault simulation Problem: Given
  - A circuit
  - A sequence of test vectors
  - A fault model
  - Determine
    - Fault coverage - fraction (or percentage) of modeled faults detected by test vectors
    - Set of undetected faults
- Motivation
  - Determine test quality and in turn product quality
  - Find undetected fault targets to improve tests
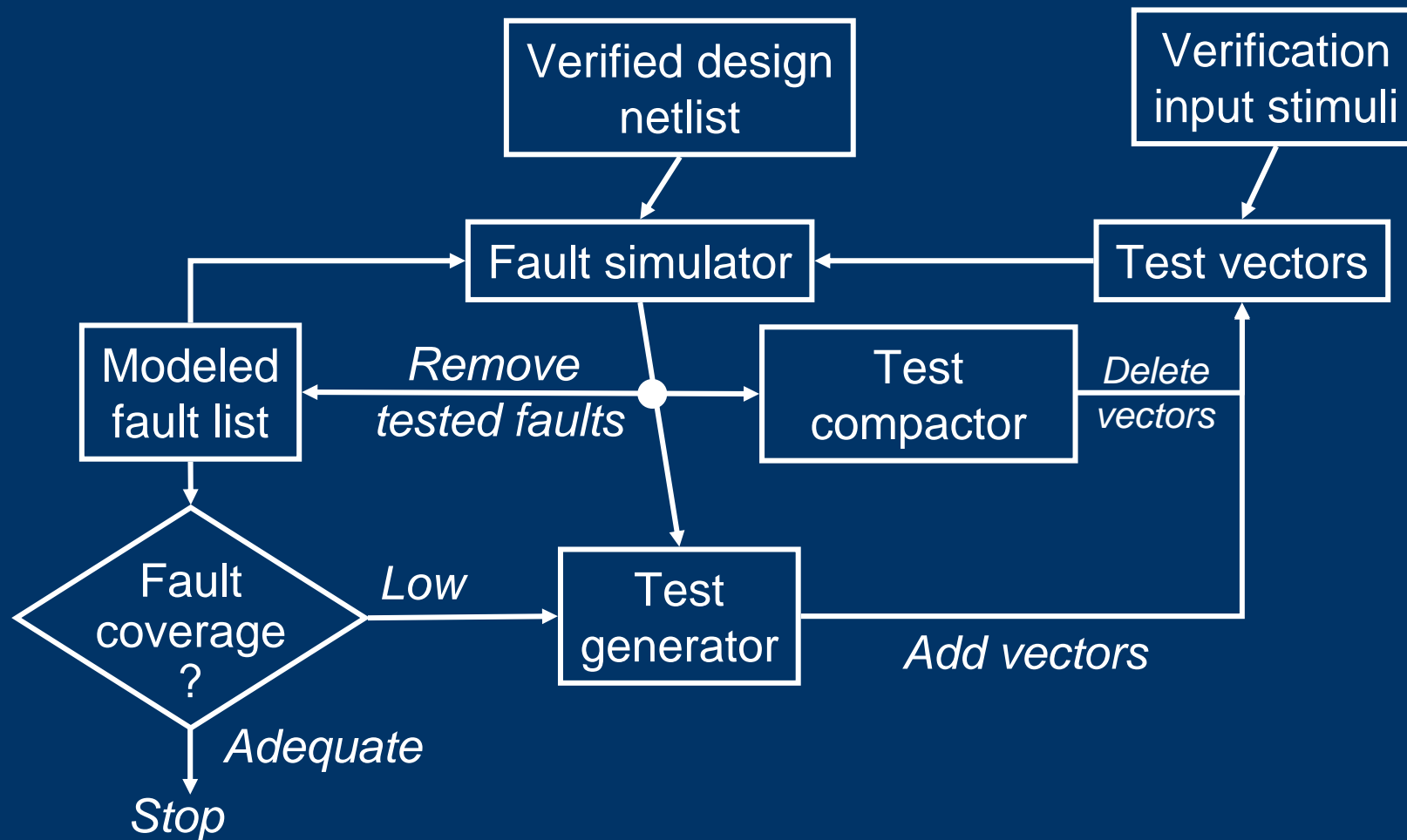
# Fault simulator in a VLSI Design Process



# Fault Simulation Scenario

- Mostly single stuck-at faults
- Sometimes stuck-open, transition, and path-delay faults; analog circuit fault simulators are not yet in common use
- Equivalence fault collapsing of single stuck-at faults
- Fault-dropping -- a fault once detected is dropped from consideration as more vectors are simulated; fault-dropping may be suppressed for diagnosis
- Fault sampling -- a random sample of faults is simulated when the circuit is large

# Fault Simulation Algorithms


- Serial
- Parallel
- Deductive
- Random Fault Sampling

# Serial Algorithm

- Algorithm: Simulate fault-free circuit and save responses. Repeat following steps for each fault in the fault list:
  - Modify netlist by injecting one fault
  - Simulate modified netlist, vector by vector, comparing responses with saved responses
  - If response differs, report fault detection and suspend simulation of remaining vectors
- Advantages:
  - Easy to implement; needs only a simulator, less memory
  - Most faults, including analog faults, can be simulated
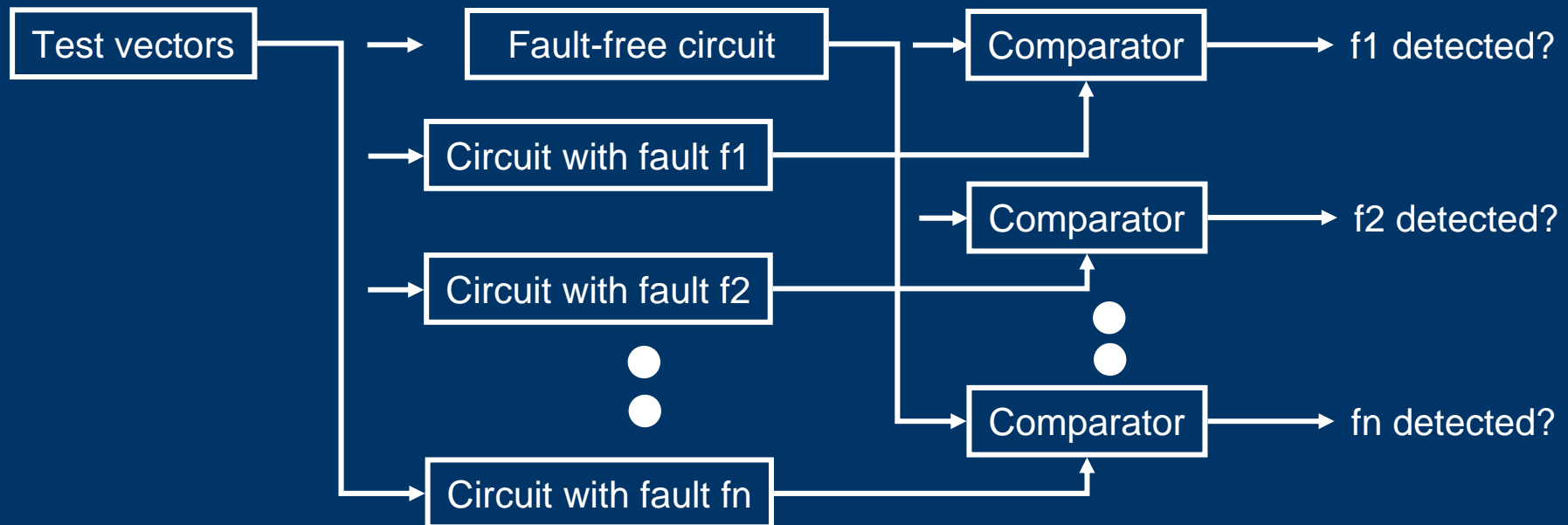
# Serial Algorithm (Cont.)


- Disadvantage: Much repeated computation; CPU time prohibitive for VLSI circuits
- Alternative: Simulate many faults together



# Parallel Fault Simulation

- Exploits inherent bit-parallelism of logic operations on computer words
- Storage: one word per line for two-state simulation
- Multi-pass simulation: Each pass simulates  $w-1$  new faults, where  $w$  is the machine word length
- Speed up over serial method  $\sim w-1$

# Parallel Fault Sim. Example

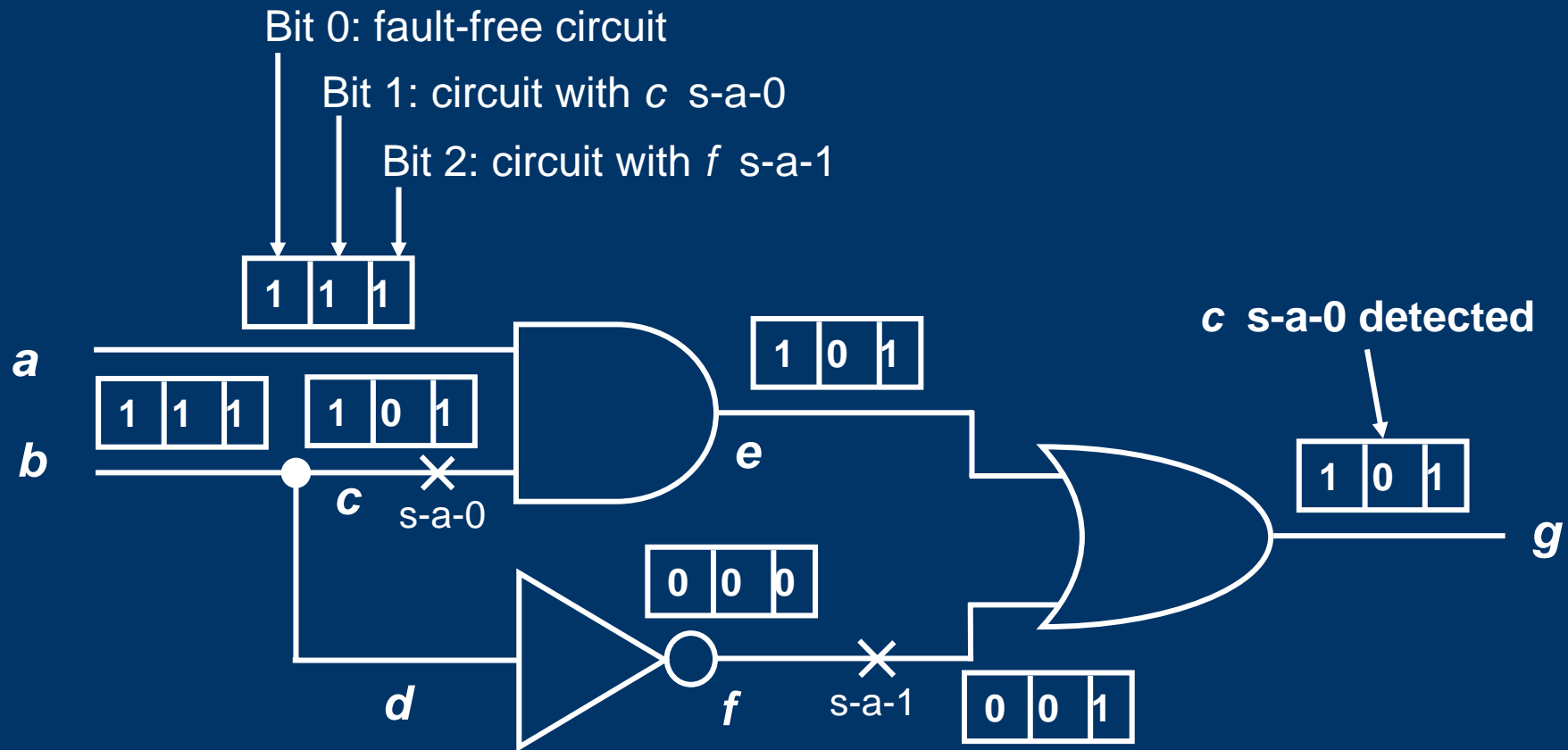


# Deductive Fault Simulation

- One-pass simulation
- Each line  $k$  contains a list  $L_k$  of faults detectable on  $k$
- Following simulation of each vector, fault lists of all gate output lines are updated using set-theoretic rules, signal values, and gate input fault lists
- PO fault lists provide detection data
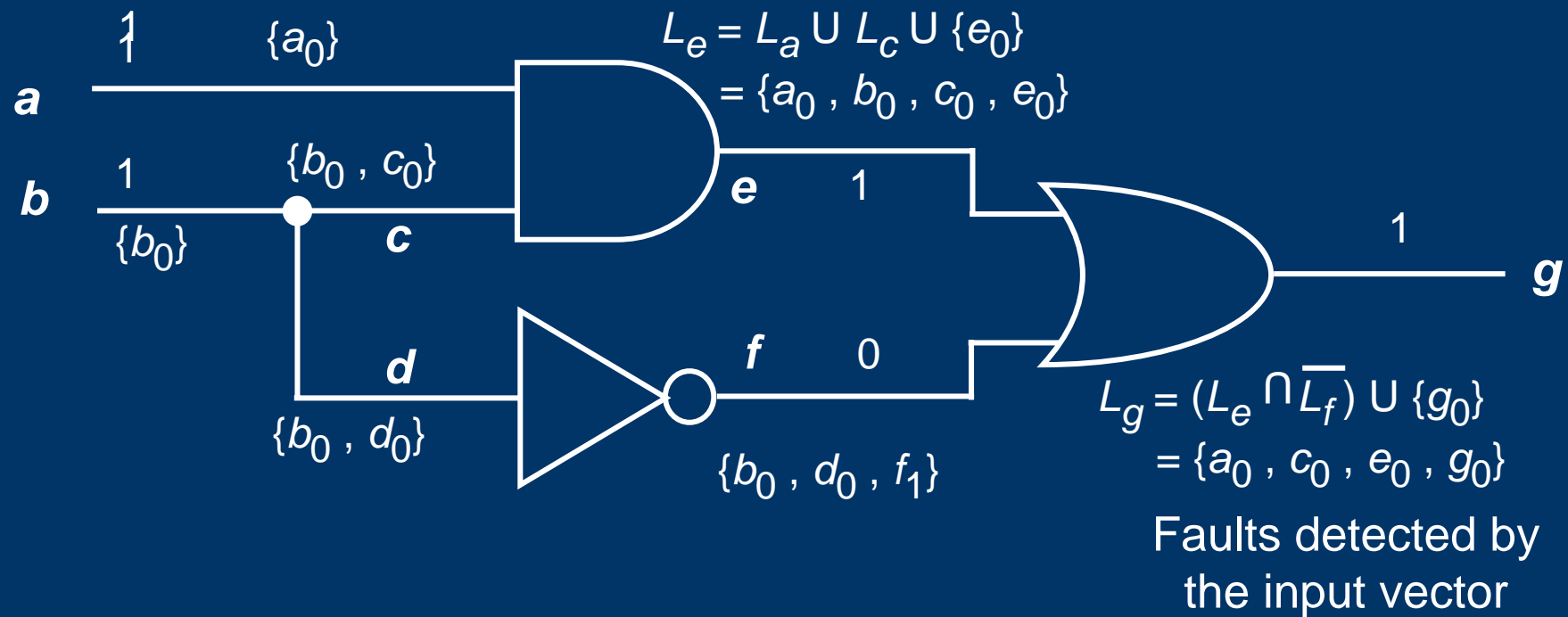
# Deductive Fault Simulation Example

Notation:  $L_k$  is fault list for line  $k$   
 $k_n$  is s-a-n fault on line  $k$



# Fault Sampling


- A randomly selected subset (sample) of faults is simulated.
- Measured coverage in the sample is used to estimate fault coverage in the entire circuit.
- Advantage: Saving in computing resources (CPU time and memory.)
- Disadvantage: Limited data on undetected faults.

# Motivation for Sampling

- Complexity of fault simulation depends on:
  - Number of gates
  - Number of faults
  - Number of vectors
- Complexity of fault simulation with fault sampling depends on:
  - Number of gates
  - Number of vectors
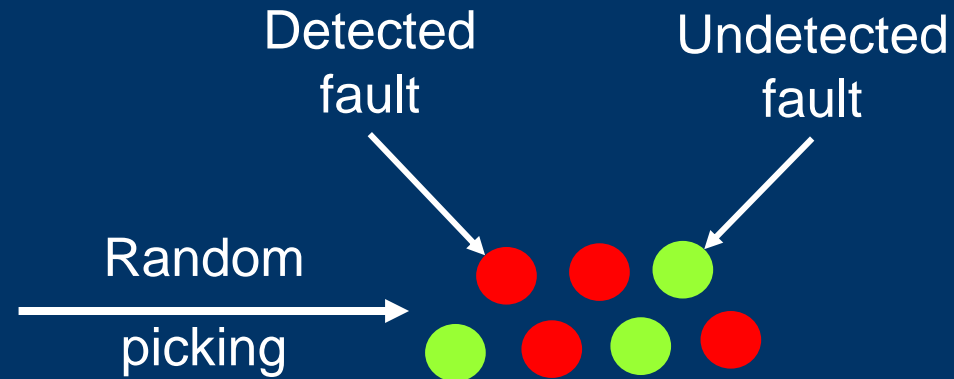
# Random Sampling Model

All faults with  
a fixed but  
unknown  
coverage



$N_p$  = total number of faults  
(population size)

$C$  = fault coverage (unknown)

$N_s$  = sample size

$$N_s \ll N_p$$

$c$  = sample coverage  
(a random variable)

# Example

A circuit with 39,096 faults has an actual fault coverage of 87.1%.

The measured coverage in a random sample of 1,000 faults is 88.7%.

CPU time for sample simulation was about 10% of that for all faults.

# Fault Injection

- Problem and Motivation
- ASIC
  - performed by simulation or
  - emulation to speed up the process
- FPGAs
  - directly into the bitstream

# Problem and Motivation


- Fault injection Problem: Given
  - A circuit
  - An application
  - A fault model
  - Determine
    - Behavior of faulty circuit
- Motivation
  - Determine product safety
  - Find unsafe states to improve product safety
  - Redesign product for fault tolerance

# Fault Injection



General: ASIC performed by simulation or emulation to speed up the process

# Fault Injection Control Block

- When should a fault be inserted?

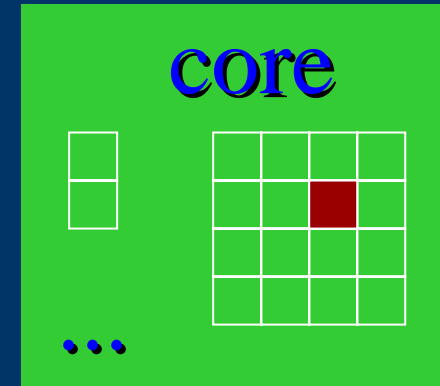


- Where should a fault be inserted?

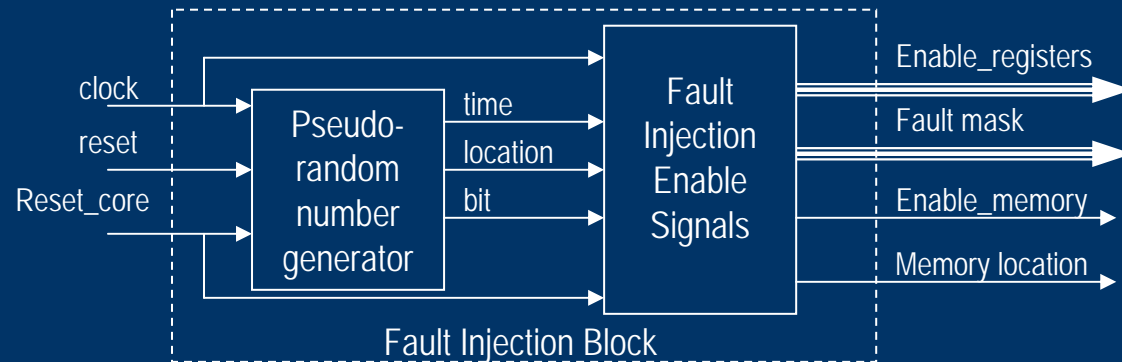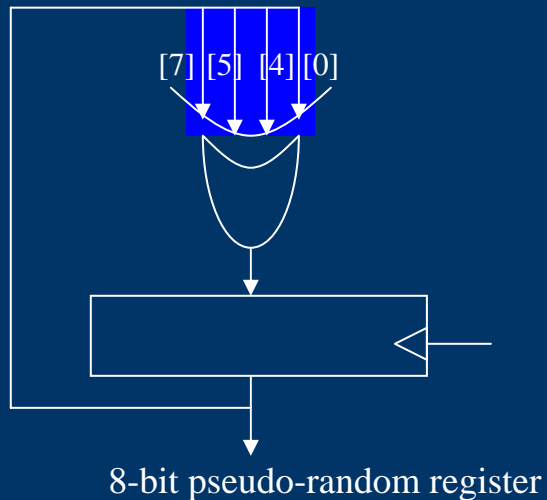

# Device Under Test Core
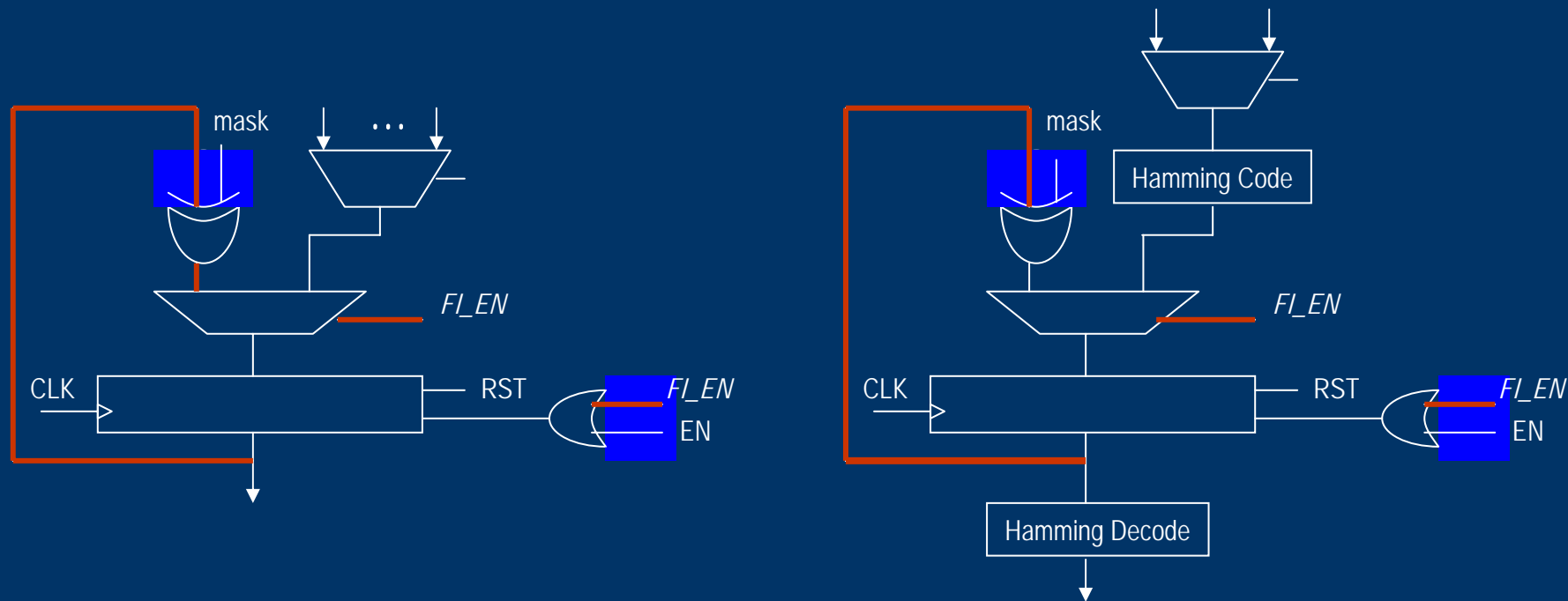
## Registers


- Special paths are required in the high-level description to ensure the full controllability of a fault insertion.



# Device Under Test Core
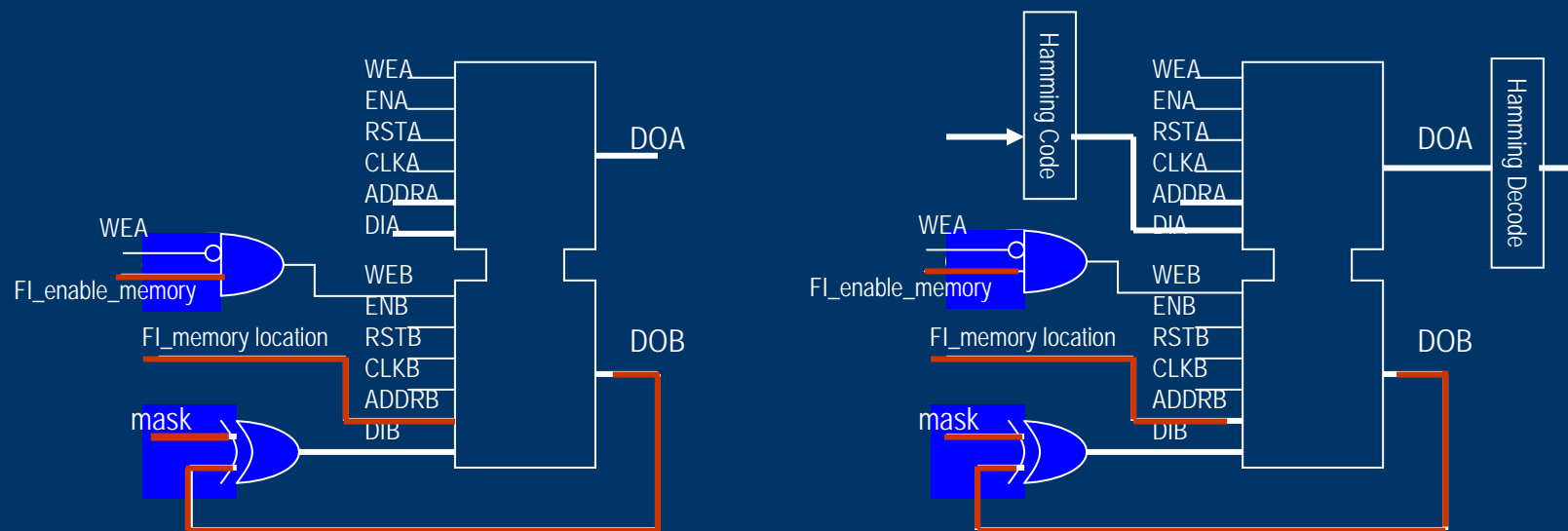
## *Memory*

- Dual-port memories allows high flexibility with low extra logic.
- Good fault model approximation: the faults can be injected in the memory at any time (all micro-controller states) without perturbing the normal operation.




# Monitor Block


- Observability of an error in response of a fault injected in the DUT.
- Assumption: application results will be stored in the internal memory.
- Two main tasks are performed by the monitor block:
  - Clear all the internal memory in order to avoid accumulation of faults;
  - Read all the internal memory to analyse if there is an error or not.
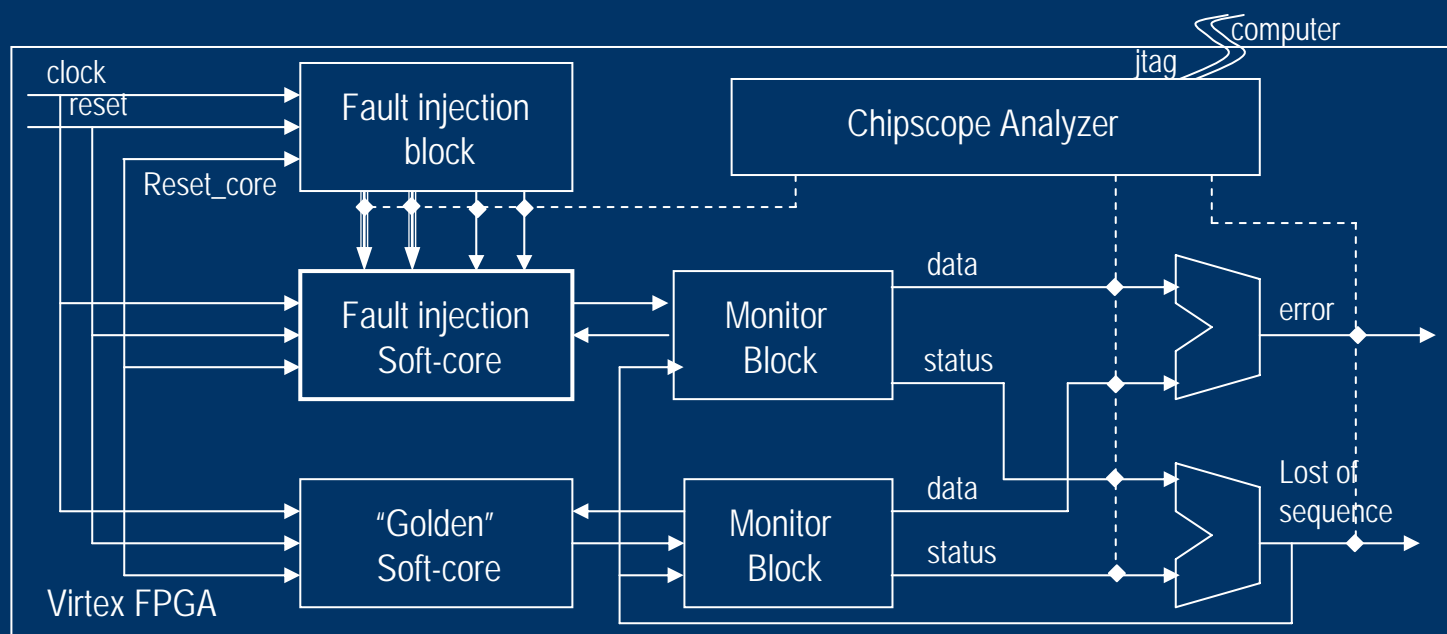
# Fault Injection Platform (Emulation)

- “Golden” chip approach was used to observe the faults in the system.
- Comparing:
  - Data memory  $\xrightarrow{\hspace{10em}}$  error
  - Application\_end signal in the end  $\xrightarrow{\hspace{10em}}$  lost of sequence.



# Fault Injection Signals

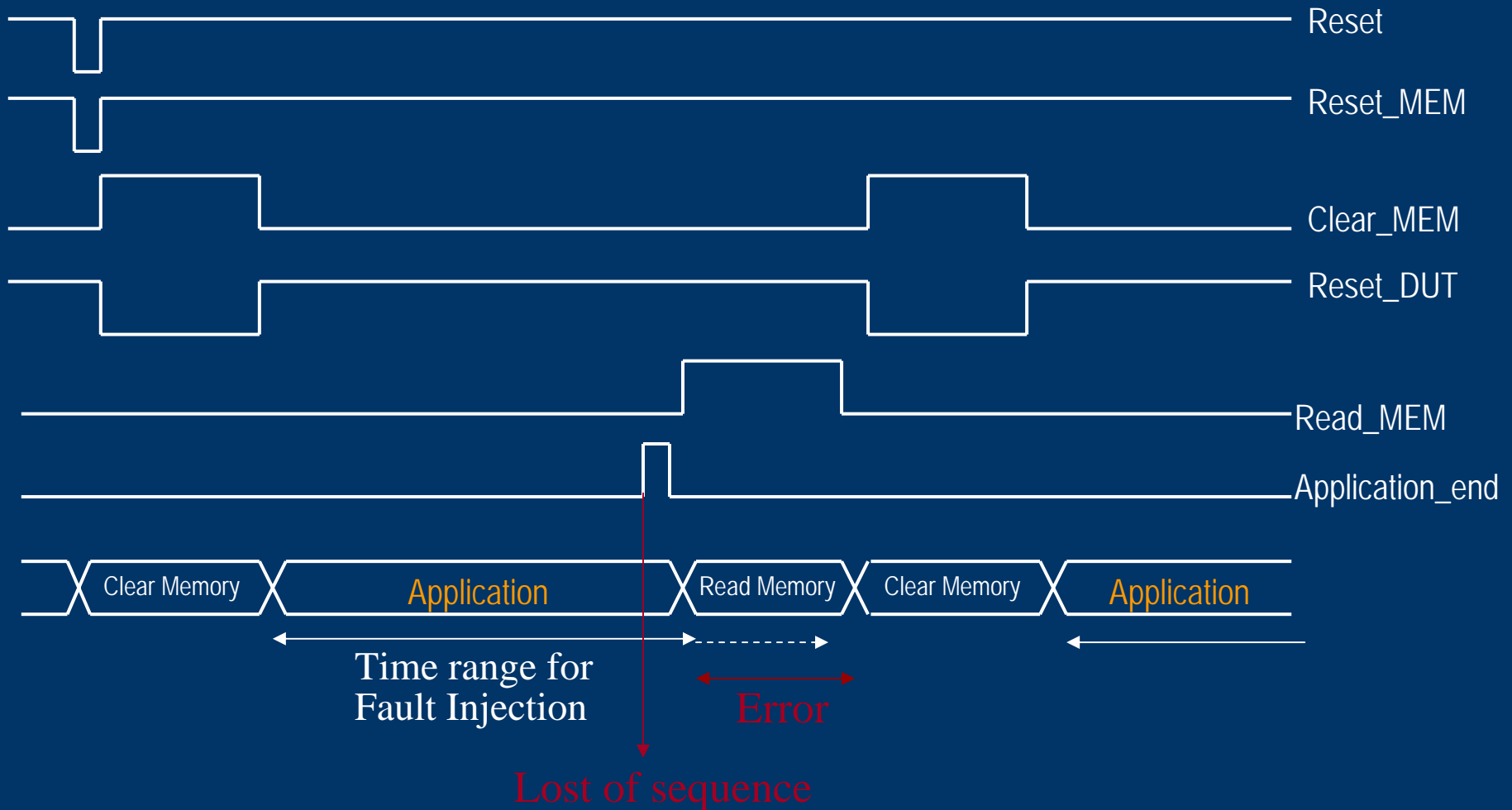




# Case Study: $\mu$ 8051 Fault Injection Experiment
 
## *Virtex Platform*

- The fault injection system and the (DUT) were implemented in Virtex FPGA platform.
- Thousands of faults were injected in some seconds
- The **emulation in FPGA** showed a  $\sim 120,000$  times acceleration



- **Component:** Virtex XCV300 - 240p
- 8051-like micro-controller runs at 10 MHz
- Fault injection Standard 8051
  - 28 % LUTs
- Fault injection Hardened 8051
  - 30 % LUTs


# Fault Injection

FPGAs

(Directly into the bitstream)
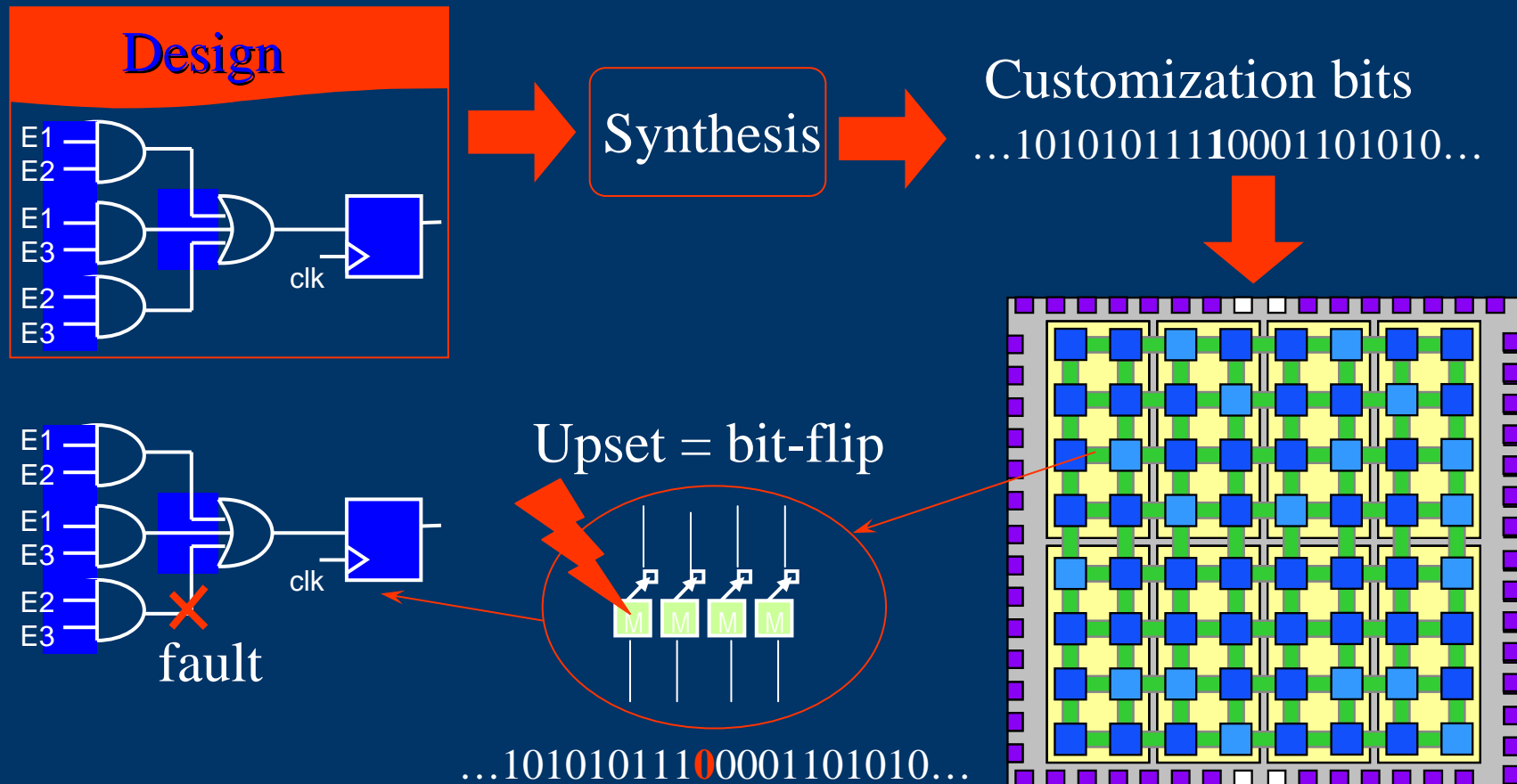
# Context

- Many digital designs are synthesized in SRAM based FPGAs
- Transient faults?



# Motivation

- A way to test the reliability of a (fault-tolerant) design is to perform **fault injection**, simulating the effects of upsets (bit-flips), and see how the design responds
- The estimated time for injecting one bit fault in a FPGA bitstream is around **1 to 3 seconds**
- The **main steps** of the fault injection are:
  - read the bit file
  - flip one bit
  - write the new bit file
  - download it to the board by the configuration mode interface
  - check the output signal

# Fault Injection Cost Analysis

## XCV300 Analysis


CLB Rows x CLB Cols  
32 x 48

Total of 1.536 CLBs  
1.327.104 CLB Bits

31 days!


Total of 470 CLBs Used  
406.080 CLB Bits

9.5 days!

 
 
# CLB View in the FPGA Editor



Which bit in the bitstream correspond to the logic?



Which bit in the bitstream correspond to this connection?

# Virtex Bitstream

586 bits

  

What does this bit do?

# SEUs Effects on FPGAs I




The diagram shows a complex grid of routing lines representing an FPGA. A specific line is highlighted in pink, indicating a bit flip. A blue line points from a text box to this pink line. The text box contains the following information:

**Bit Flip in a Single Line**  
bit: 03 frame: 29

**Fault effect:**  
- Open Circuit

# SEUs Effects on FPGAs II

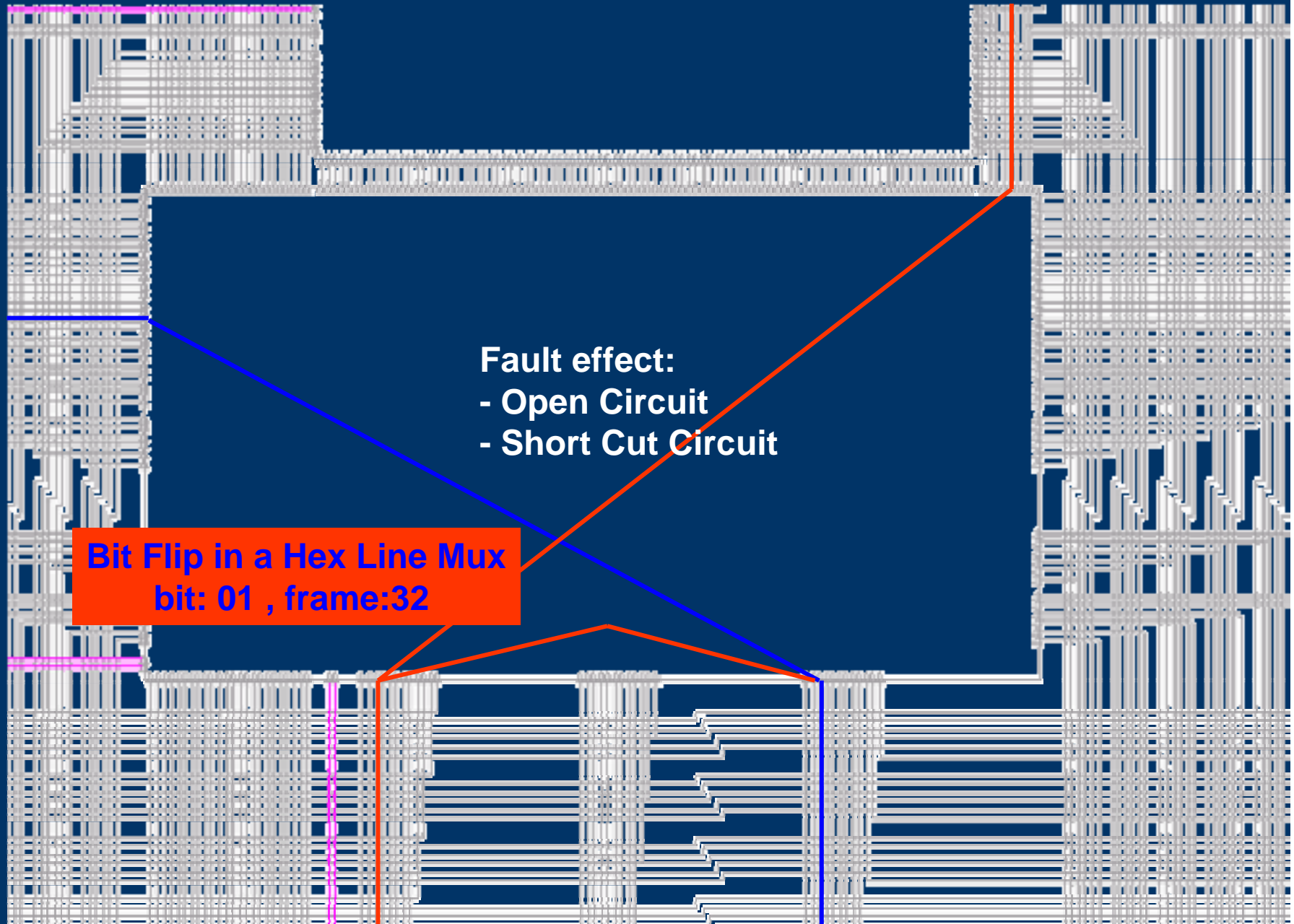

Fault effect:  
- Open Circuit  
- Short Cut Circuit

Bit Flip in a Hex Line Mux  
bit: 01 , frame:32