

SISTEMAS DIGITAIS

Linguagem de Descrição de Hardware
VHDL

Prof. Fernanda Gusmão de Lima Kastensmidt
fglima@inf.ufrgs.br

Linguagem de Descrição de Hardware

- Hardware Description Language (HDL) = "Programming"-language para modelar hardware digital
- **VHDL = VHSIC Hardware Description Language**
- **VHSIC = Very High Speed Integrated Circuit Hardware description, simulation, and synthesis**

Descreve o hardware em diferentes níveis:

- comportamental, equação lógica, estrutural
- Metodologia de projeto Top-down
- Independe de tecnologia


VHDL

- VHDL foi desenvolvido primeiramente pelo Departamento de Defesa Americano: the American Department of Defense (DoD).
- Em 1987, VHDL foi padronizado pelo Instituto Americano de Engenharia Eletro e Eletrônica: American Institute of Electrical and Electronics Engineers (IEEE) em 1993.

International Standards

- **IEEE Std 1076-1987**
- **IEEE Std 1076-1993**
- VHDL para circuitos análogos e mistos é chamado de VHDL-AMS (**a**nalogue- **m**ixed- **s**ignal) e é um subconjunto do VHDL.
 - **Analogue- and mixed-signal extension: VHDL-AMS**
 - **IEEE Std 1076.1-1999**

Fluxo de Projeto

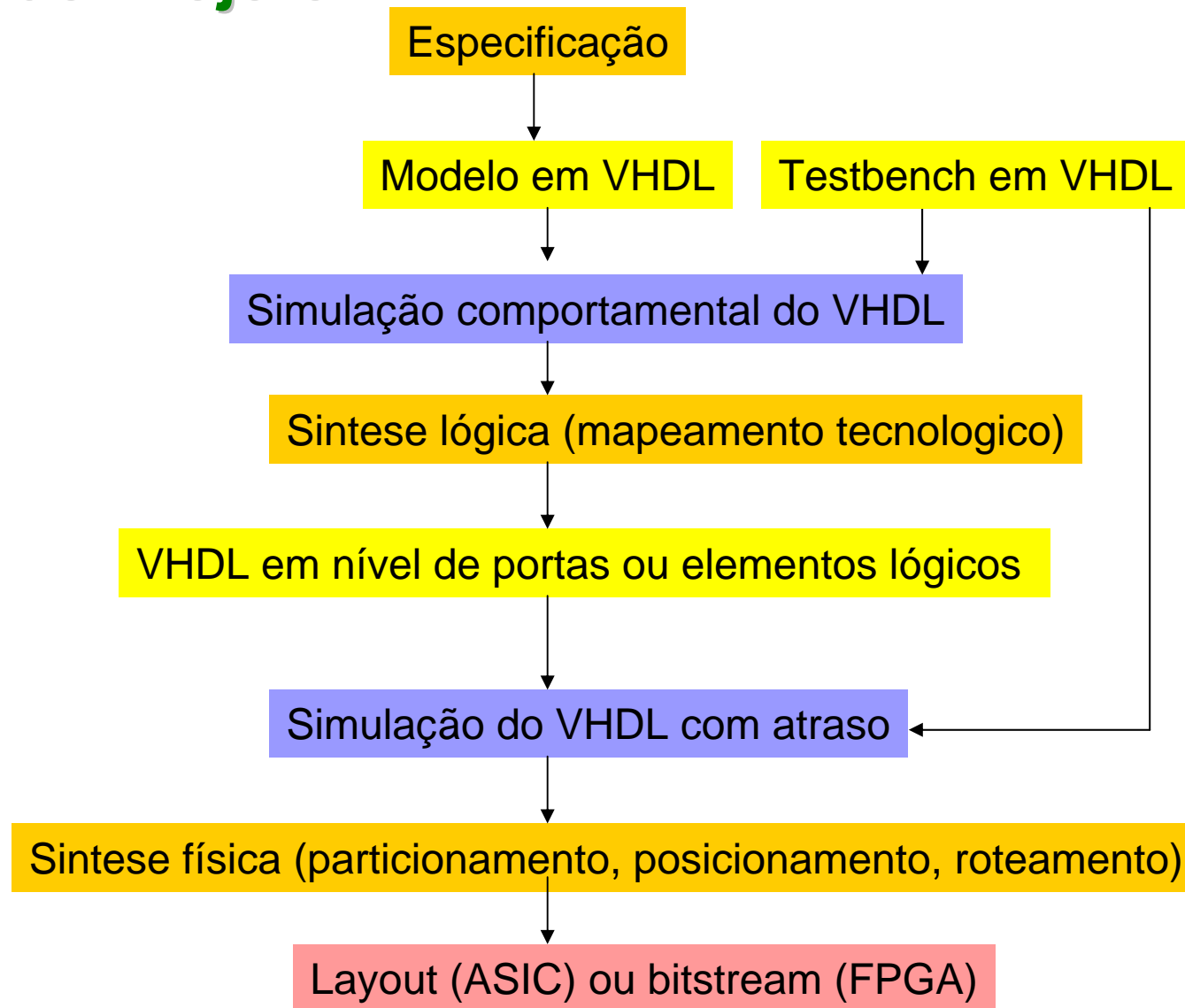

Sintaxe da linguagem VHDL

Geral

- Não é sensível a maiúsculas e minúsculas
- Comentário de linha inteira usando dois traços (--) no começo da linha
- Comandos são terminados por ponto e vírgula (;)
- Delimitador de elementos de uma lista: vírgula (,)
- Assinalamento de sinais com flecha (<=)
- Nomes devem começar com letras

Elementos Estruturais

- **Entity** : entidade que define a interface
- **Architecture** : implementação da arquitetura que pode ser comportamental ou estrutural
- **Configuration** : usado para configurar a simulação ou síntese, fazendo a conexão entre a arquitetura e a entidade.
- **Process** : controlado por um evento, os processos são todos concorrentes.
- **Package** : projeto modular, define os tipos de dados e as constantes a serem usadas no projeto.
- **Library** : usada para funções específicas de aritmética, lógica e outras.

Estrutura do VHDL

```
library library_name;  
use library_name.tipo;
```

```
entity name is  
port(pino1 : in tipo;  
      pino2 : in tipo;  
      pino3 : out tipo);  
name end;
```

```
architecture name_tipo of name is
```

→ <declaração de componentes> 5

→ <declaração de sinais> 3

```
begin
```

```
process(sinais)  
begin  
end process;
```

```
process(clk)  
begin  
end process;
```

→ <outros comandos> 4

→ <instanciação de componentes>

```
end;
```

Bibliotecas IEEE para VHDL

Library IEEE

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_textio.all;  
use IEEE.std_logic_arith.all;  
use IEEE.numeric_bit.all;  
use IEEE.numeric_std.all;  
use IEEE.std_logic_signed.all;  
use IEEE.std_logic_unsigned.all;  
use IEEE.math_real.all;  
use IEEE.math_complex.all;
```

```
library IEEE;  
use IEEE.std_logic_1164.all;
```

- The package [std_logic_1164](#) provides enhanced signal types
- Types defined include:
- std_ulogic
- std_ulogic_vector
- std_logic
- std_logic_vector

```
library IEEE;  
use IEEE.std_logic_textio.all;
```

- The package [textio](#) provides user input/output.
- Types defined include:
 - line
 - text
 - side
 - width
- Functions defined include: readline, read, writeline, write, endl

```
library IEEE;  
use IEEE.std_logic_arith.all;
```

- [std_logic_arith_syn.vhd](#) defines types signed and unsigned and has arithmetic functions that operate on signal types signed and unsigned and std_logic_vector and std_ulogic_vector, but adding A to B of std_logic_vector type, needs unsigned(A) + unsigned(B).
- [std_logic_arith_ex.vhd](#) has arithmetic functions that operate on signal types std_logic_vector and std_ulogic_vector

```
library IEEE;  
use IEEE.numeric_bit.all;  
use IEEE.numeric_std.all
```

- The package [numeric_bit](#) provides numerical computation Types defined include: unsigned signed arrays of type bit for signals
- The package [numeric_std](#) provides numerical computation Types defined include: unsigned signed arrays of type std_logic for signals

```
library IEEE;  
use IEEE.std_logic_signed.all;  
use IEEE.std_logic_unsigned.all
```


- The package [std_logic_signed](#) provides signed numerical computation on type std_logic_vector
- The package [std_logic_unsigned](#) provides unsigned numerical computation on type std_logic_vector

```
library IEEE;  
use IEEE.math_real.all;  
use IEEE.math_complex.all;
```

- The package [math_real](#) provides numerical computation on type real
- The package [math_complex](#) provides numerical computation Types defined include: complex, complex_vector, complex_polar


Modos dos pinos da Entity e de Sinais Internos

Modos dos pinos da entidade

 


in:

Valor do sinal do pino é read-only

 

out:

Valor do sinal do pino é write-only

 

buffer:


O sinal pode ser também lido da saída

inout:

Pino bidirecional

 Exemplos de entidades


```
entity HALFADDER is
  port(
    A, B:          in  std_logic;
    SUM, CARRY: out std_logic);
end HALFADDER;
-- VHDL'93: end entity HALFADDER
```



```
entity ADDER is
  port(
    A, B:          in  std_logic_vector(3 downto 0);
    SUM:          out std_logic_vector(3 downto 0);
    CARRY:        out std_logic );
end ADDER;
```

Tipos de dados de pinos e sinais e declaração de sinais

Standard Data Types

 

```
package STANDARD is
  type BOOLEAN is (FALSE,TRUE);
  type BIT is (`0`,`1`);
  type CHARACTER is (-- ascii set);
  type INTEGER is range
    -- implementation defined
  type REAL is range
    -- implementation defined
  -- BIT_VECTOR, STRING, TIME
end STANDARD;
```

Tipo de dado: TIME

- **Uso:**
 - testbenches
 - Atraso de portas
- **Unidades de tempo disponíveis:**
 - fs,
 - ps,
 - ns,
 - us,
 - ms,
 - sec,
 - min,
 - hr

```
architecture EXAMPLE of TIME_TYPE is
    signal CLK : bit := `0';
    constant PERIOD : time := 50 ns;

begin
    process
    begin
        wait for 50 ns;
        ...
        wait for PERIOD ;
        ...
        wait for 5 * PERIOD ;
        ...
        wait for PERIOD * 5.5;
    end process;

    ...

    -- concurrent signal assignment
    CLK <= not CLK after 0.025 us;
    -- or with constant time
    -- CLK <= not CLK after PERIOD/2;
end EXAMPLE;
```

Tipo de dados: Bit

- O tipo de dado deve estar especificado no:
 - Port
 - Declaração dos sinais
- Os tipos devem ser compatíveis no assinalamento.

```
entity FULLADDER is
  port(A, B, CARRY_IN: in  bit;
        SUM, CARRY:      out bit);
end FULLADDER;

architecture MIX of FULLADDER is

begin
  SUM <= A xor B xor CARRY_IN;
  CARRY <= (A and B) or (A and CARRY_IN)
or (B and CARRY_IN);

end MIX;
```

Problemas com o tipo: BIT

type BIT is ('0', '1')

- **Valores `0` e `1`, apenas**
 - Valor padrão `0`
- **Para simulação e síntese é preciso outros valores como:**
 - Não inicializado
 - Alta impedancia
 - Não definido
 - Não interessa (X)
 - Diferentes correntes

Tipo Binário com múltiplos valores: STD_LOGIC

- IEEE-standard
- 9 valores padronizados pela IEEE
- standard IEEE 1164 (STD_LOGIC_1164)

IEEE Standard Logic Type

```
type STD_ULOGIC is (  
    `U`, -- uninitialized  
    `X`, -- strong 0 or 1 (= unknown)  
    `0`, -- strong 0  
    `1`, -- strong 1  
    `Z`, -- high impedance  
    `W`, -- weak 0 or 1 (= unknown)  
    `L`, -- weak 0  
    `H`, -- weak 1  
    `-`, -- don't care);
```

Exemplo de declaração de sinais

signal <nome> : tipo := inicialização;

```
Library ieee;
Use ieee.std_logic_1164.all;

entity FULLADDER is
  port(A, B, CARRY_IN: in  std_logic;
        SUM, CARRY:      out std_logic);
end FULLADDER;

architecture MIX of FULLADDER is
  signal x : std_logic;
begin
  x <= A xor B;
  SUM <= x xor CARRY_IN;
  CARRY <= (A and B) or (A and CARRY_IN)
  or (B and CARRY_IN);

end MIX;
```



Tipo de dados: Std_logic

- O tipo de dado deve estar especificado no:
 - port
 - Declaração dos sinais
- Os tipos devem ser compatíveis no assinalamento.

```
Library ieee;
Use ieee.std_logic_1164.all;

entity FULLADDER is
  port(A, B, CARRY_IN: in  std_logic;
        SUM, CARRY:      out std_logic);
end FULLADDER;

architecture MIX of FULLADDER is


begin
  SUM <= A xor B xor CARRY_IN;
  CARRY <= (A and B) or (A and CARRY_IN)
or (B and CARRY_IN);

end MIX;
```

Definição de Array

- Coleção de sinais do mesmo tipo
- Array pre-definido
 - bit_vector (array of bit)
 - string (array of character)
- A definição do tamanho do array é dada na declaração do sinal ou do pino.
 
```
signal A_BUS, Z_BUS : bit_vector (3 downto 0);
```



```
signal A_BUS, Z_BUS : std_logic_vector(3 downto 0);
```

```
Z_BUS <= A_BUS
```




```
Z_BUS(3) <= A_BUS(0)
```



Assignments with Array Types
 
```
architecture EXAMPLE of ARRAYS is  
  signal Z_BUS : std_logic_vector (3 downto 0);  
  signal C_BUS : std_logic_vector (0 to 3);  
begin  
  Z_BUS <= C_BUS;  
end EXAMPLE;
```



Cuidado ao usar (X downto 0) ou (0 to X)

Tipo Integer, Signed e Unsigned

- Os numeros inteiros podem variar de $-2^{31} + 1$ to $+2^{31} - 1$
- (-2147483647 to +2147483647).
- A representação padrão é em decimal.
- Para utilizar uma outra representação é preciso mostrar explicitamente:

binary 2#...#

Octal 8#...#

Hexadecimal 16#...#

Tipos de assinalamento para 'std_logic'

architecture EXAMPLE of ASSIGNMENT is

```
signal Z_BUS : std_logic_vector (3 downto 0);  
signal BIG_BUS : std_logic_vector (15 downto 0);
```

```
begin
```

```
-- legal assignments:
```

```
Z_BUS(3) <= '1';
```

```
Z_BUS <= "1100";
```

```
Z_BUS <= b" 1100 ";
```

```
Z_BUS <= x" c ";
```

```
Z_BUS <= X" C ";
```

```
BIG_BUS <= B` `0000 _ 0001_0010_0011 ` `;
```

```
end EXAMPLE;
```

Simple para um dígito


Aspas duplas para múltiplos dígitos

Concatenação (&)

```
architecture EXAMPLE_1 of CONCATENATION is
  signal BYTE          : std_logic_vector (7 downto 0);
  signal A_BUS, B_BUS : std_logic_vector (3 downto 0);
begin

  BYTE  <= A_BUS & B_BUS;


end EXAMPLE;
```

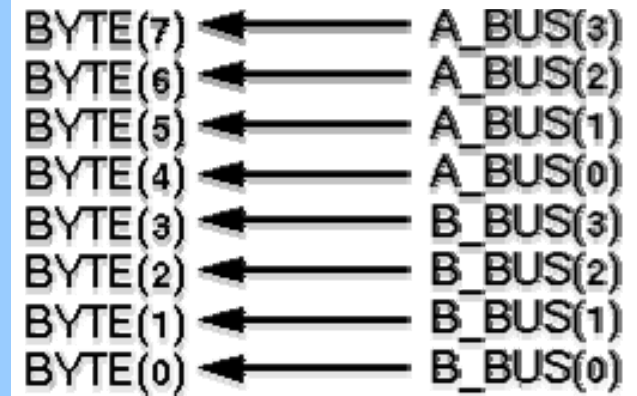

```
architecture EXAMPLE_2 of CONCATENATION is
  signal Z_BUS : std_logic_vector (3 downto 0);
  signal A_BIT, B_BIT, C_BIT, D_BIT : bit;
begin

  Z_BUS <= A_BIT & B_BIT & C_BIT & D_BIT;

end EXAMPLE;
```

 

Lado direito do assinalamento

Agregação

```
architecture EXAMPLE of AGGREGATES is
  signal BYTE : std_logic_vector (7 downto 0);
  signal Z_BUS : std_logic_vector (3 downto 0);
  signal A_BIT, B_BIT, C_BIT, D_BIT : std_logic;
begin
  Z_BUS <= ( A_BIT, B_BIT, C_BIT, D_BIT );
  ( A_BIT, B_BIT, C_BIT, D_BIT ) <= std_logic'(`1011`);
  ( A_BIT, B_BIT, C_BIT, D_BIT ) <= BYTE(3 downto 0);

  BYTE <= ( 7 => `1`, 5 downto 1 => `1`, 6 => B_BIT, others => `0` );
end EXAMPLE;
```

Utilizando Porções de Arrays

```
architecture EXAMPLE of SLICES is
  signal BYTE : std_logic_vector (7 downto 0);
  signal A_BUS, Z_BUS : std_logic_vector (3 downto 0);
  signal A_BIT : bit;
begin
  BYTE (5 downto 2) <= A_BUS;
  --BYTE (5 downto 0) <= A_BUS;           -- wrong

  Z_BUS (1 downto 0) <= `0` & A_BIT;
  Z_BUS           <= BYTE (6 downto 3);
  --Z_BUS (0 to 1) <= `0` & B_BIT;     -- wrong

  A_BIT <= A_BUS (0);
end EXAMPLE;
```

Tipos Enumerados

architecture EXAMPLE of ENUMERATION is

```
type T_STATE is (RESET, START, EXECUTE, FINISH);
```

```
signal CURRENT_STATE, NEXT_STATE : T_STATE ;  
signal TWO_BIT_VEC : std_logic_vector(1 downto 0);
```

```
begin
```

```
-- valid signal assignments
```

```
NEXT_STATE      <= CURRENT_STATE;
```

```
CURRENT_STATE <= RESET;
```

```
-- invalid signal assignments
```

```
CURRENT_STATE <= "00";
```

```
CURRENT_STATE <= TWO_BIT_VEC;
```

```
end EXAMPLE;
```

Multidimensional Arrays

architecture EXAMPLE of ARRAY is

```
type INTEGER_VECTOR is  
array (1 to 8) of integer;
```

```
-- 1 --
```

```
type MATRIX_A is  
array(1 to 3) of INTEGER_VECTOR ;
```

```
-- 2 --
```

```
type MATRIX_B is  
array(1 to 4, 1 to 8) of integer ;
```

```
signal MATRIX_3x8 : MATRIX_A;  
signal MATRIX_4x8 : MATIRX_B;
```

```
begin
```

```
MATRIX_3x8(3)(5) <= 10; --array of array
```

```
MATRIX_4x8(4, 5) <= 17; -- 2 dim array
```

```
end EXAMPLE;
```

2 possibilities

- array of array
- multidimensional array

• Different referencing

• Barely supported by synthesis tools

architecture EXAMPLE of AGGREGATE is

type INTEGER_VECTOR is

array (1 to 8) of integer;

type MATRIX_A is

array(1 to 3) of INTEGER_VECTOR;

type MATRIX_B is

array(1 to 4, 1 to 8) of integer;

signal MATRIX3x8 : MATRIX_A;

signal MATRIX4x8 : MATIRX_B;

signal VEC0, VEC1,

VEC2, VEC3 : INTEGER_VECTOR;

begin

MATRIX3x8 <= (VEC0, VEC1, VEC2);

MATRIX4x8 <= (VEC0, VEC1, VEC2, VEC3);

MATRIX3x8 <= (others => VEC3);

MATRIX4x8 <= (others => VEC3);

MATRIX3x8 <= (others => (others => 5));

MATRIX4x8 <= (others => (others => 5));

end EXAMPLE;

Type Conversion

```
architecture EXAMPLE of CONVERSION is
    type MY_BYTE is array (7 downto 0) of std_logic;

    signal VECTOR:      std_logic_vector(7 downto 0);
    signal SOME_BITS:  bit_vector(7 downto 0);
    signal BYTE:       MY_BYTE;

begin

    SOME_BITS <= VECTOR;           -- wrong
    SOME_BITS <= Convert_to_Bit( VECTOR );

    BYTE <= VECTOR;               -- wrong
    BYTE <= MY_BYTE( VECTOR );

end EXAMPLE;
```

Conversions

Operator	Argument (arg)	Result
conv_integer(arg)	std_logic std_logic_vect or signed unsigned	integer
conv_unsigned(arg, size: integer) size: number of bits of the final result	std_logic signed unsigned integer	unsigned
conv_signed(arg, size: integer) size: number of bits of the final result	std_logic signed unsigned integer	signed
conv_std_logic_vector(arg, size: integer) size: number of bits of the final result	std_logic signed unsigned integer	std_logic_vector

Subtypes

architecture EXAMPLE of SUBTYPES is

```
type MY_WORD is array (15 downto 0) of std_logic;  
subtype SUB_WORD is std_logic_vector (15 downto 0);
```

```
subtype MS_BYTE is integer range 15 downto 8;  
subtype LS_BYTE is integer range 7 downto 0;
```

```
signal VECTOR:    std_logic_vector(15 downto 0);  
signal SOME_BITS: bit_vector(15 downto 0);  
signal WORD_1: MY_WORD;  
signal WORD_2: SUB_WORD;
```

begin

```
SOME_BITS <= VECTOR;                -- wrong  
SOME_BITS <= Convert_to_Bit(VECTOR);
```


```
WORD_1 <= VECTOR;                  -- wrong  
WORD_1 <= MY_WORD(VECTOR);
```

```
WORD_2 <= VECTOR;                  -- correct!
```

```
WORD_2(LS_BYTE) <= "11110000";  
end EXAMPLE;
```


Package

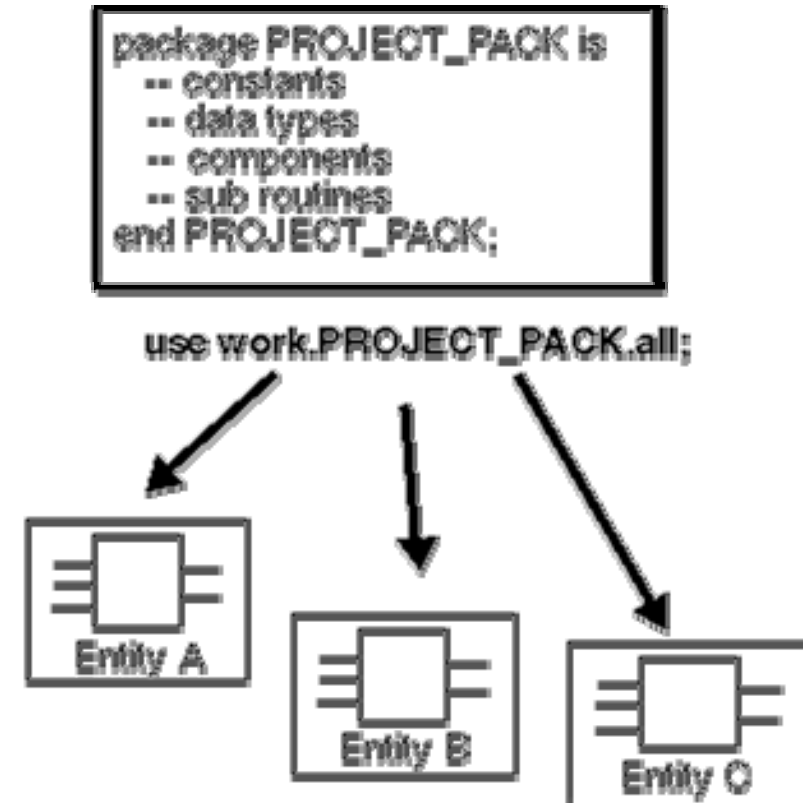- **Coleção de definições, tipos de dados e sub programas ou funções**
- **Referencia feita pelo grupo de projeto**
- **Vantagem:**
 - **Qualquer mudança é vista por todo o time rapidamente.**
 - **Mesmo tipo de dado e uso ("downto vs. to")**
 - **Funções para todos!**



Declaração de sinais e constantes

architecture name_type **of** name_entity **is**

signal A, B, C : std_logic := '0';


signal D : std_logic_vector(3 downto 0) := "0000";

signal F: integer range 0 to 4;

constant G : integer := 9;

BEGIN

inicialização

 

Operadores e Comandos

Operadores

logical not

and

or

nand

nor

xor

xnor

relational

=

/=

<

<=

>=

>

shift sll

srl

sla

sra

rol

ror

arithmetic

+

-

/

mod

rem

abs

Operadores e seus Argumentos

arg1 operator arg2 → result, operator: + , -	
arg1, arg2	result
both std_logic_vector std_logic_vector, std_logic (or reverse) std_logic_vector, integer (or reverse)	std_logic_vector
both unsigned unsigned, std_logic (or reverse) unsigned, integer (or reverse)	unsigned or std_logic_vector
both signed signed, std_logic (or reverse) signed, integer (or reverse) signed, unsigned (or reverse)	signed or std_logic_vector

Table 1: Operators +,-

Operadores e seus Argumentos

arg1 operator arg2 → result, operator: *	
arg1, arg2	result
both std logic vector	std logic vector
both unsigned	unsigned o std_logic_vector
both signed	signed o std_logic_vector
signed, unsigned (or reverse)	signed o std_logic_vector

Table 2: *Operators* *

Operadores e seus Argumentos

arg1 operator arg2 → result, operator: <, <=, >, >=, =, /=	
arg1, arg2	result
both std_logic_vector std_logic_vector, integer (or reverse)	boolean
both unsigned both signed unsigned, integer (or reverse) signed, integer (or reverse) signed, unsigned (or reverse)	boolean

Table 3: *Comparison Operators*

Operadores Lógicos

Prioridade

- not (maior prioridade)
- and, or, nand, nor, xor, xnor (mesma prioridade)

Pre-definidos para

- bit, bit_vector
- boolean
- Para std_logic precisa usar a library `ieee.std_logic_1164.all;`

```
entity LOGIC_OP is
  port (A, B, C, D : in bit;
        Z1:         out bit;
        EQUAL :    out boolean);
end LOGIC_OP;
```

```
architecture EXAMPLE of LOGIC_OP is
begin
```



```
  Z1 <= A and (B or (not C xor D));
```

```
  EQUAL <= A xor B;           -- wrong
```

```
end EXAMPLE;
```

Operados Lógicos em Arrays
  
```
architecture EXAMPLE of LOGICAL_OP is  
  signal A_BUS, B_BUS : std_logic_vector (3 downto 0);  
  signal Z_BUS :      std_logic_vector (4 to 7);  
begin  
  Z_BUS <= A_BUS and B_BUS;  
end EXAMPLE;
```



Comandos concorrentes

Comandos concorrentes:

```
C <= A and B after 5 ns;
```

```
E <= C or D after 5 ns;
```

Se um atraso não é especificado, um “delta” atraso é assumido

```
C <= A and B;
```

```
E <= C or D;
```

A ordem do comando concorrente não é importante

```
E <= C or D;
```


```
C <= A and B;
```

Esse comando executa repidamente

```
CLK <= not CLK after 10 ns;
```

Este comando causa um erro na simulação






```
CLK <= not CLK;
```

 

Operadores de Deslocamento: só funcionam com bit_vector

```
signal A_BUS, B_BUS, Z_BUS : bit_vector (3 downto 0);  
Z_BUS <= A_BUS sll 2;  
Z_BUS <= B_BUS sra 1;  
Z_BUS <= A_BUS ror 3;
```

     At the end, the first value of the type is used for filling up



Assinalamento condicional

Comandos concorrentes

```
TARGET <= VALUE_1 when CONDITION_1 else  
      VALUE_2 when CONDITION_2 else  
      ...  
      VALUE_n;
```

Assinalamento seletivo

Comandos concorrentes

with EXPRESSION select

```
TARGET <= VALUE_1 when CHOICE_1,  
        VALUE_2 when CHOICE_2 | CHOICE_3,  
        VALUE_3 when CHOICE_4 to CHOICE_5,  
        VALUE_n when others;
```

Operadores de relação

BEGIN

```
S_out <= "00" when A <=B else  
    "11" when A="1100" else  
    "01";
```

END;

<=
less or equal

<
less than

=
equal

/=
unequal

>=
greater or equal

>
greater

Importante

- Comandos seletivos são puramente combinacionais e por isso, todas as possibilidades devem estar cobertas no comando.

```
TARGET <= VALUE_1 when CONDITION_1 else  
      VALUE_2 when CONDITION_2 else  
      VALUE_n;
```

with EXPRESSION select

```
TARGET <= VALUE_1 when CHOICE_1,  
      VALUE_2 when CHOICE_2 | CHOICE_3,  
      VALUE_3 when CHOICE_4 to CHOICE_5,  
      VALUE_n when others;
```

- Caso isso não aconteça, surgirão latches e flip-flops indesejados na síntese o que irá comprometer o desempenho do circuito.

Operadores Aritméticos

```
signal A, B, C: integer;  
signal RESULT: integer;
```

```
BEGIN
```

```
RESULT <= A + B * C;
```

+
addition

/
division

*
multiplication

-
subtraction

mod
modulo

**
exponentiation

abs
absolute value

rem
remainder

Uso da biblioteca `ieee.std_logic_arith.all`;

Declaração e Instanciação de Componentes

Declaração de componente

```
entity FULLADDER is
  port (A,B, CARRY_IN: in std_logic;
        SUM, CARRY: out std_logic);
end FULLADDER;
```

```
architecture STRUCT of FULLADDER is
  signal W_SUM, W_CARRY1, W_CARRY2 : std_logic;
```


```
  component HALFADDER
    port (A, B : in std_logic;
          SUM, CARRY : out std_logic);
  end component;
```

```
  component ORGATE
    port (A, B : in std_logic;
          RES : out std_logic);
  end component;
```

```
begin
```

```
  . . .
```

Modelo Hierarquico

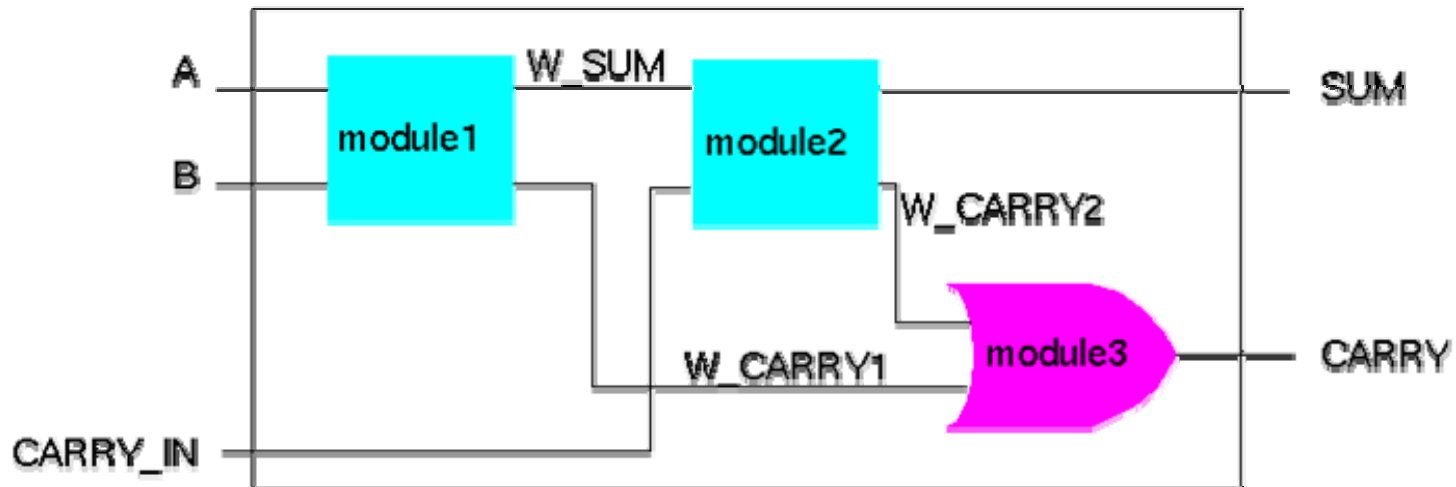

Full adder: 2 halfadders + 1 OR-gate

Instanciação de Componente

Assinalamento dos sinais (ports) pela ordem dos pinos na interface do componente

```
architecture STRUCT of FULLADDER is
  component HALFADDER
    port (A, B :          in  std_logic;
          SUM, CARRY : out std_logic);
  end component;
  component ORGATE
    port (A, B : in  std_logic;
          RES : out std_logic);
  end component;

  signal W_SUM, W_CARRY1, W_CARRY2: std_logic;

begin

  MODULE1: HALFADDER
    port map( A, B, W_SUM, W_CARRY1 );

  MODULE2: HALFADDER
    port map ( W_SUM, CARRY_IN,
              SUM, W_CARRY2 );

  MODULE3: ORGATE
    port map ( W_CARRY2, W_CARRY1, CARRY );

end STRUCT;
```

Instanciação de Componente: associação de nomes dos ports

```
entity FULLADDER is
  port (A,B, CARRY_IN: in  std_logic;
        SUM, CARRY:  out std_logic);
end FULLADDER;

architecture STRUCT of FULLADDER is

  component HALFADDER
    port (A, B :          in std_logic;
          SUM, CARRY : out std_logic);
  end component;

  ...
  signal W_SUM, W_CARRY1, W_CARRY2 : std_logic;

begin

  MODULE1: HALFADDER
    port map ( A      => A,
              SUM     => W_SUM,
              B       => B,
              CARRY   => W_CARRY1 );

  ...
end STRUCT;
```

Assinalamento explícito



Uso de configuração

- **Seleciona a arquitetura para a entidade topo (top-level entity)**
- **Gera a hierarquia de simulação ou síntese**

```
entity FULLADDER is
...
end FULLADDER;

architecture STRUCT of FULLADDER is
...
end STRUCT;

architecture SCHEME of FULLADDER is
...
end SCHEME;

configuration CFG_FULLADDER of FULLADDER is
  for STRUCT -- select architecture STRUCT
    -- use default configuration rules
  end for;
end configuration CFG_FULLADDER ;
```

Configuração: Exemplo (1)

```
entity A is
  port(A, B: in std_logic;
        SUM, CARRY: out std_logic);
end A;
```

```
architecture RTL of A is
  ...
```

```
entity B is
  port(U,V: in std_logic;
        X,Y: out std_logic);
end B;
```

```
architecture GATE of B is
  ...
```

```
entity FULLADDER is
  port(A, B, CARRY_IN: in std_logic;
        SUM, CARRY: out std_logic);
end FULLADDER;
architecture STRUCT of FULLADDER is

  component HALFADDER
    port(A, B: in std_logic;
          SUM, CARRY: out std_logic);
    ...

    signal W_SUM, W_CARRY1, W_CARRY2: std_logic;

begin
  MODULE1: HALFADDER
    port map (A, B, W_SUM, W_CARRY1);

  MODULE2: HALFADDER
    port map(W_SUM, CARRY_IN, SUM, W_CARRY2);
    ...

end STRUCT;
```

Configuração: Exemplo (2)

```
entity A is
  port (A, B:          in  std_logic;
        SUM, CARRY: out std_logic);
end A;
```

```
architecture RTL of A is
  ...
```

```
entity B is
  port (U,V: in  std_logic;
        X,Y: out std_logic);
end B;
```

```
architecture GATE of B is
  ...
```


```
configuration CFG_FULLADDER of FULLADDER is
  for STRUCT
    for MODULE2: HALFADDER
      use entity work.B(GATE);
      port map ( U => A,
                 V => B,
                 X => SUM,
                 Y => CARRY );
    end for;

    for others : HALFADDER
      use entity work.A(RTL);
    end for;
  end for;
end CFG_FULLADDER;
```


Testbench

Testbench

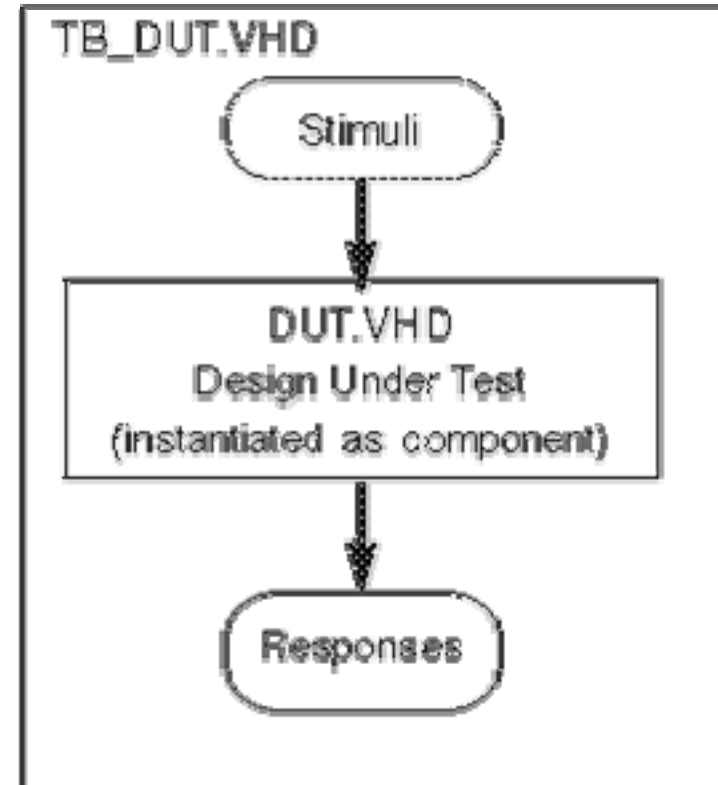- VHDL code para a arquitetura topo
- Pode não ter sinais de interface
- O projeto DUT deve ser instanciado no testbench
- Comandos para o estímulo de sinais
- Testbenches simples: a análise da resposta por inspeção das formas de onda.
- Testbenches sofisticados podem ocupar mais de 50% do projeto.



Example of Testbench

 

Design Under Test (DUT)

```
entity ADDER IS
port (A,B :          in bit;
      CARRY,SUM : out bit);
end ADDER;
```

```
architecture RTL of ADDER is
begin
SUM <= A xor B;
CARRY <= A and B;
end RTL;
```

```
entity TB_ADDER IS
end TB_ADDER;
```

```
architecture TEST of TB_ADDER is
  component ADDER
```

```
port (A, B:          in bit;
      CARRY, SUM: out bit);
```

```
end component;
```

```
signal A_I, B_I, CARRY_I, SUM_I : bit;
```

```
begin
```

```
DUT: ADDER port map (A_I, B_I, CARRY_I, SUM_I);
```

```
STIMULUS: process
```

```
begin
```

```
A_I <= '1'; B_I <= '0';
```

```
wait for 10 ns;
```

```
A_I <= '1'; B_I <= '1';
```

```
wait for 10 ns;
```

```
-- and so on ...
```

```
end process STIMULUS;
```

```
end TEST;
```