

CMP238

Projeto e Teste de Sistemas VLSI


Linguagem de Descrição de Hardware
VHDL

Prof. Fernanda Gusmão de Lima Kastensmidt
fglima@inf.ufrgs.br

7 e 8
Comandos Sequencias

Comandos Sequenciais

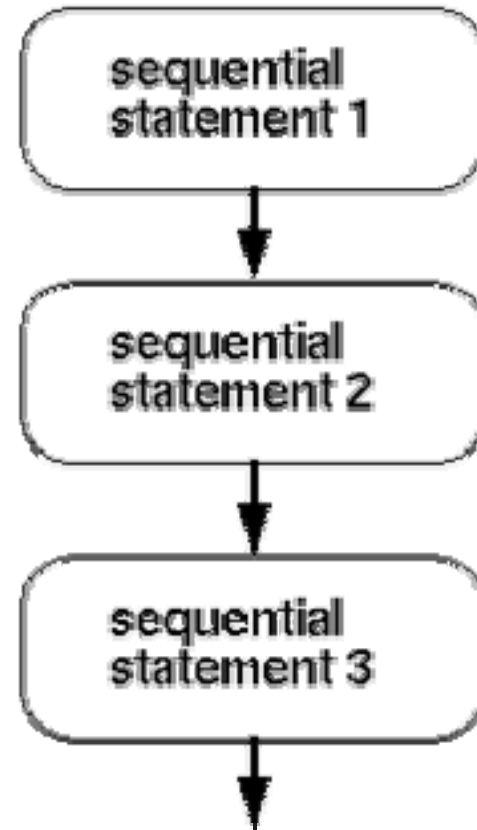- Execução de acordo com a ordem com que os comandos sequenciais aparecem.
- Permitido apenas dentro da estrutura **process**
- Usado para representar algoritmos.



Process


- Contem comandos sequenciais
- Existe apenas dentro da arquitetura
- Todos os **process** rodam ao mesmo tempo de maneira concorrente.
- **A execução dos process são controladas por:**
 - Lista de sensibilidade (sinais de trigger para a execução do **process**), **ou**
 - Comandos de **wait**
- O label do process é opcional

```
<label>: process (lista)
begin

<comandos>

end process;
```

VHDL Communication Model

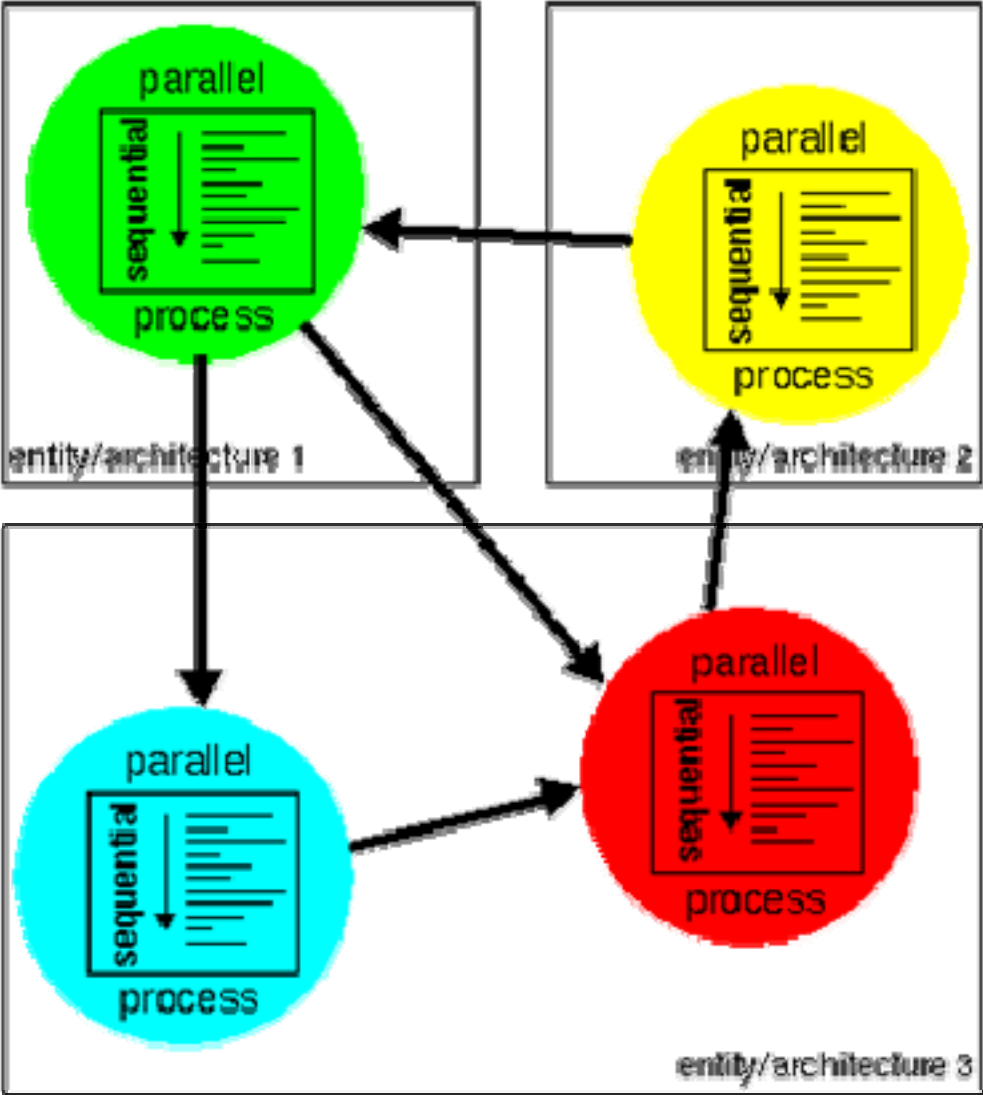

Exemplo de Process

```
entity AND_OR_XOR is
  port (A,B :                in std_logic;
        Z_OR, Z_AND, Z_XOR : out std_logic);
end AND_OR_XOR;
```

```
architecture RTL of AND_OR_XOR is
begin
```

```
  A_O_X: process (A, B)
  begin
    Z_OR  <= A or  B;
    Z_AND <= A and B;
    Z_XOR <= A xor B;
  end process A_O_X ;
```

```
end RTL;
```

Exemplo de Process


```
entity AND_OR_XOR is
  port (A,B           : in  std_logic;
        Z_OR         : out std_logic);
end AND_OR_XOR;
```

```
architecture RTL of AND_OR_XOR is
begin
```

```
  A_O_X: process (A, B)
  begin
    Z_OR <= A or  B;
    Z_OR <= A and B;
    Z_OR <= A xor B;
  end process A_O_X ;
```

```
end RTL;
```

Qual hardware é
gerado na síntese?

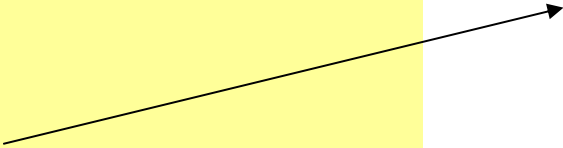

Comando: IF... then ... else

```
if CONDITION then
  -- sequential statements
end if;
```

```
if CONDITION then
  -- sequential statements
else
  -- sequential statements
end if;
```

```
if CONDITION then
  -- sequential statements
elsif CONDITION then
  -- sequential statements
...
else
  -- sequential statements
end if;
```

A condição é uma expressão booleana

Opcional:

-elsif

-else

Cuidado: todas as opções de ifs devem estar cobertas no comando, se não, latches e flip-flops indesejados surgirão na síntese.

IF Statement: Exemplo

```
entity IF_STATEMENT is
    port (A, B, C, X : in std_logic_vector (3 downto 0);
          Z           : out std_logic_vector (3 downto 0);
    end IF_STATEMENT;
```

```
architecture EXAMPLE1 of IF_STATEMENT is
begin
    process (A, B, C, X)
    begin
        Z <= A;
        if (X = "1111") then
            Z <= B;
        elsif (X > "1000") then
            Z <= C;
        end if;
    end process;
end EXAMPLE1;
```

```
architecture EXAMPLE2 of IF_STATEMENT is
begin
    process (A, B, C, X)
    begin
        if (X = "1111") then
            Z <= B;
        elsif (X > "1000") then
            Z <= C;
        else
            Z <= a;
        end if;
    end process;
end EXAMPLE2;
```

Todos os sinais
usados no process
estão na lista de
sensibilidade

Tente não cobrir todas as opções para ver o que acontece....

```
entity IF_STATEMENT is
    port (A, B, C, X : in std_logic_vector (3 downto 0);
          Z           : out std_logic_vector (3 downto 0);
    end IF_STATEMENT;
```

```
architecture EXAMPLE1 of IF_STATEMENT is
begin
    process (A, B, C, X)
    begin
        -- Z <= A;
        if (X = "1111") then
            Z <= B;
        elsif (X > "1000") then
            Z <= C;
        end if;
    end process;
end EXAMPLE1;
```

Todos os sinais
usados no process
estão na lista de
sensibilidade

```
architecture EXAMPLE2 of IF_STATEMENT is
begin
    process (A, B, C, X)
    begin
        if (X = "1111") then
            Z <= B;
        elsif (X > "1000") then
            Z <= C;
        --else
        -- Z <= a;
        end if;
    end process;
end EXAMPLE2;
```

Comando: CASE ... is... WHEN

```
case EXPRESSION is

  when VALUE_1 =>
    -- sequential statements

  when VALUE_2 | VALUE_3 =>
    -- sequential statements

  when VALUE_4 to VALUE_N =>
    -- sequential statements

  when others =>
    -- sequential statements

end case ;
```

- Opções não podem ser coincidentes.
- Todas as opções devem ser cobertas:
 - valores simples
 - intervalo de valores
 - seleção de valores por ("|" que significa "or")
 - uso obrigatório de "when others" para cobrir a(s) última(s) opções.

```
entity CASE_STATEMENT is
  port (A, B, C : in std_logic_vector(3 downto 0);
        X       : in std_logic_vector(3 downto 0);
        Z       : std_logic_vector(3 downto 0));
end CASE_STATEMENT;
```

architecture EXAMPLE of CASE_STATEMENT is
signal X_int : integer range from 0 to 15;

```
begin
X_int <= conv_integer(X);
  process (A, B, C, X_int)
  begin
    case X_int is
      when 0 =>
        Z <= A;
      when 7 | 9 =>
        Z <= B;
      when 1 to 5 =>
        Z <= C;
      when others =>
        Z <= 0;
    end case;
  end process;
end EXAMPLE;
```

```
entity RANGE_2 is
port (A, B, C, X : in  std_logic_vector(3 downto 0);
      Z          : out std_logic_vector(3 downto 0);
end RANGE_2;
```

```
architecture EXAMPLE of RANGE_2 is
begin
```

```
  process (A, B, C, X)
  begin
```

```
    case X is
```

```
      when "0000" =>
```

```
        Z <= A;
```

```
      when "0111" | "1001" =>
```

```
        Z <= B;
```

```
      when "0001" to "0101" =>           -- wrong
```

```
        Z <= C;
```

```
      when others =>
```

```
        Z <= 0;
```

```
    end case;
```

```
  end process;
```

```
end EXAMPLE;
```

A sequencia de valores é indefinida para arrays.

```
entity CONDITIONAL_ASSIGNMENT is
  port (A, B, C, X : in std_logic_vector (3 downto 0);
        Z_CONC : out std_logic_vector (3 downto 0);
        Z_SEQ   : out std_logic_vector (3 downto 0));
end CONDITIONAL_ASSIGNMENT;
```

```
architecture EXAMPLE of CONDITIONAL_ASSIGNMENT is
begin
```

```
-- Concurrent version of conditional signal assignment
Z_CONC <= B when X = "1111" else
  C when X > "1000" else
  A;
```

Comando concorrente

```
-- Equivalent sequential statements
process (A, B, C, X)
begin
```

```
  if (X = "1111") then
    Z_SEQ <= B
  elsif (X > "1000") then
    Z_SEQ <= C;
  else
    Z_SEQ <= A;
  end if;
```

Comando sequencial no process


```
  end process;
end EXAMPLE;
```

IMP: ambos comandos são concorrentes entre si e geram o mesmo circuito combinacional.

Variaveis

- **Variaveis são usadas apenas em processes**
 - São declaradas antes do begin do process
 - Conhecidas apenas localmente no process onde foram declaradas
- **VHDL 93: variaveis globais**
 - Não sintetizavel
- **Assinalamento global**
 - signal to variable
 - variable to signal
 - types have to match

 
```
architecture RTL of XYZ is
    signal A, B, C : std_logic_vector(7 downto 0);
    signal Y, Z : std_logic_vector(7 downto 0);
begin
    process (A, B, C)
        variable M, N : std_logic_vector(7 downto 0);
    begin
        M := A;
        N := B;
        Z <= M + N;
        M := C;
        Y <= M + N;
    end process;
end RTL;
```




Variaveis vs. Sinais

- Valores de sinais são assinalados depois da execução do process.
- Apenas o ultimo assinalamento é levado em consideração
- $M \leq A$;
é sobre escrito por $M \leq C$;
- A segunda entrada do somador é conectado a C.

 
```
signal A, B, C, Y, Z : std_logic_vector(7 downto 0);  
begin  
  process (A, B, C)  
    variable M, N : std_logic_vector(7 downto 0);  
  begin  
    M := A;  
    N := B;  
    Z <= M + N;  
    M := C;  
    Y <= M + N;  
  end process;
```


 
```
signal A, B, C, Y, Z : std_logic_vector(7 downto 0);  
signal M, N : std_logic_vector(7 downto 0);  
begin  
  process (A, B, C, M, N)  
  
  begin  
    M <= A;  
    N <= B;  
    Z <= M + N;  
    M <= C;  
    Y <= M + N;  
  end process;
```



Uso de Variaveis

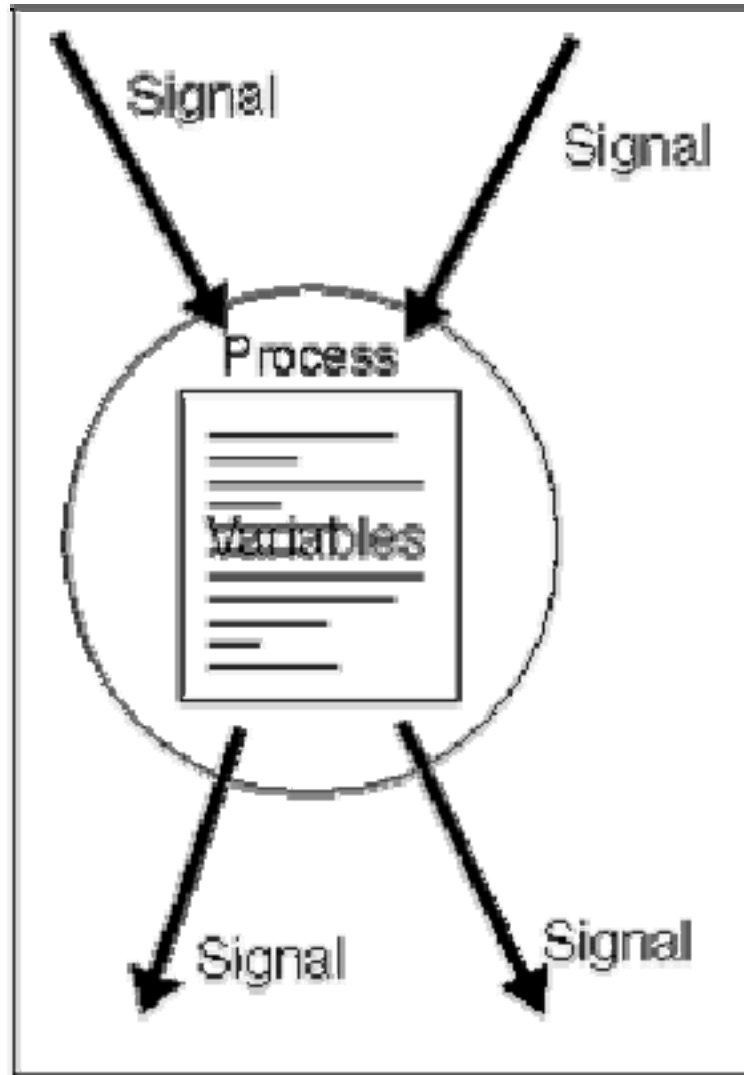

Global Variables (VHDL'93)

```
architecture BEHAVE of SHARED is
    shared variable S : integer;
begin
    process (A, B)
    begin
        S := A + B;
    end process;

    process (A, B)
    begin
        S := A - B;
    end process;
end BEHAVE;
```

Acessível por todos os processos.

Não é sintetizável

Pode ocasionar erros muito comuns de valores de saída indeterminado.

Comando: FOR Loops

```
entity FOR_LOOP is
  port (A : in integer range 0 to 3;
        Z : out std_logic_vector (3 downto 0));
end FOR_LOOP;
```

```
architecture EXAMPLE of FOR_LOOP is
begin
  process (A)
  begin
    Z <= "0000";
    for I in 0 to 3 loop
      if (A = I) then
        Z(I) <= `1`;
      end if;
    end loop;
  end process;
end EXAMPLE;
```

Se o LOOP é para ser sintetizado, o intervalo do loop não pode depender do valor de um sinal ou variável, ou seja, deve ser totalmente estático o intervalo.

Loop Sintaxe

```
[LOOP_LABEL :]  
for IDENTIFIER in DISCRETE_RANGE loop  
  -- sequential statements  
end loop [LOOP_LABEL] ;
```

```
[LOOP_LABEL :]  
while CONDITION loop  
  -- sequential statements  
end loop [LOOP_LABEL] ;
```

```

entity CONV_INT is
    port (VECTOR: in  bit_vector(7 downto 0);
          RESULT: out integer);
end CONV_INT;

```

```

architecture A of CONV_INT is
begin
    process(VECTOR)
        variable TMP: integer;

    begin
        TMP := 0;

        for I in 7 downto 0 loop
            if (VECTOR(I)='1') then
                TMP := TMP + 2**I;
            end if;
        end loop;

        RESULT <= TMP;
    end process;
end A;

```

```

architecture B of CONV_INT is
begin
    process(VECTOR)
        variable TMP: integer;

    begin
        TMP := 0;

        for I in VECTOR'range loop
            if (VECTOR(I)='1') then
                TMP := TMP + 2**I;
            end if;
        end loop;

        RESULT <= TMP;
    end process;
end B;

```

```

architecture C of CONV_INT is
begin
    process(VECTOR)
        variable TMP: integer;
        variable I      : integer;

    begin
        TMP := 0;
        I := VECTOR'high;
        while (I >= VECTOR'low) loop
            if (VECTOR(I)='1') then
                TMP := TMP + 2**I;
            end if;
            I := I - 1;
        end loop;
        RESULT <= TMP;
    end process;
end C;

```

Geração de código

```
[LOOP_LABEL :]  
for IDENTIFIER in DISCRETE_RANGE generate  
  -- statements  
end generate [LOOP_LABEL] ;
```

```
signal A, B : std_logic_vector(8 downto 0);  
signal F : std_logic_vector(7 downto 0);
```

```
architecture B of CONV_INT is  
begin  
t1: for l in 1 to 7 generate  
  F(i) <= A(l+1) or B(l-1);  
  end generate;  
end B;
```

```

entity PARITY is
  port (DATA: in  std_logic_vector (3 downto 0);
        ODD : out std_logic);
end PARITY;

```

architecture RTL of PARITY is
begin

```

  process (DATA)

```

```

    variable TMP : bit;

```

```

  begin

```

```

    TMP := `0`;

```

```

    for I in DATA`low to DATA`high loop

```

```

      TMP := TMP xor DATA(I);

```

```

    end loop;

```

```

    ODD <= TMP;

```

```


  end process;

```

```

end RTL;

```

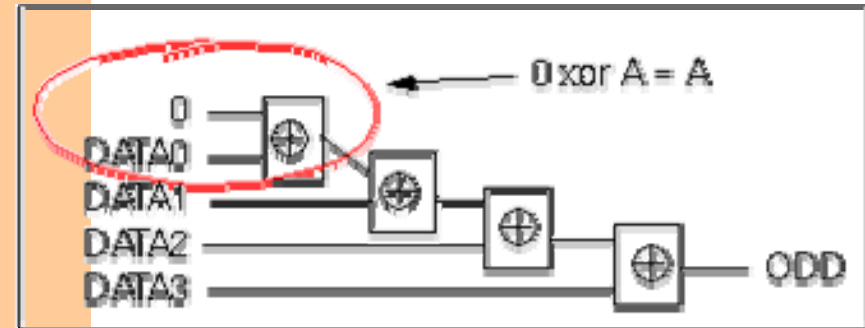

Comando: WAIT

O comando wait' para a execução do process

– O process é continuado quando a instrução é completada.

– wait para um especifico tempo

– wait por um evento do sinal

– wait por uma condição verdadeira
(necessita de um evento do sinal)

– indefinido (process não é mais ativado)


WAIT Statement: Exemplos

```
STIMULUS: process
begin
    SEL    <= `0`;
    BUS_B <= "0000";
    BUS_A <= "1111";
    wait for 10 ns;

    SEL <= `1`;
    wait for 10 ns;

    SEL <= `0`;
    wait for 10 ns;

    wait;
end process STIMULUS;
```

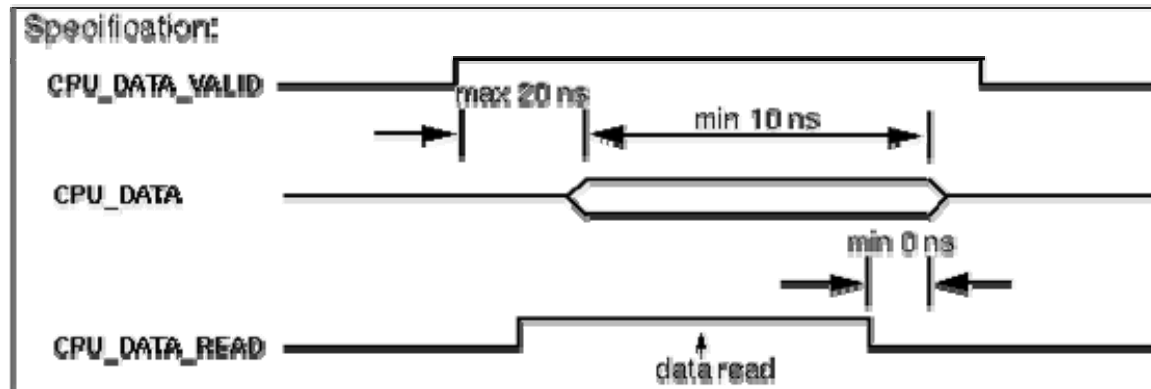

```

READ_CPU : process
begin
    wait until CPU_DATA_VALID = `1`;
    CPU_DATA_READ <= `1`;
    wait for 20 ns;
    LOCAL_BUFFER <= CPU_DATA;
    wait for 10 ns;
    CPU_DATA_READ <= `0`;
end process READ_CPU;

```

WAIT Statement: Exemplos

```
entity FF is
  port (D, CLK : in bit;
        Q      : out bit);
end FF;

architecture BEH_2 of FF is
begin
  process
  begin
    wait until CLK='1';

    Q <= D;

  end process;
end BEH_2;
```

Aprendendo por exemplos

Recapitulando VHDL de comandos que geram circuitos combinacionais

Somador 1 bit

Comandos concorrentes de atribuição simples

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity somador1bit is
  Port ( a : in  STD_LOGIC;
        b : in  STD_LOGIC;
        cin : in  STD_LOGIC;
        sum : out STD_LOGIC;
        cout : out STD_LOGIC);
end somador1bit;

architecture Behavioral of somador1bit is

begin

sum <= a xor b xor cin;
cout <= (a and b) or (a and cin) or (b and cin);

end Behavioral;
```

Somador 8 bits

Comandos concorrentes de atribuição simples e instanciação hierarquica de Componentes.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity somador8bits is
  Port ( dadoa : in  STD_LOGIC_VECTOR (7 downto 0);
        dadob : in  STD_LOGIC_VECTOR (7 downto 0);
        carry_in : in  STD_LOGIC;
        dado_soma : out  STD_LOGIC_VECTOR (7 downto 0);
        carry_out : out  STD_LOGIC);
end somador8bits;

architecture Behavioral of somador8bits is

  component somador1bit is
    Port ( a : in  STD_LOGIC;
          b : in  STD_LOGIC;
          cin : in  STD_LOGIC;
          sum : out  STD_LOGIC;
          cout : out  STD_LOGIC);
  end component;

  signal carry_int : std_logic_vector(6 downto 0);

begin

  bit0: somador1bit
  port map(dadoa(0), dadob(0), carry_in, dado_soma(0), carry_int(0));
  bit1: somador1bit
  port map(dadoa(1), dadob(1), carry_int(0), dado_soma(1), carry_int(1));
  bit2: somador1bit
  port map(dadoa(2), dadob(2), carry_int(1), dado_soma(2), carry_int(2));
  bit3: somador1bit
  port map(dadoa(3), dadob(3), carry_int(2), dado_soma(3), carry_int(3));
  bit4: somador1bit
  port map(dadoa(4), dadob(4), carry_int(3), dado_soma(4), carry_int(4));
  bit5: somador1bit
  port map(dadoa(5), dadob(5), carry_int(4), dado_soma(5), carry_int(5));
  bit6: somador1bit
  port map(dadoa(6), dadob(6), carry_int(5), dado_soma(6), carry_int(6));
  bit7: somador1bit
  port map(dadoa(7), dadob(7), carry_int(6), dado_soma(7), carry_out);

end Behavioral;
```

Somador de 8 bits

Uso de componentes e do comando FOR - GENERATE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity somador8bits_vfor is
  Port ( dadoa : in  STD_LOGIC_VECTOR (7 downto 0);
        dadob : in  STD_LOGIC_VECTOR (7 downto 0);
        carry_in : in  STD_LOGIC;
        dado_soma : out  STD_LOGIC_VECTOR (7 downto 0);
        carry_out : out  STD_LOGIC);
end somador8bits_vfor;

architecture Behavioral of somador8bits_vfor is

  component somador1bit is
    Port ( a : in  STD_LOGIC;
          b : in  STD_LOGIC;
          cin : in  STD_LOGIC;
          sum : out  STD_LOGIC;
          cout : out  STD_LOGIC);
  end component;

  signal carry_int : std_logic_vector(7 downto 0);

  bit0: somador1bit
  port map(dadoa(0), dadob(0), carry_in, dado_soma(0), carry_int(0));

  I1: for i in 1 to 7 generate
  bitx: somador1bit
  port map(dadoa(i), dadob(i), carry_int(i-1), dado_soma(i), carry_int(i));
  end generate;

  carry_out <= carry_int(7);

end Behavioral;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity comparador_4bits is
  Port ( dadox : in  STD_LOGIC_VECTOR (3 downto 0);
        dadoy : in  STD_LOGIC_VECTOR (3 downto 0);
        comp : out STD_LOGIC_VECTOR (1 downto 0));
end comparador_4bits;
```

```
architecture Behavioral of comparador_4bits is
```

```
begin

process(dadox, dadoy)
begin
  if (dadox>dadoy) then
    comp <= "10";
  elsif (dadox=dadoy) and dadox="1111" then
    comp <= "11";
  elsif (dadox=dadoy) and dadox="0000" then
    comp <= "00";
  else
    comp <= "01";
  end if;
end process;


end Behavioral;
```

Multiplexador

USA PROCESS e comandos sequenciais como CASE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux is
  Port ( d0 : in  STD_LOGIC_VECTOR (7 downto 0);
        d1 : in  STD_LOGIC_VECTOR (7 downto 0);
        d2 : in  STD_LOGIC_VECTOR (7 downto 0);
        d3 : in  STD_LOGIC_VECTOR (7 downto 0);
        d4 : in  STD_LOGIC_VECTOR (7 downto 0);
        d5 : in  STD_LOGIC_VECTOR (7 downto 0);
        d6 : in  STD_LOGIC_VECTOR (7 downto 0);
        d7 : in  STD_LOGIC_VECTOR (7 downto 0);
        sel : in  STD_LOGIC_VECTOR (2 downto 0);
        out_mux : out  STD_LOGIC_VECTOR (7 downto 0));
end mux;
```

 

architecture Behavioral of mux is

begin

```
process(d0, d1, d2, d3, d4, d5, d6, d7, sel)
begin
  case sel is
    WHEN "000" => out_mux <=d0;
    WHEN "001" => out_mux <=d1;
    WHEN "010" => out_mux <=d2;
    WHEN "011" => out_mux <=d3;
    WHEN "100" => out_mux <=d4;
    WHEN "101" => out_mux <=d5;
    WHEN "110" => out_mux <=d6;
    WHEN others => out_mux <=d7;
  end case;
end process;
```

end Behavioral;

ULA de 8 bits c/ 4 operações

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity ULA_8bits is  
  Port ( A : in  STD_LOGIC_VECTOR (8 downto 0);  
        B : in  STD_LOGIC_VECTOR (8 downto 0);  
        controle : in  STD_LOGIC_VECTOR(1 downto 0);  
        saida : out  STD_LOGIC_VECTOR (8 downto 0));  
end ULA_8bits;
```

architecture Behavioral of ULA_8bits is

begin

```
process(A, B, controle)
```

```
begin
```

```
  CASE controle IS
```

```
    WHEN "00" => saida <= A + B;
```

```
    WHEN "01" => saida <= A - B;
```


```
    WHEN "10" => saida <= A xor B;
```

```
    WHEN others => saida <= A and (not B);
```

```
  END CASE;
```

```
end process;
```

```
end Behavioral;
```

 

ULA de 8 bits c/ 4 operações

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;


entity ULA_8bits_sp is
    Port ( A : in STD_LOGIC_VECTOR (8 downto 0);
          B : in STD_LOGIC_VECTOR (8 downto 0);
          controle : in STD_LOGIC_VECTOR(1 downto 0);
          saida : out STD_LOGIC_VECTOR (8 downto 0));
end ULA_8bits_sp;

architecture Behavioral of ULA_8bits_sp is

begin

saida <= A+B when controle="00" else
        A-B when controle="01" else
        A xor B when controle="10" else
        A and (not B);

end Behavioral;
```

 

Implementação de circuitos sequenciais

Sensíveis ao relógio (clk)

Clocked Process: Detecção da borda do Clock

```
if  
clock_signal_name'EVENT and clock_signal_name='1'  
clock_signal_name='1' and clock_signal_name'EVENT  
not clock_signal_name'STABLE and clock_signal_name='1'  
clock_signal_name='1' and not clock_signal_name'STABLE  
RISING_EDGE ( clock_signal_name )
```

IEEE 1076.6 is not fully supported by all tools

Clocked Process: Clock Edge Detection

wait until

- ***clock_signal_name*'EVENT and *clock_signal_name*='1'**
- ***clock_signal_name*='1' and *clock_signal_name*'EVENT**
- **not *clock_signal_name*'STABLE and *clock_signal_name*='1'**
- ***clock_signal_name*='1' and not *clock_signal_name*'STABLE**
- **RISING_EDGE (*clock_signal_name*)**
- ***clock_signal_name*='1'**

IEEE 1076.6 is not fully supported by all tools

Detection of a Rising Edge by Use of Functions

- Defined in std_logic_1164 package

```
process
begin
    wait until RISING_EDGE (CLK);
    Q <= D;
end process;
```

```
function RISING_EDGE (signal CLK : std_ulogic)
    return boolean is
begin
    if (CLK`event and CLK = `1` and CLK`last_value = `0`) then
        return true;
    else
        return false;
    end if;
end RISING_EDGE;
```

Clocked Process: Rules

```
process
begin
  wait until CLK'event and CLK='1';
  if RESET = '1' then
    -- synchronous register reset
  else
    -- combinatorics
  end if;
end process;
```

```
process(CLK, RST)
begin
  if (RST = `1`) then
    -- asynchronous register reset
  elsif (CLK`event and CLK=`1`) then
    -- combinatorics
  end if;
end process;
```

Elementos de memória são inferidos, ou seja, gerados sempre que os sinais receberem assinalamentos dentro de uma process controlado por relógio (clock)

Wait-form:
no sensitivity list
Synchronous reset

If-form:
only clock and asynchronous signals (reset) in sensitivity list
Synchronous and asynchronous reset

Registrador: Asynchronous Set/Reset

```
library IEEE;
use IEEE.std_logic_1164.all;

entity ASYNC_FF is
port (
CLK, SET, RST : in std_logic;
D : in std_logic_vector(7 downto 0);
Q : out std_logic_vector(7 downto 0));
end ASYNC_FF;

architecture RTL of ASYNC_FF is
begin
process (CLK, RST, SET)
begin
if (RST = `1`) then
Q <= `0`;
elsif SET = '1' then
Q <= '1';
elsif (CLK`event and CLK = `1`) then
Q <= D;
end if;
end process;
end RTL;
```

Registrador: Synchronous Set/Reset

```
library IEEE;
use IEEE.std_logic_1164.all;

entity ASYNC_FF is
port (
CLK, SET, RST : in std_logic;
D : in std_logic_vector(7 downto 0);
Q : out std_logic_vector(7 downto 0));
end ASYNC_FF;

architecture RTL of ASYNC_FF is
begin
process (CLK)
begin
if (CLK'event and CLK = '1') then
if (RST = '1') then
Q <= `0`;
elsif SET = '1' then
Q <= '1';
else
Q <= D;
end if;
end if;
end process;
end RTL;
```

Registrador: Synchronous Set/Reset

```
library IEEE;
use IEEE.std_logic_1164.all;

entity ASYNC_FF is
port (D, CLK, SET, RST : in std_logic;
      Q : out std_logic);
end ASYNC_FF;

architecture RTL of ASYNC_FF is
begin
  process (CLK)
  begin
    if (CLK`event and CLK = `1`) then
      if (RST = `1`) then
        Q <= `0`;
      elsif SET = '1' then
        Q <= '1';
      else
        Q <= D;
      end if;
    end if;
  end process;
end RTL;
```

Registrador Contador

```
library IEEE;
use IEEE.std_logic_1164.all;

entity COUNTER is
port (CLK: in std_logic;
      Q  : out std_logic_vector(3 downto 0);
end COUNTER;

architecture RTL of COUNTER is
signal COUNT : std_logic_vector(3 downto 0);
begin
process (CLK)
begin
if CLK'event and CLK = '1' then
if (COUNT >= "1001") then
COUNT <= "0000";
else
COUNT <= COUNT + 1;
end if;
end if;
end process;

Q <= COUNT ;
```

COUNT: 4 flip flops

Q: not used in clocked process pois é um pino de saída e NÃO pode ser lido no process.

